




**Sensing, Computing, Actuating**

Sander Stuijk ([s.stuijk@tue.nl](mailto:s.stuijk@tue.nl))

# RESISTIVE STRAIN SENSORS

(Chapter 5.8)

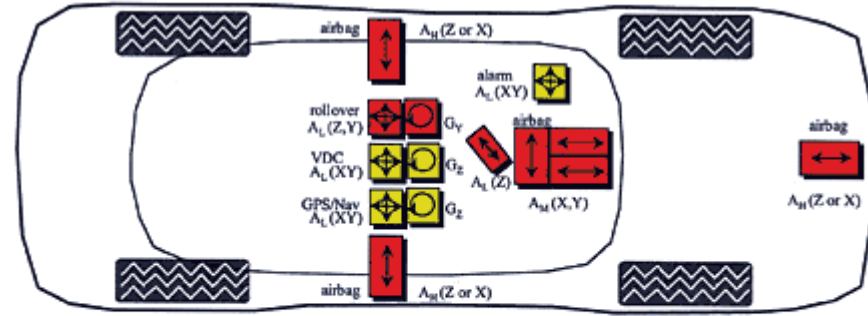


**Legend**  
 G = Gyro  
 A = Acceleration  
 • L = low (<5g)  
 • M = medium (50g)  
 • H = high (>100g)  
 ■ Airbag system  
 ■ Non-Airbag system


- Fuel efficient engines and transmissions
- Power conserving climate control systems
- Cost effective air / fuel management



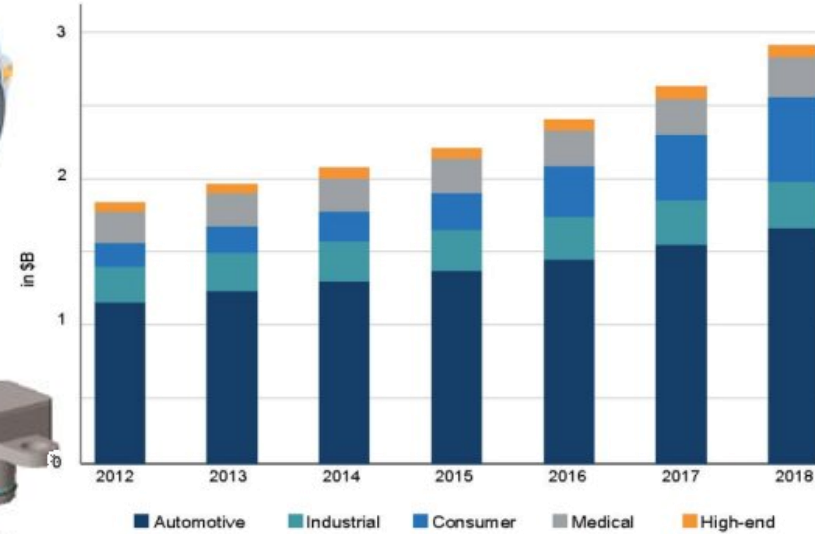MEMS pressure sensor market forecast by applications 2012-2018



(Vale Développement, April 2013)

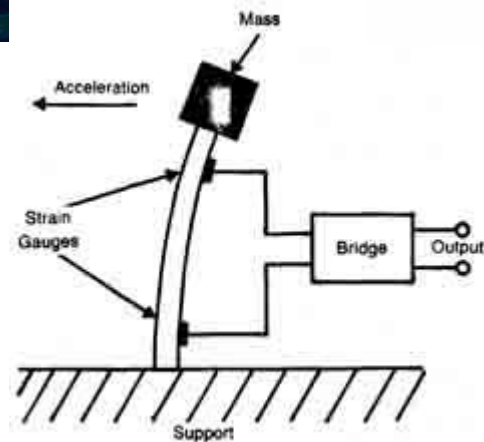


quantity	excitation	physical effect	sensor
<b>strain</b>	<b>active</b>	<b>resistive effect</b>	<b>strain gauge</b>
acceleration	active	capacitance	capacitive accelerometer
acceleration	active	inductance	inductive accelerometer
acceleration	active	resistive effect	piezoresistive accelerometer
pressure	active	capacitance	capacitive pressure sensor
pressure	active	resistive effect	piezoresistive sensor

resistive effect in strain gauge plays an important role in many sensors for different quantities


- resistance of a wire

$$R = \rho \frac{l}{a} = \frac{m}{ne^2\tau} \frac{l}{a}$$

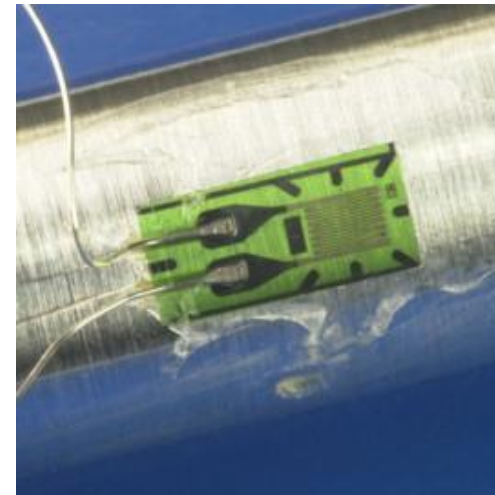- changing **temperature** affects resistance (**thermoresistive effect**)
- changing **dimensions** affects resistance (**piezoresistive effect**)
  
- **strain gauges** use piezoresistive effect to sense mechanical stress
- sensor based on strain gauges convert mechanical energy to electrical energy
  
- thermoresistive effect is an error source




- force leads to deformation of object

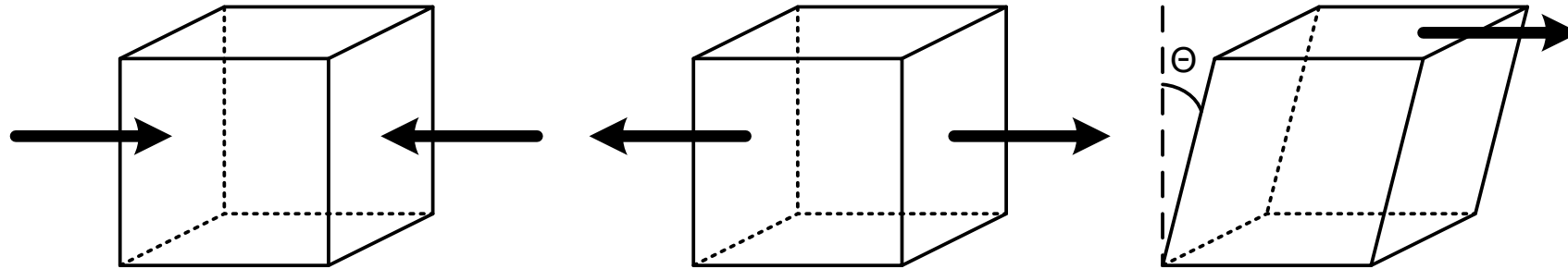

- measuring deformation provides opportunity to sense mechanical force, which in turn is related to
  - torque
  - pressure
  - acceleration
  - mass
  - ...



- force leads to deformation of object

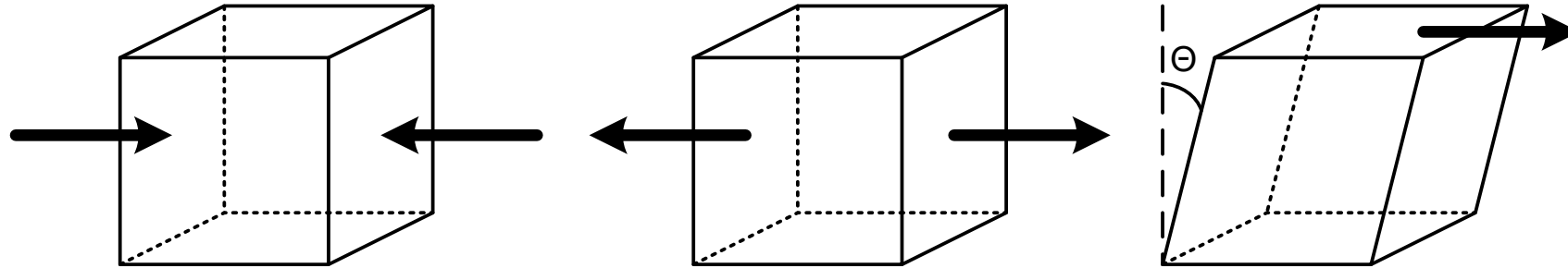

- deformation depends on force per area which is called **stress** ( $\sigma$ )


$$\sigma = \frac{F}{a}$$

- deformation also depends on
  - material properties
  - length or volume of object
- deformation per unit length (or volume) is called **strain** ( $\epsilon$ )

$$\epsilon = \frac{dl}{l}$$



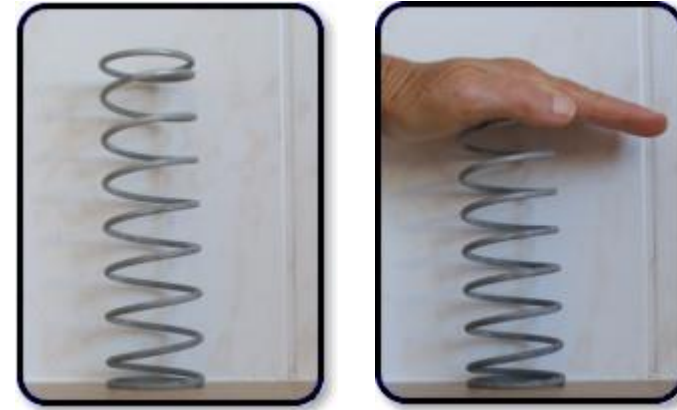
- object deform under force and restores to original state when force is removed (**elasticity**)
- materials resist deformation (**rigidity**)



- change in length due to force  $F$  given by Hooke's law

$$\sigma = \frac{F}{a} = E\varepsilon = E \frac{dl}{l}$$

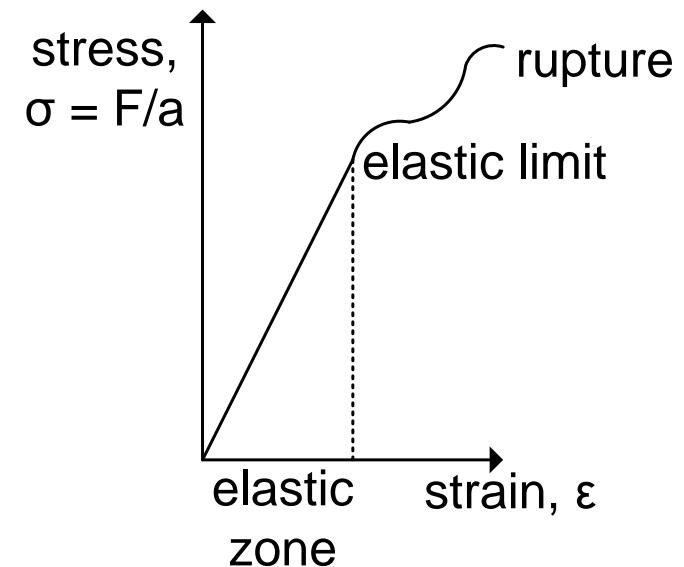- $E$  – Young's modulus, which depends on
  - material
  - temperature
- $\varepsilon$  – strain (unit deformation, dimensionless)
- strain and stress are proportional in elastic zone



- resistance of a wire

$$R = \rho \frac{l}{a}$$



- stretching wire longitudinally changes resistance


$$\frac{dR}{R} = \frac{\Delta\rho}{\rho} + \frac{\Delta l}{l} - \frac{\Delta a}{a}$$

- use  $-\Delta a$  since area decreases when wire is stretched ( $+\Delta l$ )
- change in length due to force  $F$  given by Hooke's law

$$\sigma = \frac{F}{a} = E\varepsilon = E \frac{dl}{l}$$

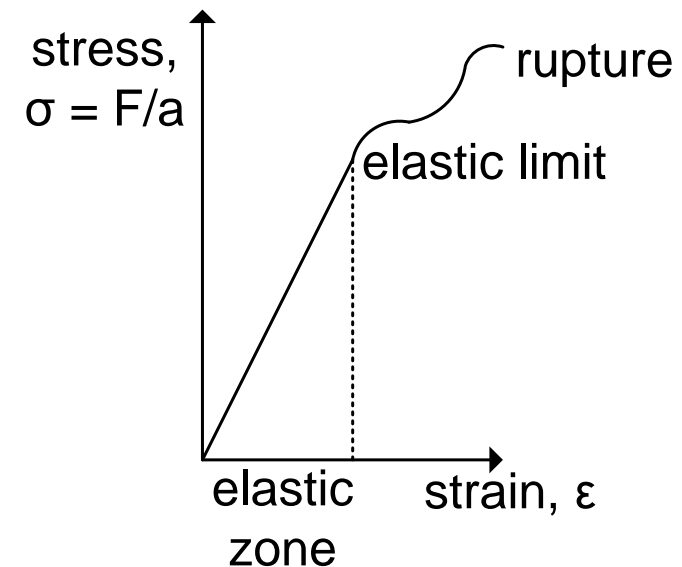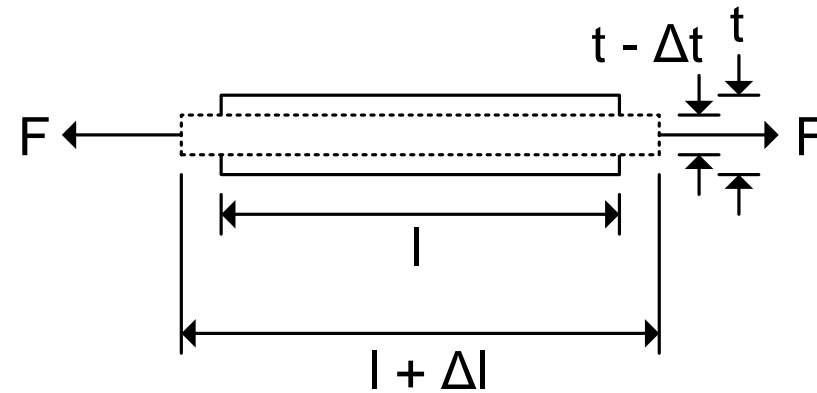- $E$  – Young's modulus, which depends on
    - material
    - temperature
  - $\varepsilon$  – strain (unit deformation, dimensionless)
- strain and stress are proportional in elastic zone



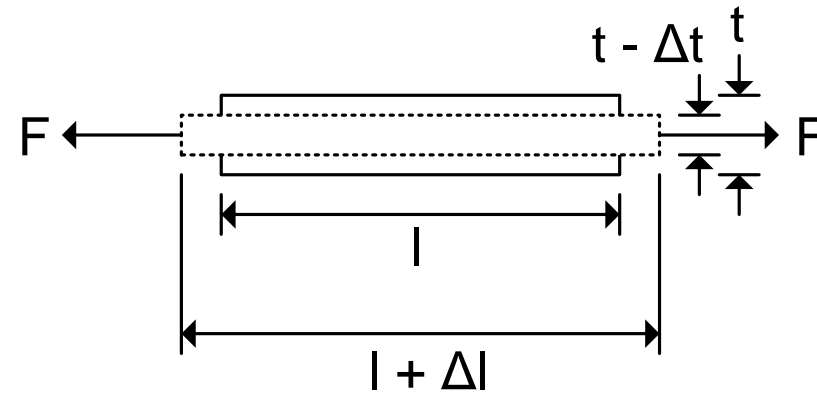


- longitudinal stress changes
  - length of wire ( $l$ )
  - thickness of wire ( $t$ )

- **Poisson ratio** gives relation between change in length and thickness

$$\nu = -\frac{dt/t}{dl/l}$$

- Poisson ratio of perfectly compressible material: 0.0 (e.g. cork)
  - deformation in one direction does not change other direction
- Poisson ratio of incompressible material: 0.5 (e.g. rubber)
  - volume of this material is constant when stress is applied

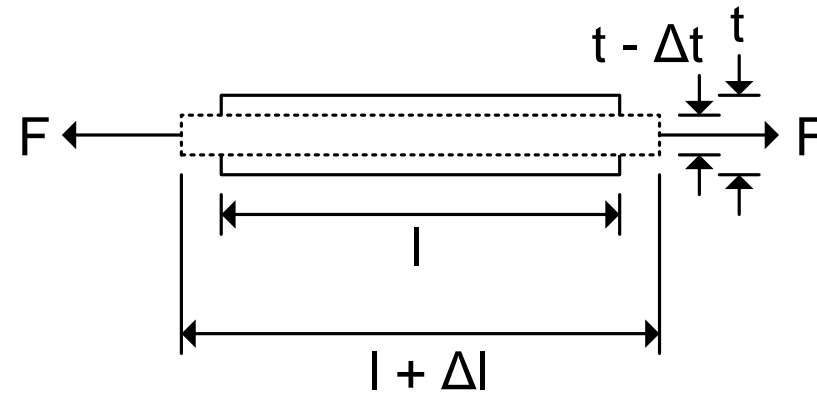- longitudinal stress changes
  - length of wire ( $l$ )
  - thickness of wire ( $t$ )




- Poisson ratio gives relation between change in length and thickness

$$\nu = -\frac{dt/t}{dl/l}$$

- Poisson ratio of metals:  $0 < \nu < 0.5$ 
  - volume of metal changes when deformed
  - cross-sectional area changes** when metals are deformed
  - using same approach as used for volume we can show

$$a = \pi \cdot \left(\frac{t}{2}\right)^2 \Rightarrow \frac{da}{a} = \frac{2dt}{t} \quad \left. \vphantom{\frac{da}{a} = \frac{2dt}{t}} \right\} \Rightarrow \frac{da}{a} = -2\nu \frac{dl}{l}$$
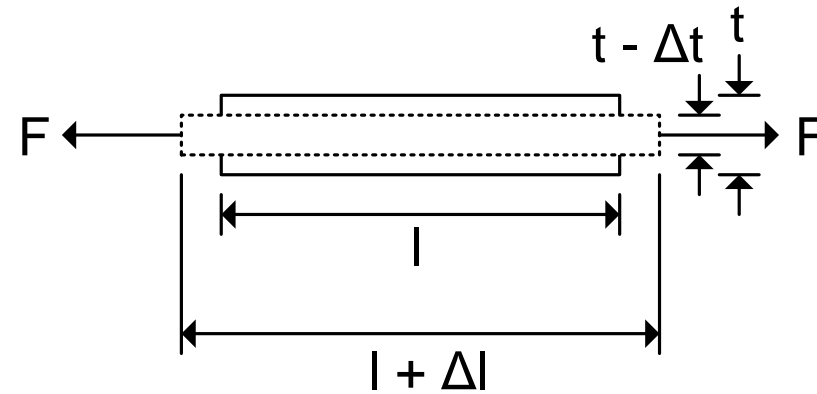
$$\nu = -\frac{dt/t}{dl/l} \Rightarrow \frac{dt}{t} = -\nu \frac{dl}{l}$$



- longitudinal stress changes
  - length of wire ( $l$ )
  - thickness of wire ( $t$ )


- Poisson ratio gives relation between change in length and thickness

$$\nu = -\frac{dt/t}{dl/l}$$

- Poisson ratio of metals:  $0 < \nu < 0.5$ 
  - volume of metal changes** when deformed
  - consider a circular wire with diameter  $t$  (and thus radius:  $t/2$ )
  - change in volume per unit volume is then equal to

$$V = \pi \cdot \left(\frac{t}{2}\right)^2 \cdot l \Rightarrow \frac{dV}{V} = \frac{dl}{l} + \frac{2dt}{t}$$
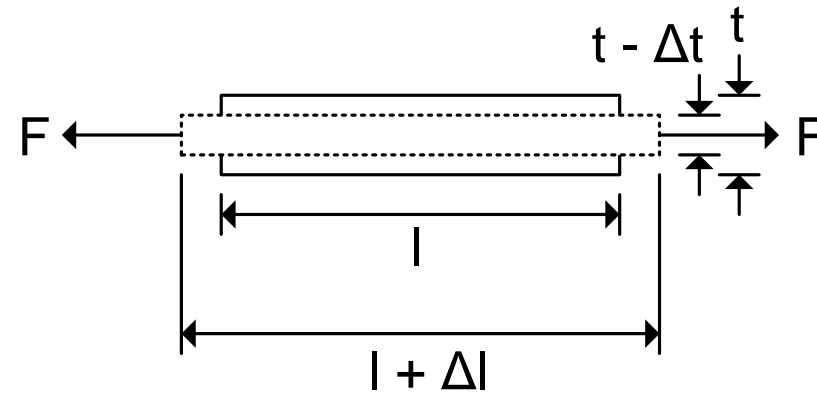
$$\left. \begin{array}{l} \frac{dV}{V} = \frac{dl}{l} + \frac{2dt}{t} \\ \nu = -\frac{dt/t}{dl/l} \Rightarrow \frac{dt}{t} = -\nu \frac{dl}{l} \end{array} \right\} \Rightarrow \frac{dV}{V} = \frac{dl}{l} - 2\nu \frac{dl}{l} = \frac{dl}{l} (1 - 2\nu)$$



- longitudinal stress changes
  - length of wire ( $l$ )
  - thickness of wire ( $t$ )

- Poisson ratio gives relation between change in length and thickness


$$\nu = -\frac{dt/t}{dl/l}$$

- Poisson ratio of metals:  $0 < \nu < 0.5$ 
  - volume of metal changes when deformed
  - because of volume change
    - amplitude of vibrations in metal lattice changes
  - results in **change of specific resistivity** (for metals)

$$\frac{d\rho}{\rho} = C \frac{dV}{V}$$

- $C$  – Bridgman's constant

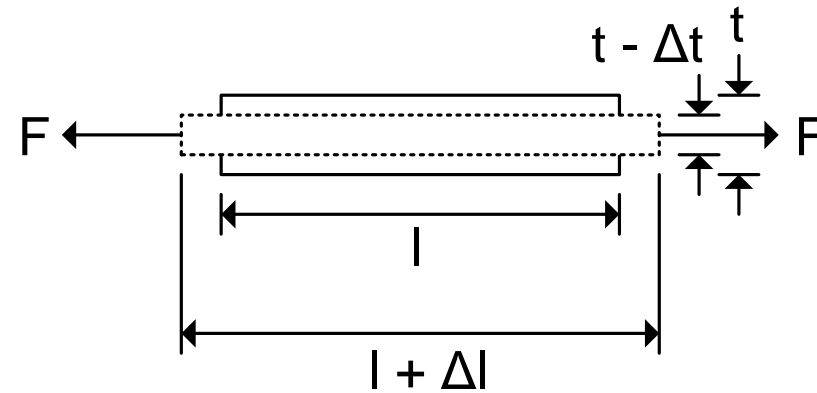- longitudinal stress changes
  - length of wire ( $l$ )
  - thickness of wire ( $t$ )



- stretching wire longitudinally changes resistance

$$\frac{dR}{R} = \frac{d\rho}{\rho} + \frac{dl}{l} - \frac{da}{a}$$

- using results found so far we find

$$\frac{dR}{R} = \frac{d\rho}{\rho} + \frac{dl}{l} - \frac{da}{a}$$

$$\frac{d\rho}{\rho} = C \frac{dV}{V}$$

$$\left. \begin{array}{l} \frac{dR}{R} = \frac{d\rho}{\rho} + \frac{dl}{l} - \frac{da}{a} \\ \frac{d\rho}{\rho} = C \frac{dV}{V} \end{array} \right\} \Rightarrow \frac{dR}{R} = C \frac{dV}{V} + \frac{dl}{l} - \frac{da}{a}$$

$$\frac{dV}{V} = \frac{dl}{l}(1 - 2\nu), \quad \frac{da}{a} = -2\nu \frac{dl}{l}$$

$$\left. \begin{array}{l} \frac{dR}{R} = C \frac{dV}{V} + \frac{dl}{l} - \frac{da}{a} \\ \frac{dV}{V} = \frac{dl}{l}(1 - 2\nu), \quad \frac{da}{a} = -2\nu \frac{dl}{l} \end{array} \right\} \Rightarrow \frac{dR}{R} = \frac{dl}{l} [C(1 - 2\nu) + 1 + 2\nu]$$

- G – gauge factor

$$\Leftrightarrow \frac{dR}{R} = G \frac{dl}{l}$$

- change in resistance related to change in length

$$\frac{dR}{R} = G \frac{dl}{l}$$

- remember Hooke's law (relates stress  $\sigma$  to strain  $\varepsilon$ )

$$\sigma = \frac{F}{a} = E\varepsilon = E \frac{dl}{l}$$


- change in resistance related to force (per unit area) and strain

$$\frac{dR}{R} = G\varepsilon = G \frac{F}{aE}$$

- strain gauge can be used to sensor force and its derived quantities
- gauge factor is constant for metals, hence

$$R = R_0 + dR = R_0 \left( 1 + \frac{dR}{R_0} \right) = R_0(1 + G\varepsilon) = R_0(1 + x)$$

- typically  $x < 0.002$

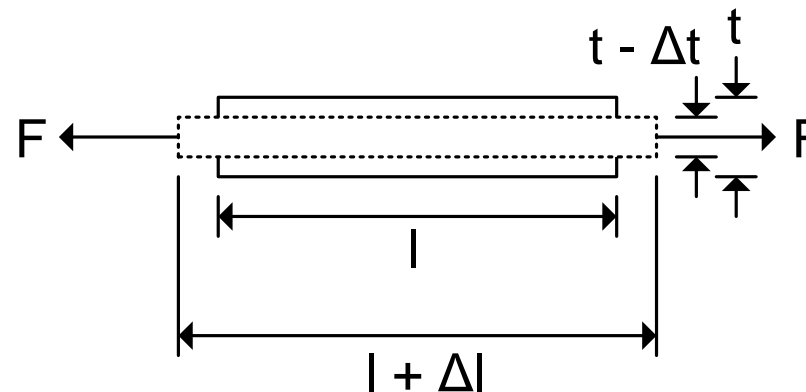



**example – strain gauge attached to aluminum strut**

- strain gauge with  $R = 350 \Omega$  and  $G = 2.1$
- aluminum strut has  $E = 73 \text{ GPa}$
- outer diameter of the strut:  $D = 50 \text{ mm}$
- inner diameter of the strut:  $d = 47.5 \text{ mm}$

**what is the change in resistance when the strut supports a load of 1000 kg?**


- area supporting the force

$$a = \frac{\pi(D^2 - d^2)}{4} = \frac{\pi((50\text{mm})^2 - (47.5\text{mm})^2)}{4} = 191\text{mm}^2$$

- change in resistance

$$\Delta R = RG\varepsilon = RG \frac{F}{aE} = (350\Omega)(2.1) \frac{9800\text{N}}{(191 \cdot 10^{-6}\text{m}^2) \cdot (73 \cdot 10^9\text{Pa})} = 0.5\Omega$$


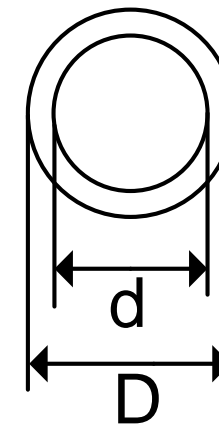
- change in resistance is less than 0.15% of the initial resistance



- bonded strain gauges
  - wires cemented onto a backing or
  - thin film resistor deposited on a substrate
  - resistor forms a long, meandering wire



- strain gauge connected to test object

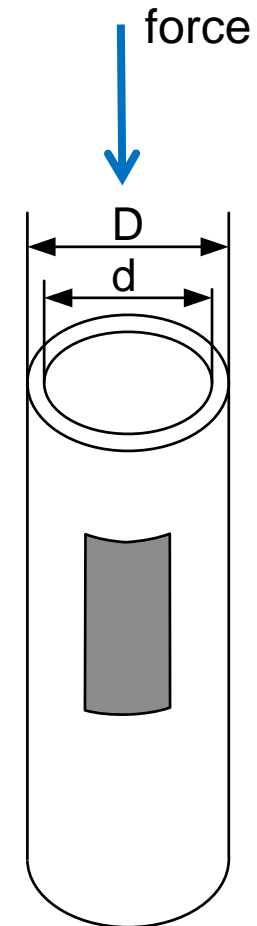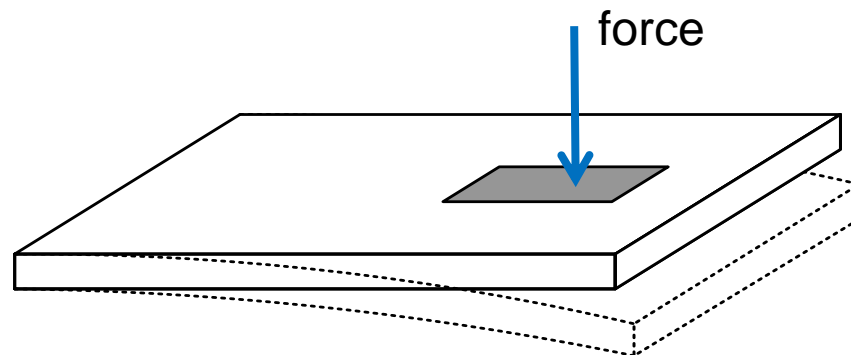

- strain gauge in resistive divider
- stress applied to gauge (resistive change 'x')
- **what is the output voltage  $v_o$ ? (assume  $k = R_1/R_0 = 1$ )**

$$v_o = \left( \frac{R_2}{R_1 + R_2} \right) V_r = \left( \frac{R_0(1+x)}{kR_0 + R_0(1+x)} \right) V_r = \left( \frac{1+x}{k+1+x} \right) V_r$$

non-linearity



- for strain gauges holds that  $x \ll k$  (typically  $x < 0.002$ )

$$v_o \approx \left( \frac{1+x}{k+1} \right) V_r = \frac{1}{k+1} V_r + \frac{x}{k+1} V_r$$


- maximal sensitivity when  $k = 1$

$$v_o \approx \frac{1}{2} V_r + \frac{x}{2} V_r$$

offset voltage

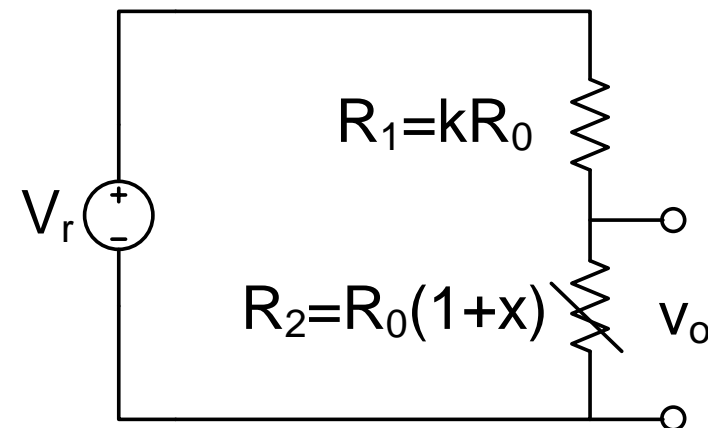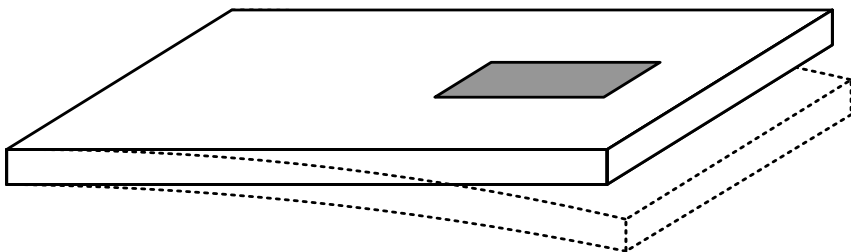

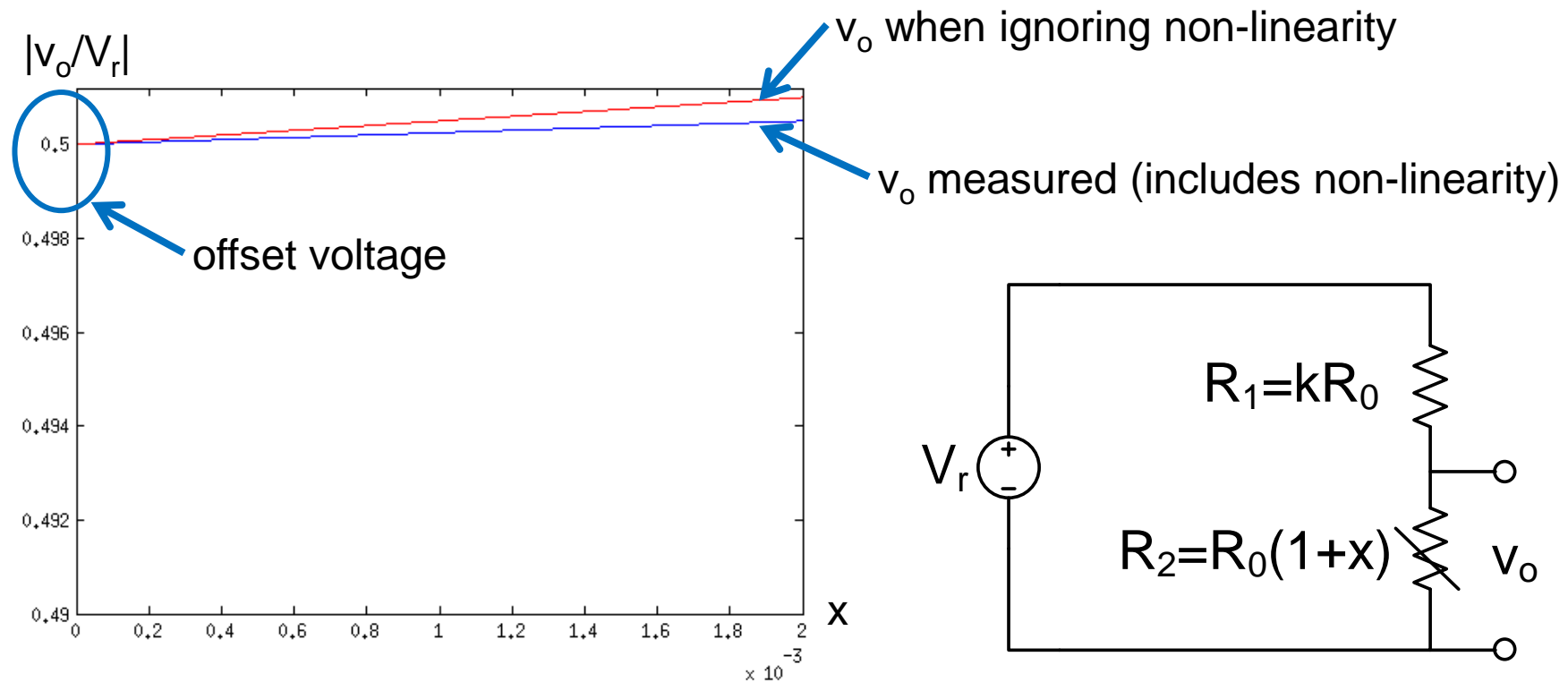- strain gauge in resistive divider
- stress applied to gauge (resistive change 'x')
- two problems when measuring output voltage
  - non-linearity in response
  - offset voltage present





- **remove offset** voltage by placing strain gauge in bridge
- stress applied to gauge (resistive change 'x')
- **what is the output voltage  $v_o$ ? (assume  $k = R_1/R_4 = R_2/R_0 = 1$ )**

$$v_o = \left( \frac{R_4}{R_1 + R_4} - \frac{R_3}{R_2 + R_3} \right) V_r = \left( \frac{R_0}{2R_0} - \frac{R_0(1+x)}{R_0(2+x)} \right) V_r = \left( \frac{1}{2} - \frac{1+x}{2+x} \right) V_r = \left( \frac{-x}{4+2x} \right) V_r \approx -\frac{x}{4} V_r$$

- intermezzo: two sources of non-linearity
  - strain gauge itself does not adhere to  $R = R_0(1+x)$
  - interface circuit causes non-linear resistance – voltage relation

non-linearity

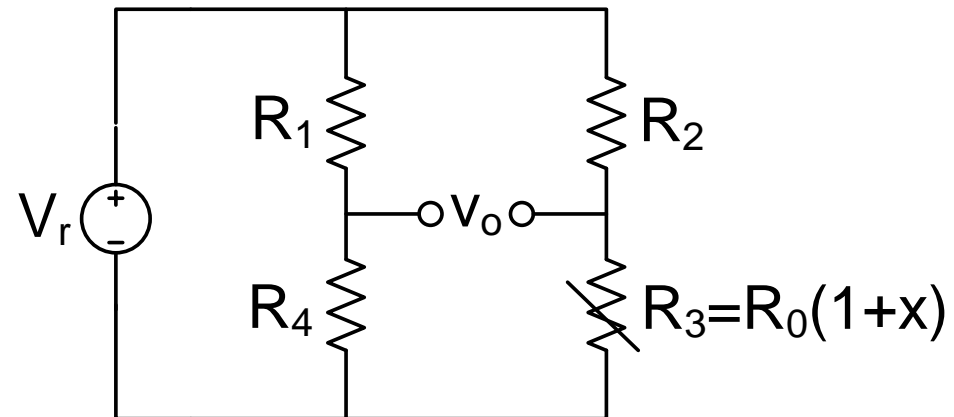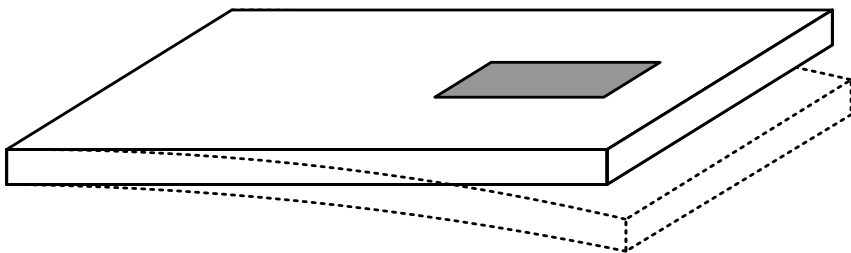



- **remove offset** voltage by placing strain gauge in bridge
- stress applied to gauge (resistive change 'x')
- **what is the output voltage  $v_o$ ? (assume  $k = R_1/R_4 = R_2/R_0 = 1$ )**

$$v_o = \left( \frac{R_4}{R_1 + R_4} - \frac{R_3}{R_2 + R_3} \right) V_r = \left( \frac{R_0}{2R_0} - \frac{R_0(1+x)}{R_0(2+x)} \right) V_r = \left( \frac{1}{2} - \frac{1+x}{2+x} \right) V_r = \left( \frac{-x}{4+2x} \right) V_r \approx -\frac{x}{4} V_r$$

- compare output voltage bridge and divider

$$v_{o,divider} \approx \frac{1}{2} V_r + \frac{x}{2} V_r$$

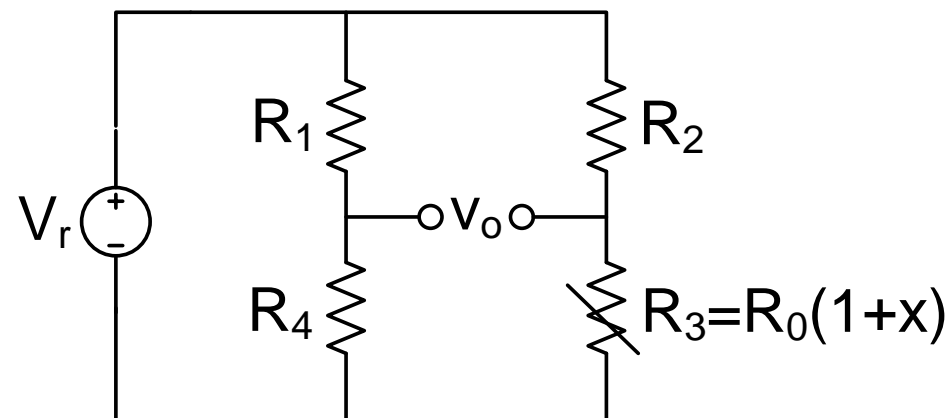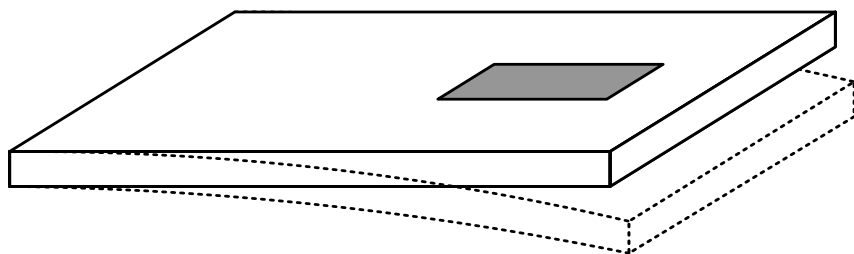- bridge **removes offset**
- bridge **reduces sensitivity**



non-linearity

- **increase sensitivity** by adding extra strain gauge to bridge
- stress applied to gauge (resistive change 'x')
- **what is the output voltage  $v_o$ ? (assume  $k = R_0/R_4 = R_2/R_0 = 1$ )**


$$v_o = \left( \frac{R_4}{R_1 + R_4} - \frac{R_3}{R_2 + R_3} \right) V_r = \left( \frac{R_0}{R_0(2+x)} - \frac{R_0(1+x)}{R_0(2+x)} \right) V_r = \left( \frac{-x}{2+x} \right) V_r \approx -\frac{x}{2} V_r$$

non-linearity

- compare output voltage to single sensor solution

$$v_{o, \text{single}} = \frac{-x}{4+2x} V_r \approx \frac{-x}{4} V_r$$



- extra sensor **increases sensitivity**

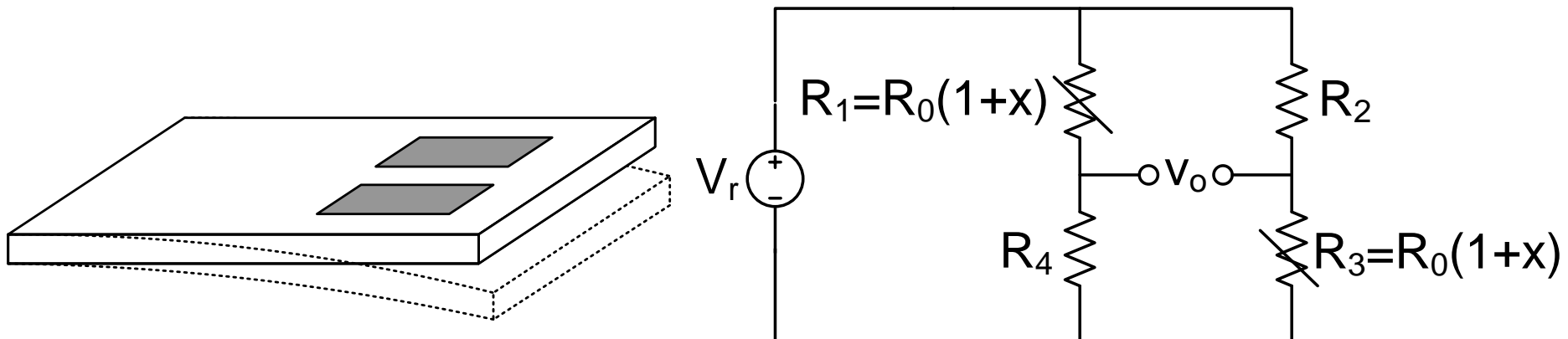


- **remove non-linearity** by adding applying opposing signal to gauge
- stress applied to gauge (resistive change 'x')
- **what is the output voltage  $v_o$ ? (assume  $k = R_0/R_4 = R_1/R_0 = 1$ )**

$$v_o = \left( \frac{R_4}{R_1 + R_4} - \frac{R_3}{R_2 + R_3} \right) V_r = \left( \frac{R_0}{2R_0} - \frac{R_0(1+x)}{R_0(1-x) + R_0(1+x)} \right) V_r = \left( \frac{R_0}{2R_0} - \frac{R_0(1+x)}{2R_0} \right) V_r = \frac{-x}{2} V_r$$

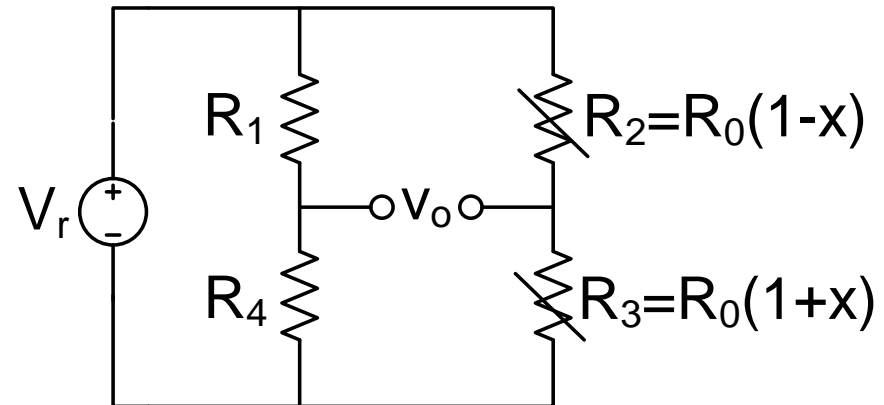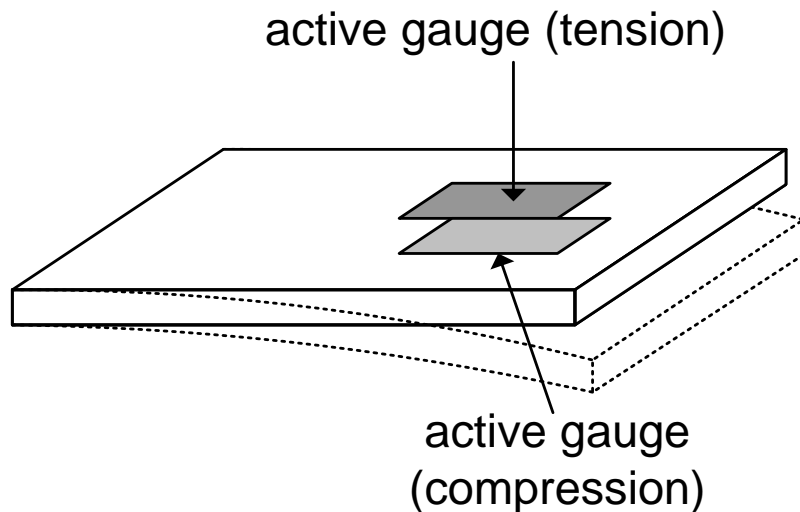- **sensitivity equal** to previous arrangement
- **non-linearity removed**






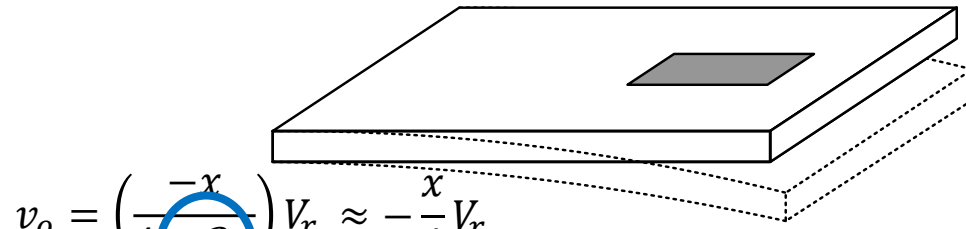

$$v_o = \left( \frac{-x}{4+2x} \right) V_r \approx -\frac{x}{4} V_r$$

non-linearity

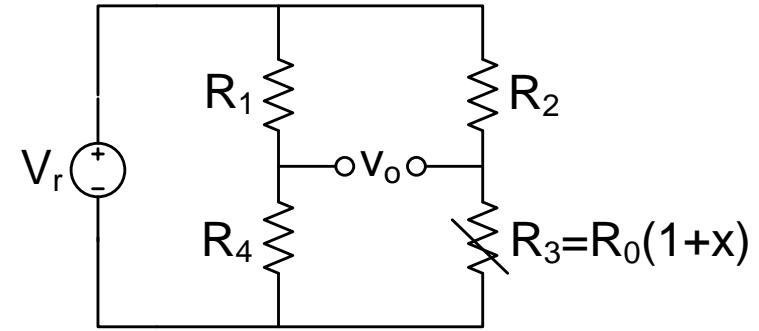


$$v_o = \left( \frac{-x}{2+x} \right) V_r \approx -\frac{x}{2} V_r$$

non-linearity


increased  
sensitivity

active gauge (tension)

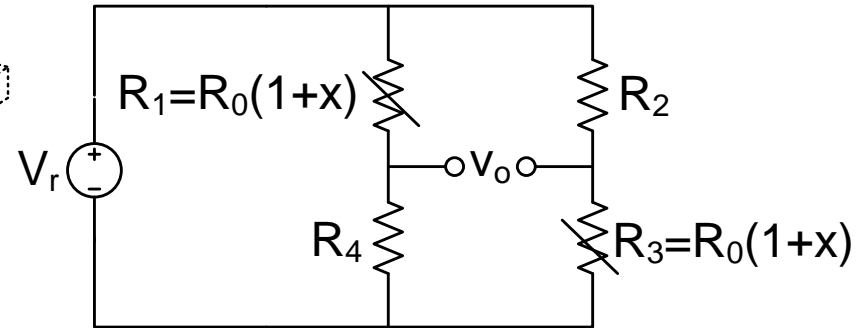

$$v_o = \frac{-x}{2} V_r$$


active gauge  
(compression)

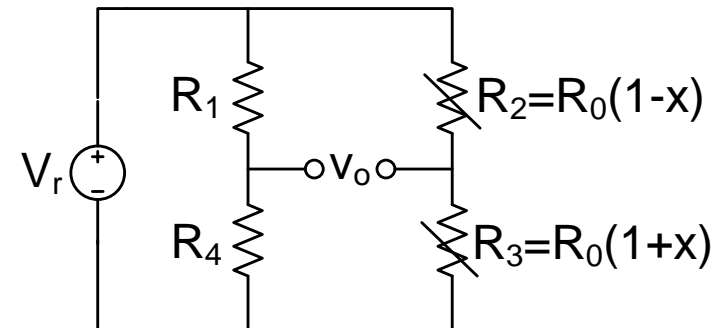

- add more strain gauges to **increase sensitivity**
- stress applied to gauge (resistive change 'x')
- **what is the output voltage  $v_o$ ?**

$$v_o = \left( \frac{R_4}{R_1 + R_4} - \frac{R_3}{R_2 + R_3} \right) V_r = \left( \frac{R_0(1-x)}{R_0(1+x) + R_0(1-x)} - \frac{R_0(1+x)}{R_0(1-x) + R_0(1+x)} \right) V_r$$


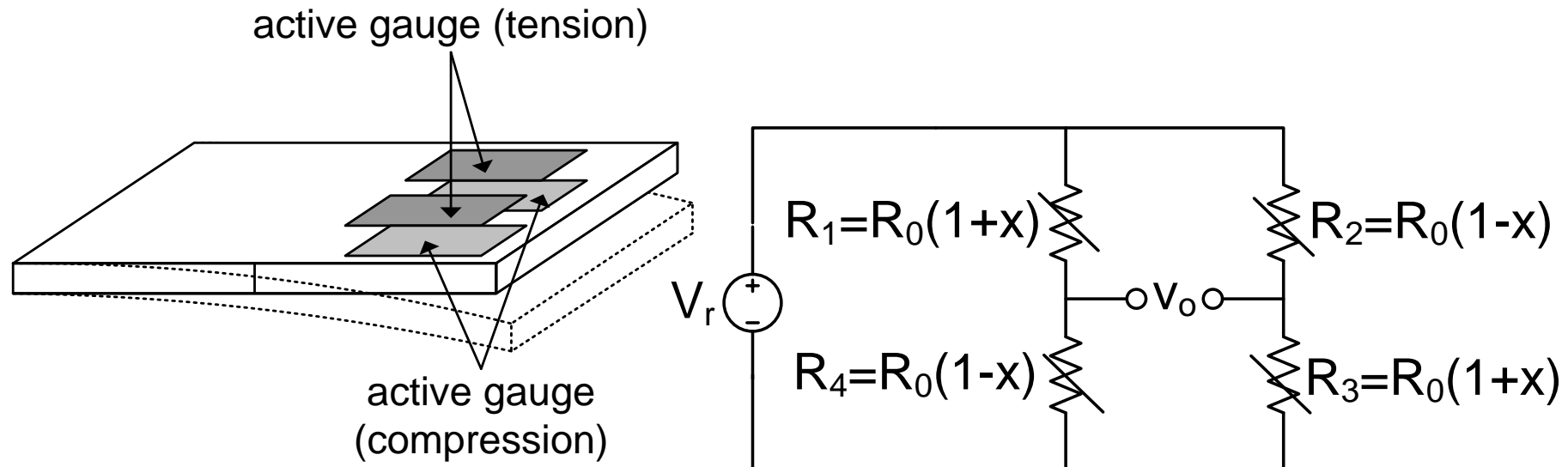
$$= \left( \frac{1-x}{2} - \frac{1+x}{2} \right) V_r = \frac{-2x}{2} V_r = -xV_r$$





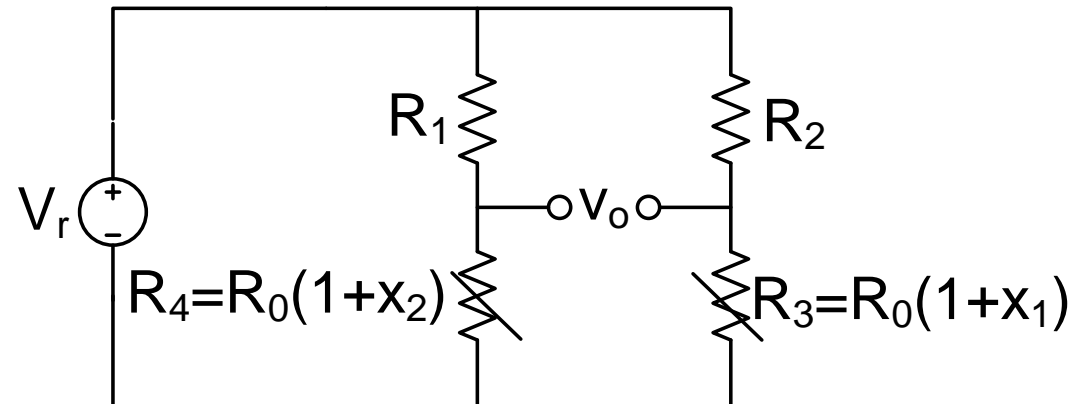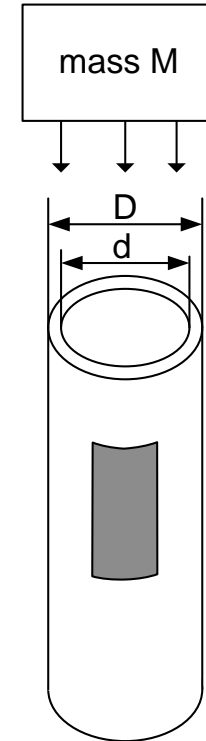
## Example – electronic two armed balance

- solution: place to two load cells in bridge circuit
- specification
  - $D = 50.0 \text{ mm}$ ,  $d = 47.5 \text{ mm}$
  - $E = 73.0 \text{ GPa} = 73.0 \cdot 10^9 \text{ Pa}$
  - $G = 2.1$ ,  $R_0 = 350 \ \Omega$
  - $R_1 = R_2 = 350 \ \Omega$
  - $V_r = 10 \text{ V}$
- **what is the output voltage  $v_o$  when load of 1000 kg is placed on  $R_4$  and a load of 2000 kg on  $R_3$ ?**



- step 1: compute output voltage of bridge circuit

$$\begin{aligned}
 v_o &= \left( \frac{R_4}{R_1 + R_4} - \frac{R_3}{R_2 + R_3} \right) V_r = \left( \frac{R_0(1+x_2)}{R_0 + R_0(1+x_2)} - \frac{R_0(1+x_1)}{R_0 + R_0(1+x_1)} \right) V_r \\
 &= \left( \frac{1+x_2}{2+x_2} - \frac{1+x_1}{2+x_1} \right) V_r = \left( \frac{(1+x_2)(2+x_1)}{(2+x_1)(2+x_2)} - \frac{(1+x_1)(2+x_2)}{(2+x_1)(2+x_2)} \right) V_r \\
 &= \frac{x_2 - x_1}{(2+x_1)(2+x_2)} V_r
 \end{aligned}$$

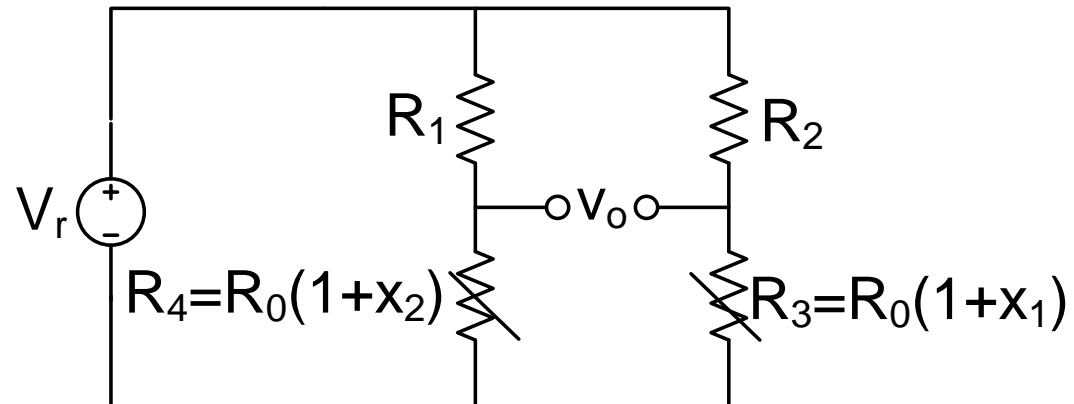

- step 2: compute change in resistance due to load of 1000 kg

$$dR = RG\varepsilon = RG \frac{dl}{l} = RG \frac{F}{AE}$$


- area on which load is applied

$$A = \frac{\pi(D^2 - d^2)}{4} = \frac{\pi((50.0\text{mm})^2 - (47.5\text{mm})^2)}{4} = 191.4\text{mm}^2$$

- change in resistance

$$dR = 350\Omega \cdot 2.1 \cdot \frac{9800\text{N}}{(191.4 \cdot 10^{-6}\text{m}^2)(73.0 \cdot 10^9\text{Pa})} = 0.5\Omega$$
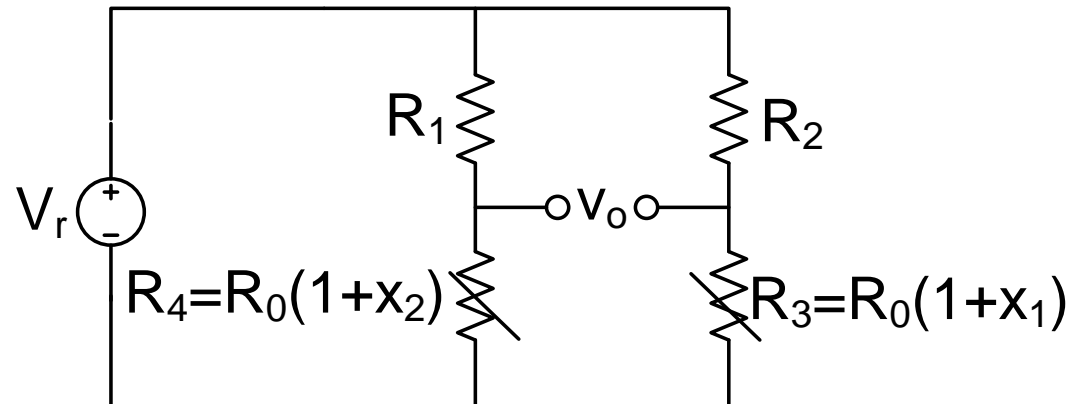
$$dR = \frac{0.5\Omega}{350\Omega} \cdot 100\% \approx 0.15\%$$




- step 3: compute change in  $x_2$  due to load of 1000 kg

$$R_4 = R_0(1 + x_2) \Rightarrow 350.5\Omega = 350\Omega(1 + x_2)$$

$$\Leftrightarrow x_2 = 0.0014$$

- step 4: compute change in  $x_1$  due to load of 2000 kg
  - relation between change in R and weight is linear

$$\Rightarrow x_1 = 2x_2$$

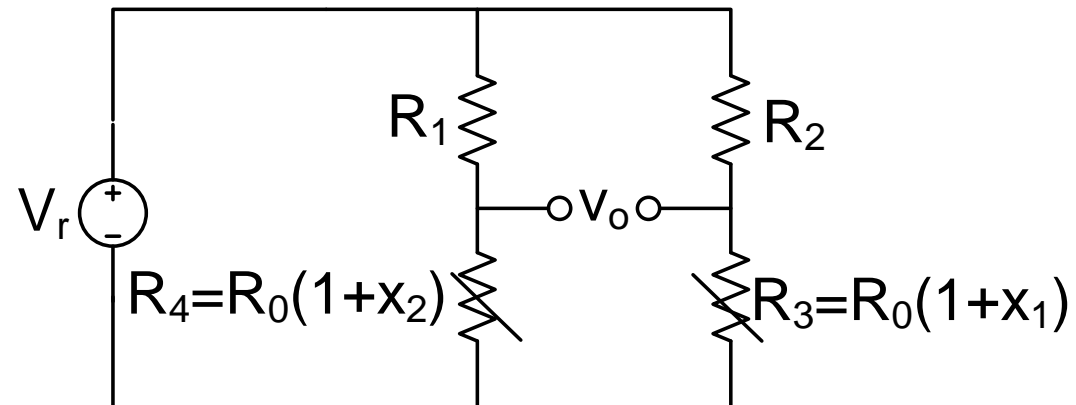

- step 5: compute output voltage of circuit for given loads


$$v_o = \frac{x_2 - x_1}{(2 + x_1)(2 + x_2)} V_r = \frac{x_2 - 2x_2}{(2 + 2x_2)(2 + x_2)} V_r = \frac{-x_2}{(2 + 2x_2)(2 + x_2)} V_r$$

- when ignoring non-linearity (assume  $x_2 \ll 2$ )

$$v_o \approx \frac{-x_2}{4} V_r = \frac{-0.0014}{4} 10V = -3.5mV$$

- taking non-linearity into account

$$v_o = -3.5mV$$

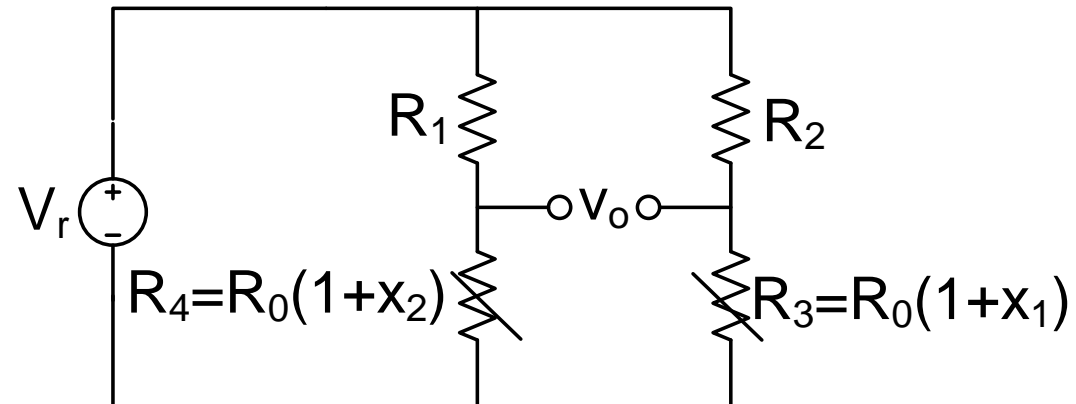




# ERROR SOURCES

(Chapter 4.8)

- resistance of a wire

$$R = \rho \frac{l}{a} = \frac{m}{ne^2\tau} \frac{l}{a}$$

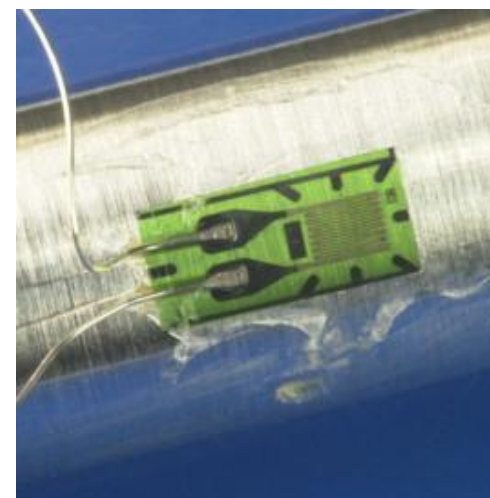- changing **temperature** affects resistance (**thermoresistive effect**)
- changing **dimensions** affects resistance (**piezoresistive effect**)
  
- **strain gauges** use piezoresistive effect to sense mechanical stress
- sensor based on strain gauges convert mechanical energy to electrical energy
  
- thermoresistive effect is an error source





- strain gauge in bridge circuit
- stress applied to active gauge (resistive change 'x')
- temperature change applied to strain gauge (resistive change 'y')
- **what is the output voltage  $v_o$ ? (assume  $k = R_1/R_4 = R_2/R_0 = 1$ )**

$$v_o = \left( \frac{R_4}{R_1 + R_4} - \frac{R_3}{R_2 + R_3} \right) V_r = \left( \frac{R_0}{2R_0} - \frac{R_0(1+x+y)}{R_0 + R_0(1+x+y)} \right) V_r = \left( \frac{1}{2} - \frac{1+x+y}{2+x+y} \right) V_r$$

$$= \frac{-x-y}{4+2x+2y} V_r \approx \frac{-x-y}{4} V_r$$

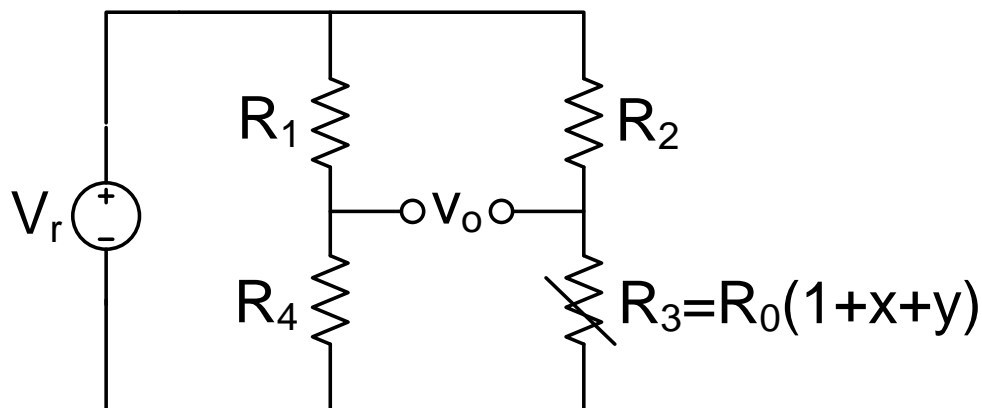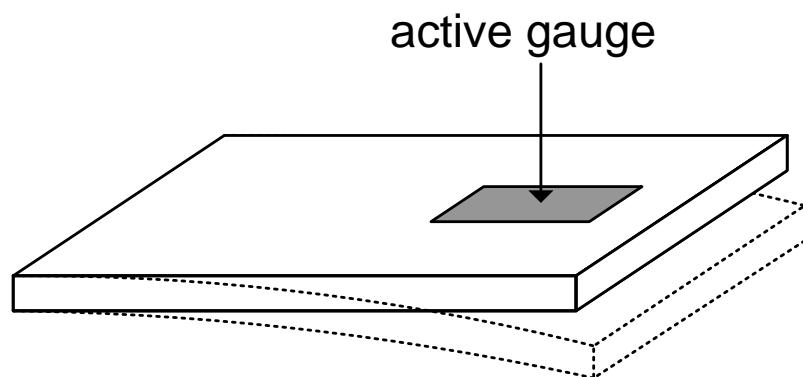- change in temperature leads to **temperature error**





- add **passive strain gauge** (only 'y' applied)
- stress applied to active gauge (resistive change 'x')
- temperature change applied to strain gauge (resistive change 'y')
- **what is the output voltage  $v_o$ ? (assume  $k = R_1/R_4 = 1$ )**



$$v_o = \left( \frac{R_4}{R_1 + R_4} - \frac{R_3}{R_2 + R_3} \right) V_r = \left( \frac{R_0}{2R_0} - \frac{R_0(1+x+y)}{R_0(1+y) + R_0(1+x+y)} \right) V_r = \left( \frac{1}{2} - \frac{1+x+y}{2+x+2y} \right) V_r$$

$$= \frac{-x}{4+2x+4y} V_r \approx \frac{-x}{4} V_r$$

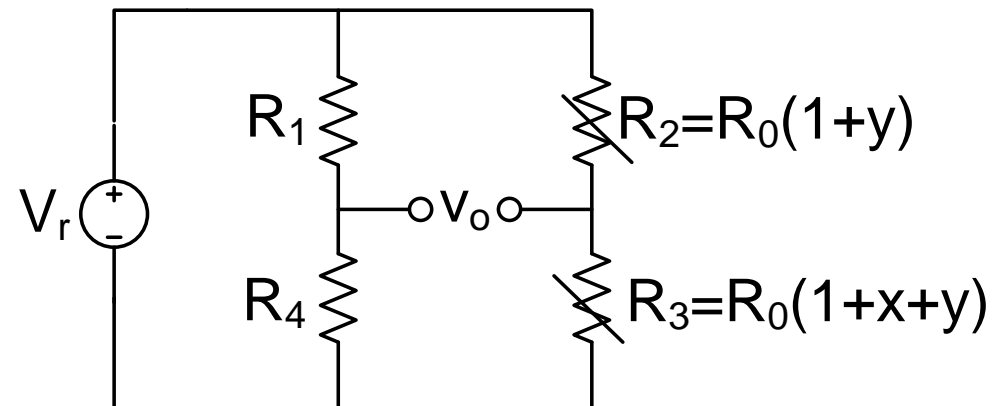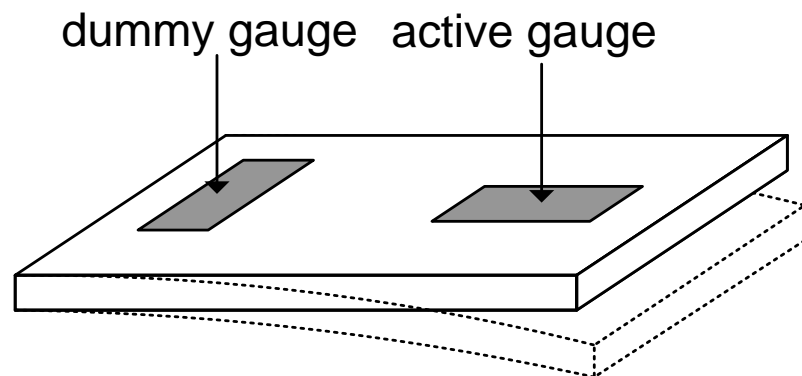
- **dummy gauge removes temperature error**



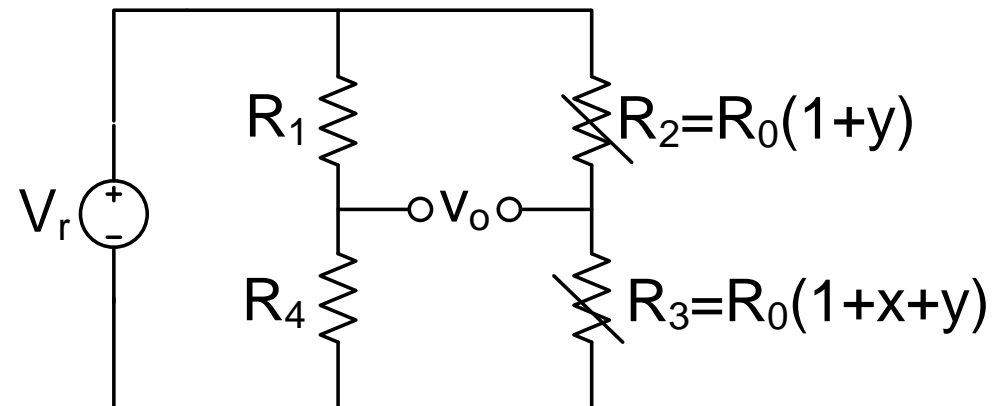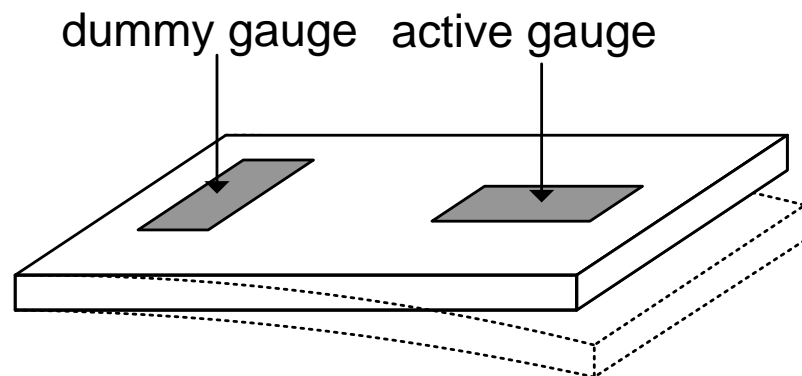- error sources (discussed)
  - non-linearity in strain gauge
  - non-linearity due to interface circuit
  - temperature dependency
  
- additional error sources
  - lead-wire resistance
  - loading effect





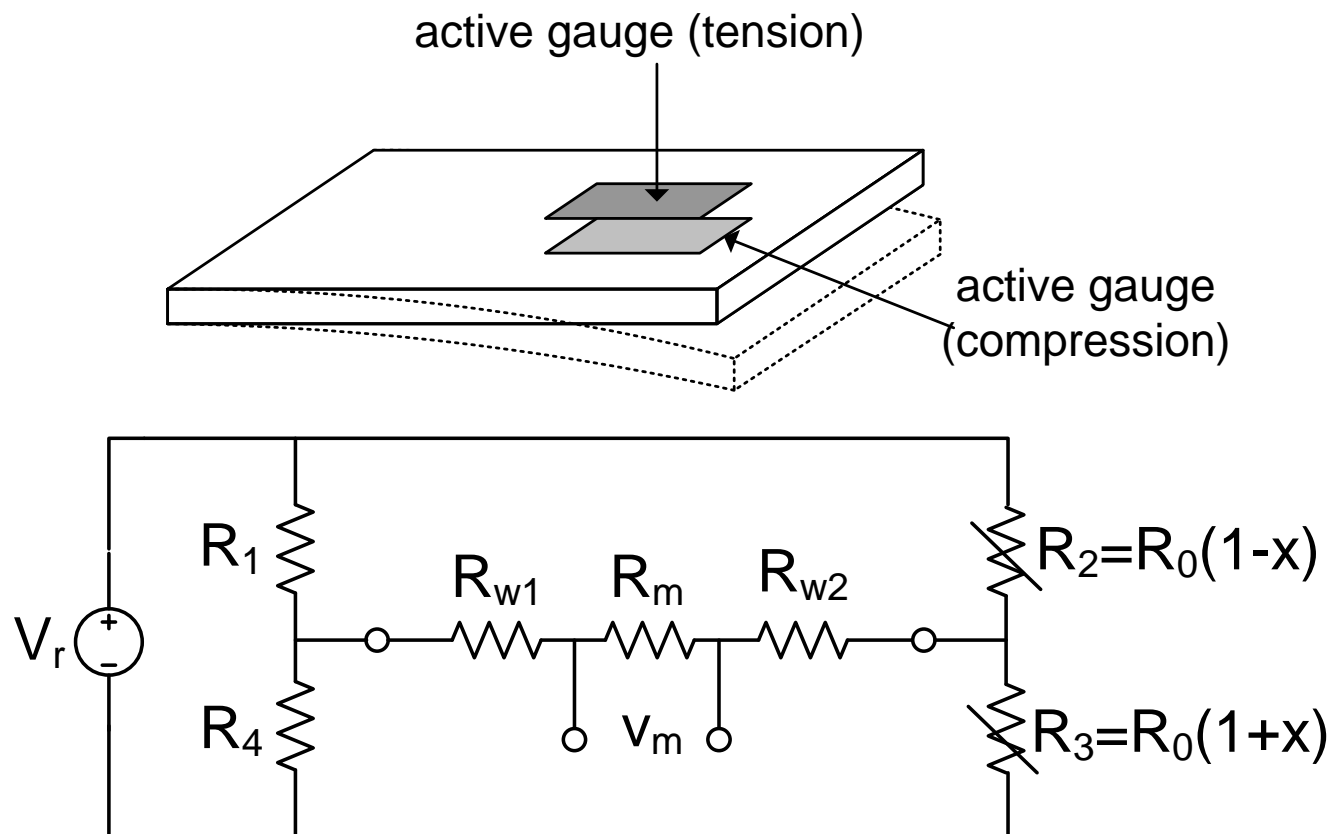- sensor circuit (bridge) connected to
  - measurement device (with resistance  $R_m$ )
  - using two wires (with resistance  $R_{w1}$  and  $R_{w2}$ )
- **what is the measured voltage  $v_m$ ? (assume  $k = R_1/R_4 = 1$ )**



- what is the measured voltage  $v_m$ ? (assume  $k = R_1/R_4 = 1$ )
- step 1: Thevenin equivalent circuit (of bridge)
  - open circuit voltage



$$v_o = \frac{-x}{2} V_r$$

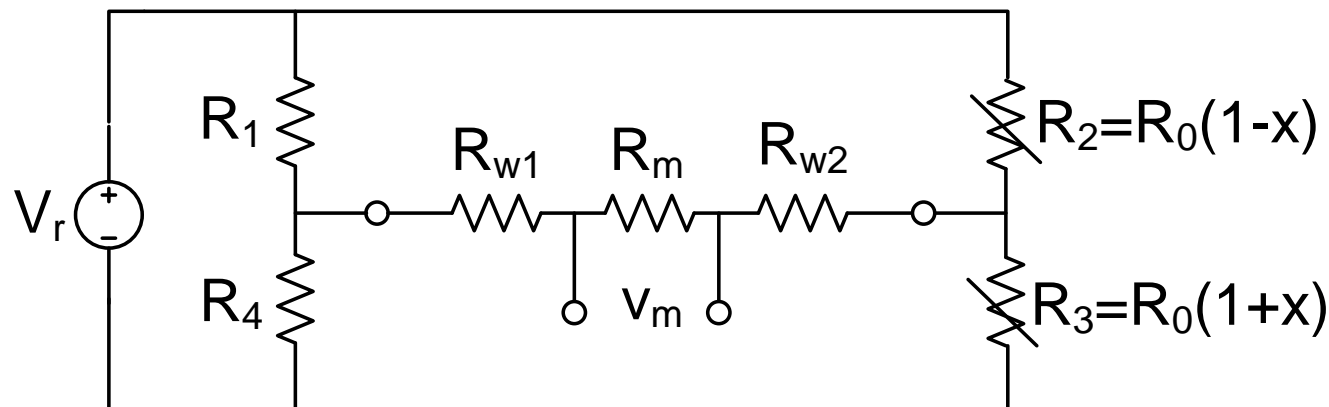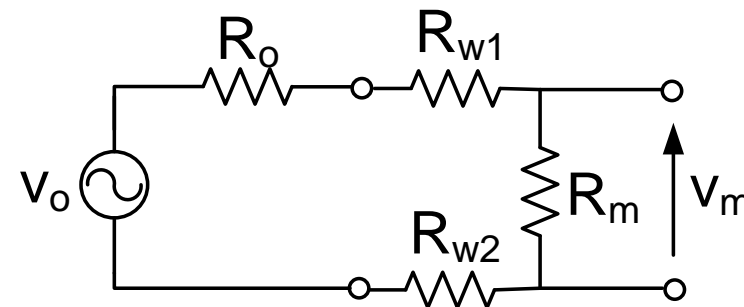

- what is the measured voltage  $v_m$ ? (assume  $k = R_1/R_4 = 1$ )
- step 1: Thevenin equivalent circuit (of bridge)
  - open circuit voltage

$$v_o = \frac{-x}{2} V_r$$

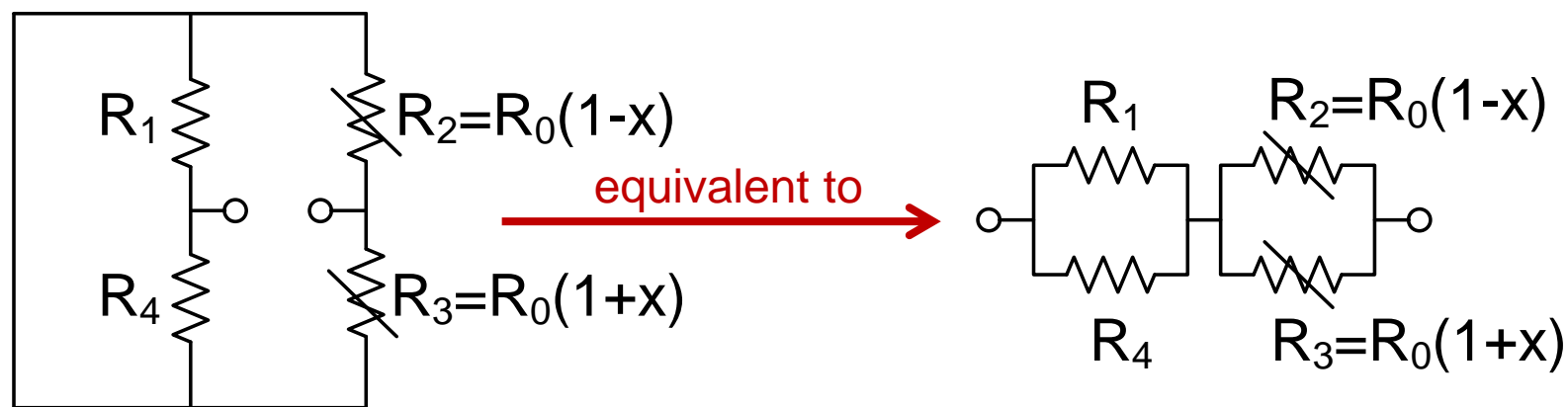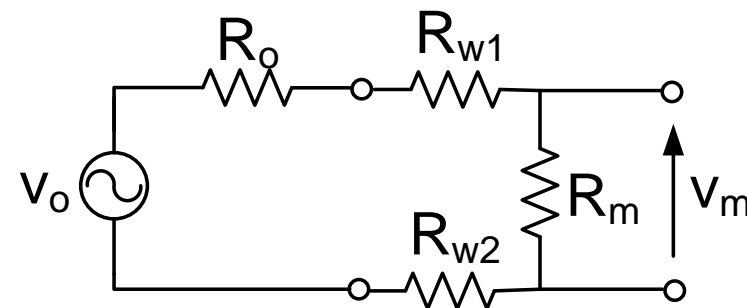- output resistance (assume  $V_r$  short circuit)



$$R_o = \frac{R_1 R_4}{R_1 + R_4} + \frac{R_2 R_3}{R_2 + R_3} = \frac{R_0}{2} + \frac{R_0(1-x^2)}{2} = \frac{R_0}{2} (2 - x^2)$$



- what is the measured voltage  $v_m$ ? (assume  $k = R_1/R_4 = 1$ )
- step 2: output voltage of resistor divider


$$v_m = \frac{R_m}{R_o + R_{w1} + R_m + R_{w2}} v_o$$

$$= \frac{R_m}{\frac{R_o}{2}(2 - x^2) + R_{w1} + R_m + R_{w2}} \frac{-x}{2} V_r$$

$$= \frac{-xR_m}{R_o(2 - x^2) + 2R_{w1} + 2R_m + 2R_{w2}} V_r$$


non-linearity

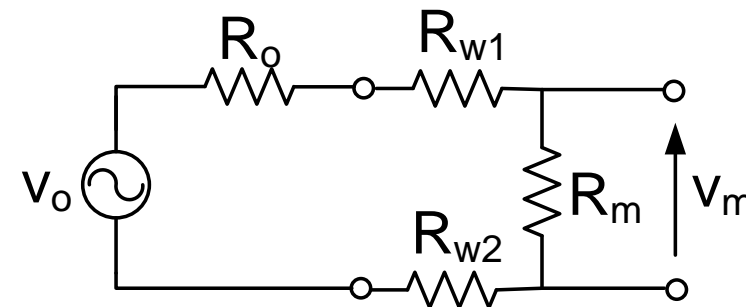- two errors in measured voltage
  - non-linearity
  - reduced sensitivity



reduced sensitivity

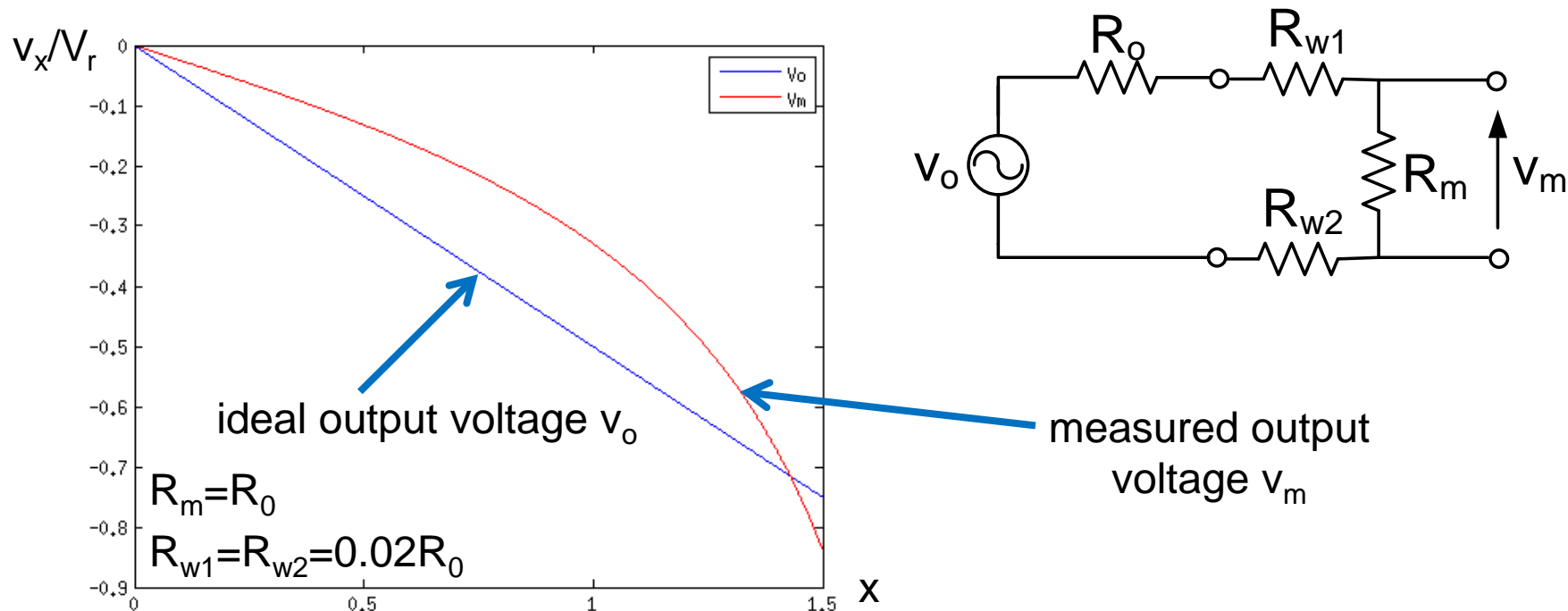- what is the measured voltage  $v_m$ ? (assume  $k = R_1/R_4 = 1$ )




- two errors in measured voltage
  - non-linearity
  - reduced sensitivity
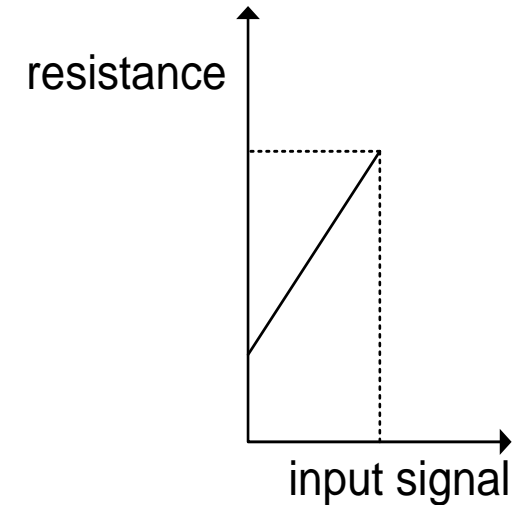
# SUMMARY

(on all resistive sensors and interface circuits seen so far)


- resistance of resistive sensor  $R = R_0 f(x)$ 
  - $f(x)$  – fractional change in resistance (with  $f(0) = 1$ )
- resistance of linear resistive sensor  $R = R_0(1 + x)$ 
  - range of  $x$  depends on type of sensor
    - $[-1, 0]$  – linear potentiometer
    - $[1, 10]$  – RTDs
    - $[0.00001, 0.002]$  – strain gauges
- requirements on signal conditioners for resistive sensors
  - electric **voltage** or **current** must be applied
    - supply and output voltage/current are limited by error sources
    - several error sources need to be considered when using sensor





- error sources
  - inherent non-linearity in sensor
  - resistance depends on temperature and strain

$$R = \rho \frac{l}{a} = \frac{m}{ne^2 \tau} \frac{l}{a}$$

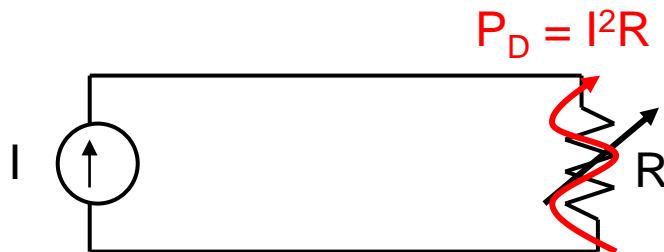- strain or temperature is signal
- other is error source
- self-heating effect
  - current passed through sensor causes heat production


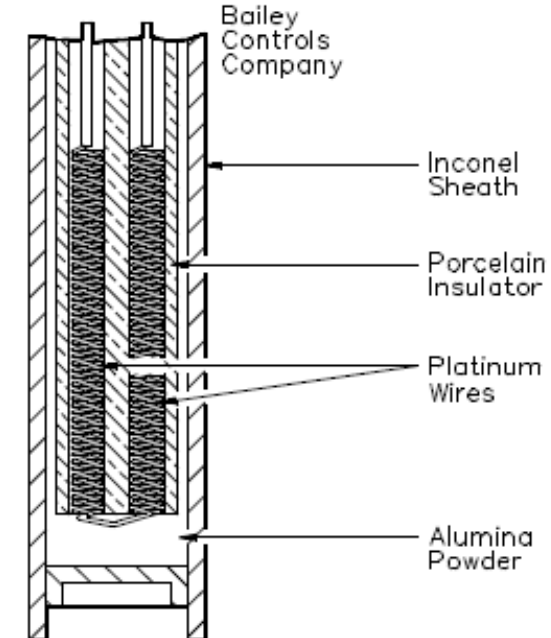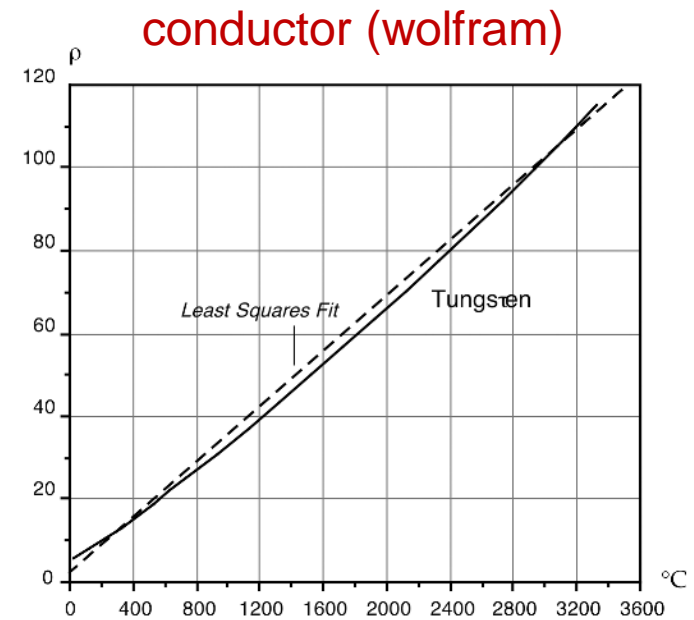
$$\Delta T = \frac{P_D}{\delta} = \frac{I^2 R}{\delta}$$



- error sources
  - loading effect ( $R_1=R_0$ )

$$v_o = \frac{1+x}{2+x} V_r \approx \frac{1}{2} V_r + \frac{x}{2} V_r$$

- measurement adds load  $R_m$
- measured voltage  $v_m$
- (use Thévenin circuit,  $R_o, v_o$ )

$$v_m = \frac{R_m}{R_m + R_o} v_o$$



with

$$R_o = R_1 // R_2 = \frac{R_0 R_0 (1+x)}{R_0 + R_0 (1+x)}$$

$$\Rightarrow v_m = \frac{R_m}{R_m + \frac{R_0(1+x)}{2+x}} v_o = \frac{(2+x)R_m}{(2+x)R_m + R_0(1+x)} v_o$$

$$k = R_m/R_0$$
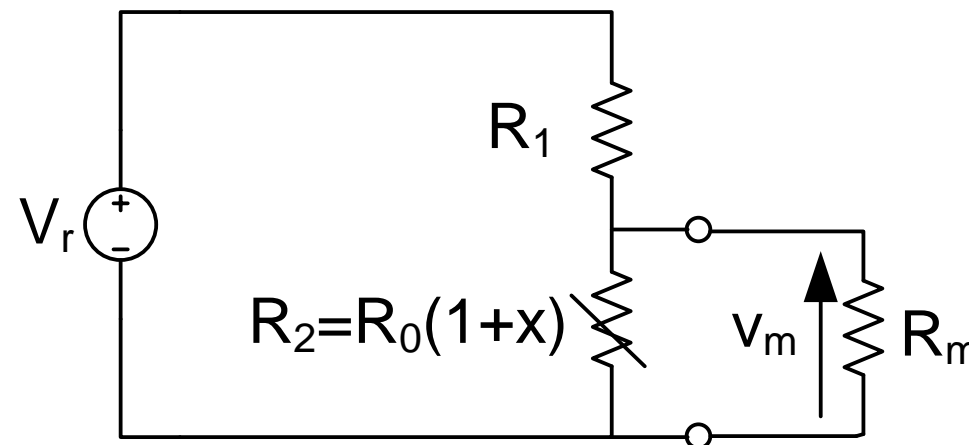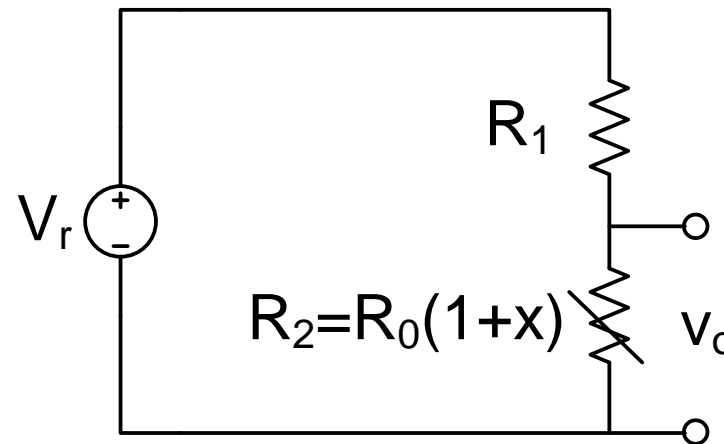
$$\left. \vphantom{\frac{(2+x)R_m}{(2+x)R_m + R_0(1+x)}}} \right\} \Rightarrow v_m = \frac{(2+x)}{(2+x) + \frac{(1+x)}{k}} v_o$$




- error sources
  - loading effect ( $R_1=R_0$ )





$$\varepsilon = \frac{v_m - v_o}{v_o} = \frac{\frac{(2+x)k}{(2+x)k + (1+x)} v_o - v_o}{v_o} = \frac{(2+x)k - (2+x)k - (1+x)}{(2+x)k + (1+x)} = \frac{-(1+x)}{(2+x)k + (1+x)}$$

absolute error

relative error

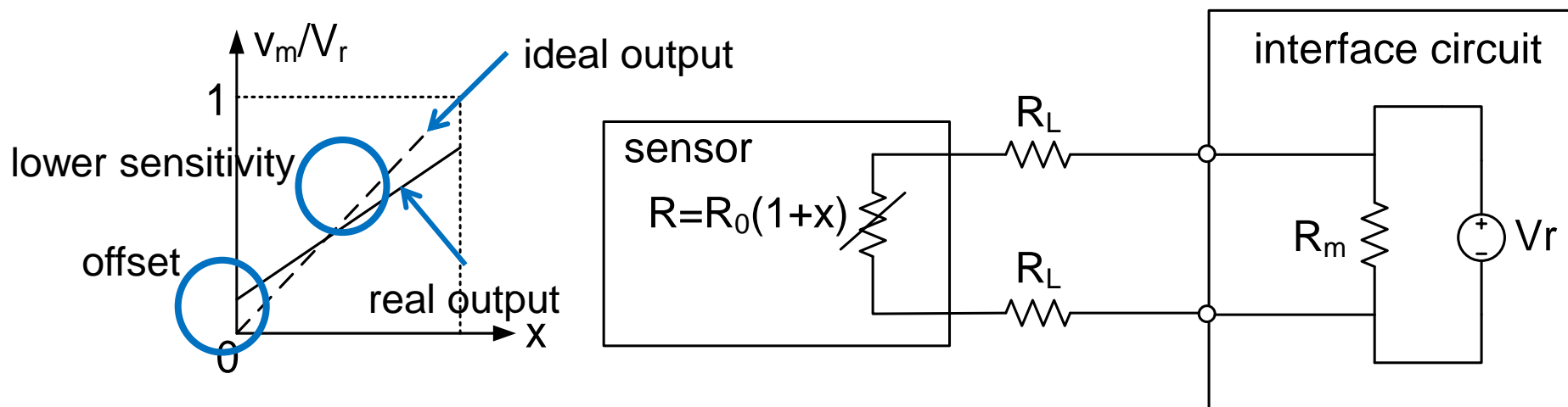- larger  $k$  means smaller error (closer to open circuit)
- lead-wire resistance



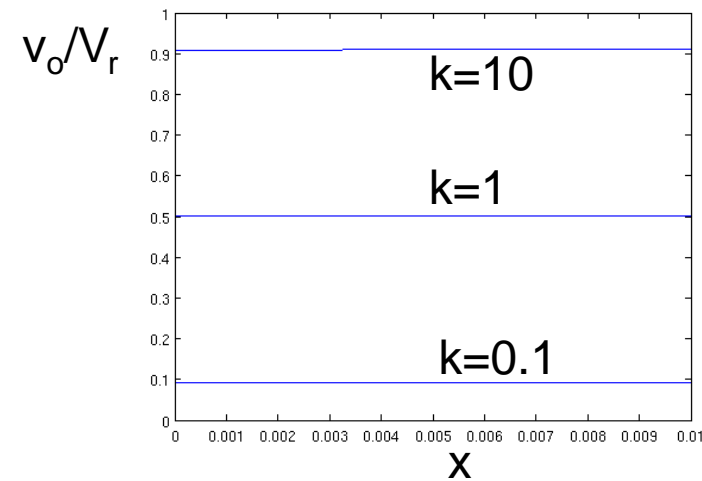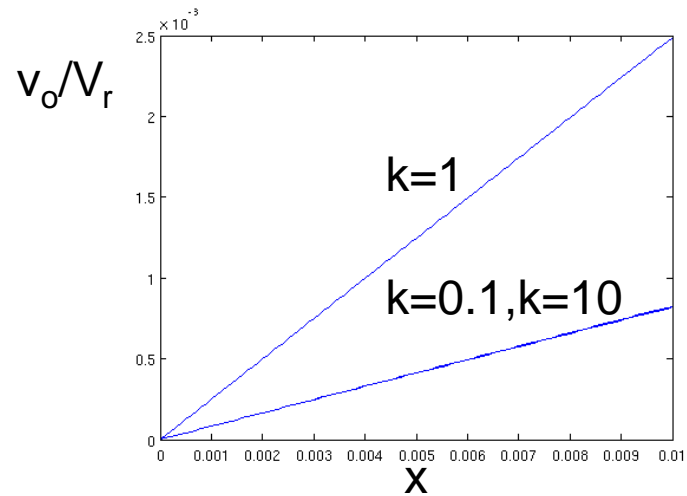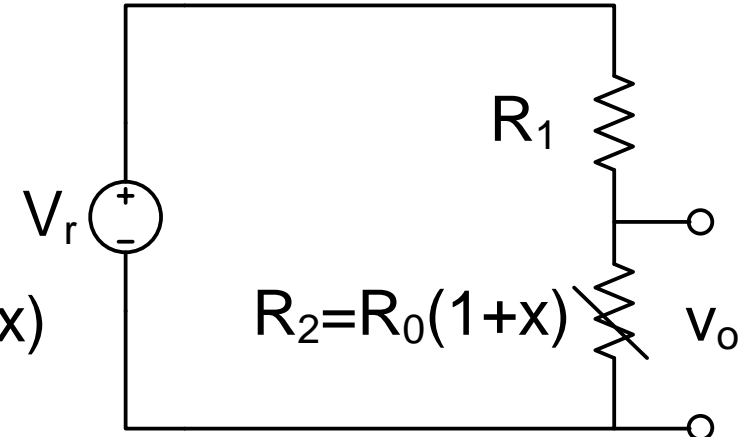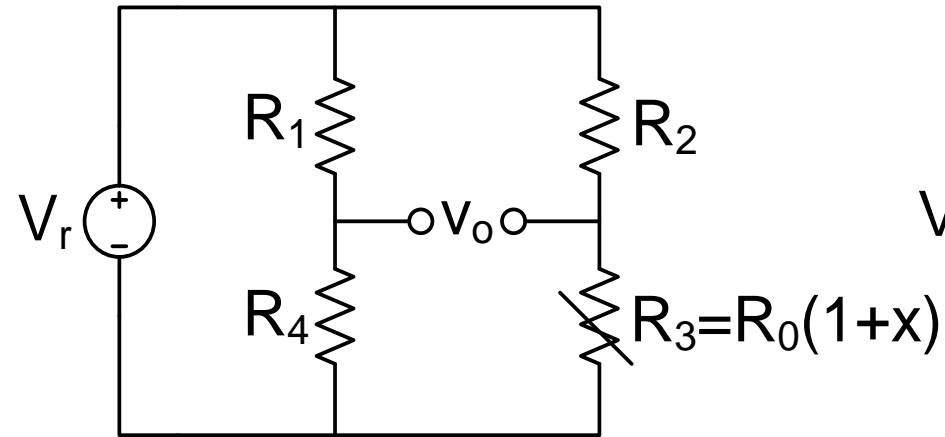

- sensitivity is equal, but DC offset makes response look “flat”