




Sensing, Computing, Actuating

Sander Stuijk (s.stuijk@tue.nl)

AMPLIFIERS

(Chapter 2.4)

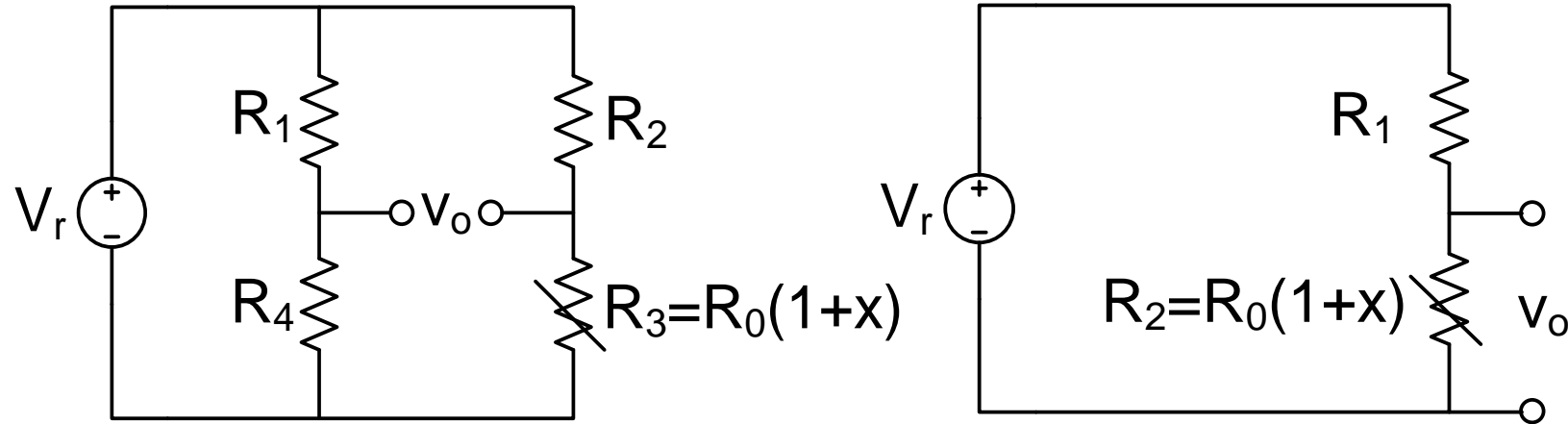

- output voltage ($k=1$)

$$v_o = \frac{x}{4 + 2x} V_r \approx \frac{x}{4} V_r$$

$$v_o = \frac{1 + x}{2 + x} V_r \approx \frac{1}{2} V_r + \frac{x}{2} V_r$$



- response of bridge output to change in x only half of response when using divider
- **can we change the bridge to get the same response?**
 - use an additional sensor
 - use operational amplifier (also amplifies non-linearity error)

- **increase sensitivity** by adding amplifier to output of bridge
- adjust voltage for digitization
- amplifier with gain G


$$v_{out} = G \cdot v_{in}$$

- circuit output voltage
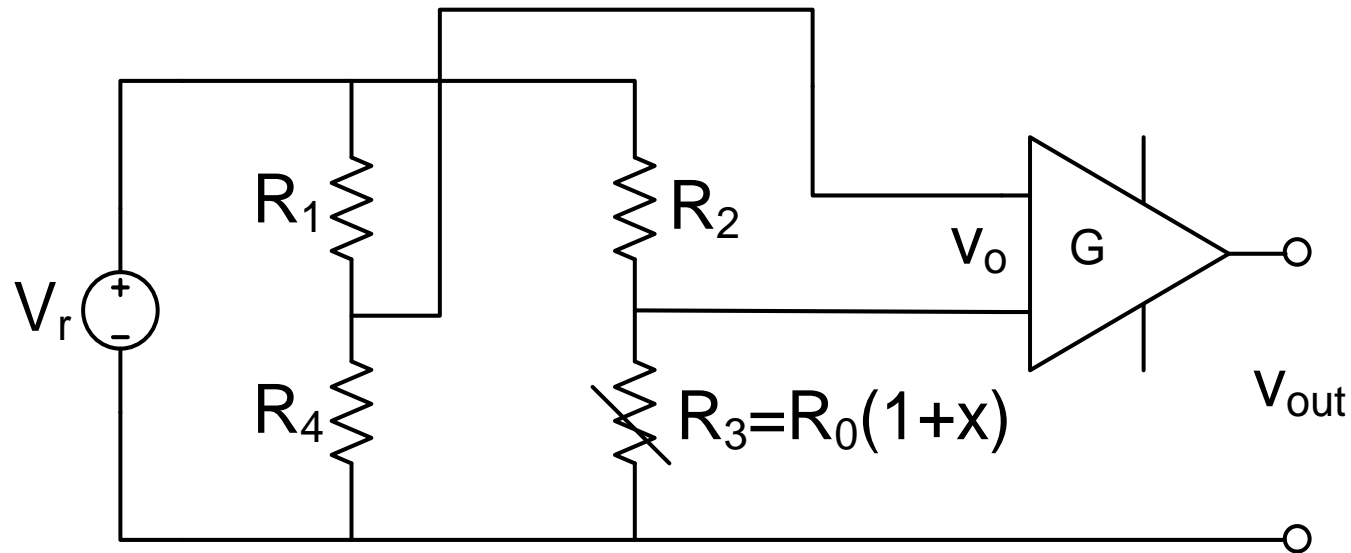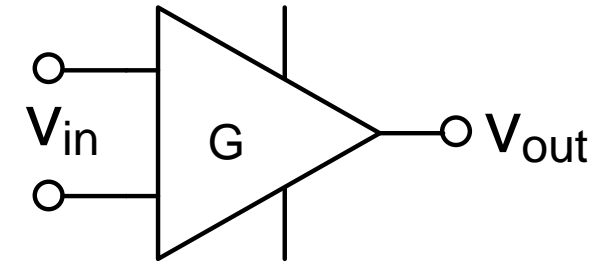
$$v_{out} = G \cdot v_o = G \cdot \frac{x}{4 + 2x} V_r \approx G \cdot \frac{x}{4} V_r$$



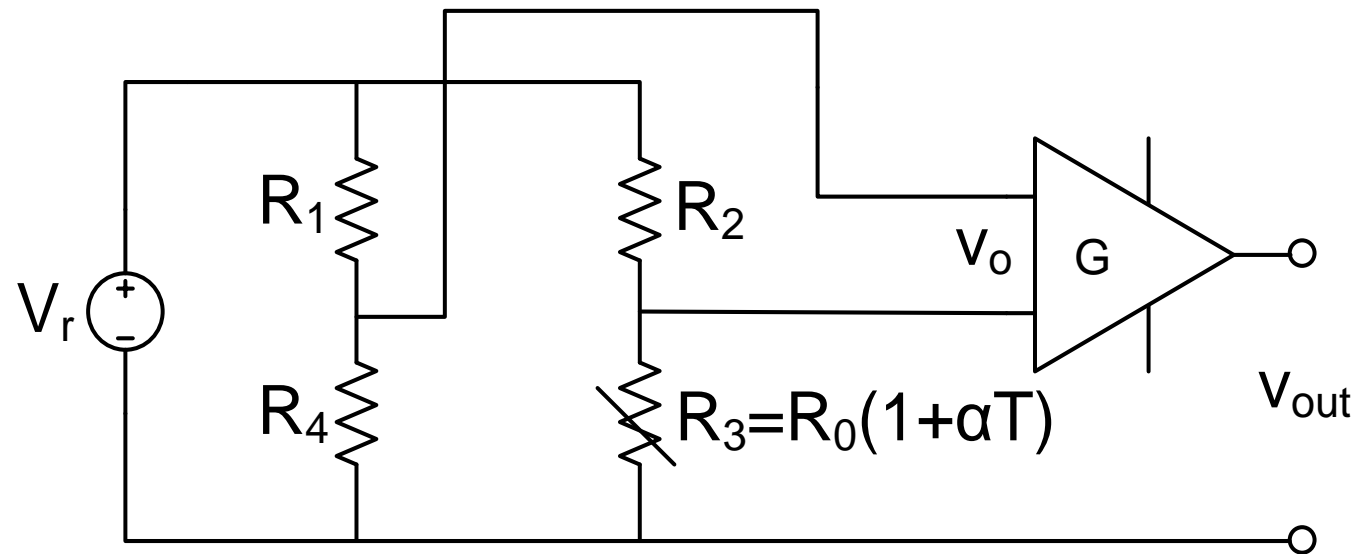- example – PT100 temperature sensor
- PT100 ($R_0=100\Omega$ and $\alpha=0.004\Omega/\Omega/K$ at 0°C)
- measure temp from -10°C to $+50^\circ\text{C}$ in environment with $\delta=5\text{mW/K}$
- output must range from -1V to $+5\text{V}$ with error $< 0.5\%$ of the reading (due to non-linearity) plus 0.2% FSO (due to self-heating)
- **what values should be used for the resistors and voltage supply, and what gain must the amplifier have?**



- example – PT100 temperature sensor
- PT100 ($R_0=100\Omega$ and $\alpha=0.004\Omega/\Omega/K$ at 0°C)
- measure temp from -10°C to $+50^\circ\text{C}$ in environment with $\delta=5\text{mW/K}$
- output must range from -1V to $+5\text{V}$ with error $< 0.5\%$ of the reading (due to non-linearity) plus 0.2% FSO (due to self-heating)
- **what values should be used for the resistors and voltage supply, and what gain must the amplifier have?**

$$v_o = \frac{k\alpha T}{(k+1)(k+1+\alpha T)} V_r$$

- assume $\alpha T \ll k+1$, the response is then equal to

$$v_i = \frac{k\alpha T}{(k+1)^2} V_r$$

- introduces an error (due to non-linearity); requirements is relative to reading, thus look at relative error; gain plays no role since its both v_o and v_i are multiplied with same gain G

$$\varepsilon = \left| \frac{v_o - v_i}{v_i} \right| = \left| \frac{-\alpha T}{k+1+\alpha T} \right|$$

- example – PT100 temperature sensor
- PT100 ($R_0=100\Omega$ and $\alpha=0.004\Omega/\Omega/K$ at 0°C)
- measure temp from -10°C to $+50^\circ\text{C}$ in environment with $\delta=5\text{mW/K}$
- output must range from -1V to $+5\text{V}$ with error $< 0.5\%$ of the reading (due to non-linearity) plus 0.2% FSO (due to self-heating)
- **what values should be used for the resistors and voltage supply, and what gain must the amplifier have?**
- maximal error when $T=50^\circ\text{C}$

$$\varepsilon = \left| \frac{-(0.004/^\circ\text{C})(50^\circ\text{C})}{k + 1 + (0.004/^\circ\text{C})(50^\circ\text{C})} \right| < 0.005$$

- this requires $k > 39$
- R_4 must be $R_3=R_0=100\Omega$ to get 0V at 0°C

$$k = \frac{R_1}{R_4} = \frac{R_2}{R_3}$$

- $R_4 = 100\Omega$ and $R_1=R_2=3900\Omega$
 - larger values of R_1 and R_2 would decrease sensitivity!

- example – PT100 temperature sensor
- PT100 ($R_0=100\Omega$ and $\alpha=0.004\Omega/\Omega/K$ at 0°C)
- measure temp from -10°C to $+50^\circ\text{C}$ in environment with $\delta=5\text{mW/K}$
- output must range from -1V to $+5\text{V}$ with error $< 0.5\%$ of the reading (due to non-linearity) plus 0.2% FSO (due to self-heating)
- **what values should be used for the resistors and voltage supply, and what gain must the amplifier have?**
- supply voltage limited by sensor self-heating

$$\Delta T = \frac{P_D}{\delta} \Rightarrow P_D = \left(\frac{V_r}{R_2 + R_3} \right)^2 R_3 < (0.002 \cdot 50^\circ\text{C}) \cdot (5\text{mW}/^\circ\text{C}) = 0.5\text{mW}$$

- maximal self-heating when $R_2=R_3$
- R_3 will however always be below R_2 in measurement range
 - maximal heating occurs at 50°C
 - $R(50^\circ\text{C}) = 120\Omega$

$$V_r < \sqrt{\frac{0.0005\text{W}}{120\Omega}} \cdot (3900\Omega + 120\Omega) = 8.2\text{V}$$

- example – PT100 temperature sensor
- PT100 ($R_0=100\Omega$ and $\alpha=0.004\Omega/\Omega/K$ at 0°C)
- measure temp from -10°C to $+50^\circ\text{C}$ in environment with $\delta=5\text{mW/K}$
- output must range from -1V to $+5\text{V}$ with error $< 0.5\%$ of the reading (due to non-linearity) plus 0.2% FSO (due to self-heating)
- **what values should be used for the resistors and voltage supply, and what gain must the amplifier have?**

$$V_r < \sqrt{\frac{0.0005\text{W}}{120\Omega}} \cdot (3900\Omega + 120\Omega) = 8.2\text{V}$$


- choose $V_r = 8\text{V}$
- output of bridge at 50°C

$$v_o = \frac{k\alpha T}{(k+1)(k+1+\alpha T)} V_r \approx \frac{39 \cdot 0.004/^\circ\text{C} \cdot 50^\circ\text{C}}{40^2} \cdot 8 = 39\text{mV}$$


- gain needed to get $+5\text{V}$ output at 50°C

$$G = \frac{5\text{V}}{39\text{mV}} = 128.2$$

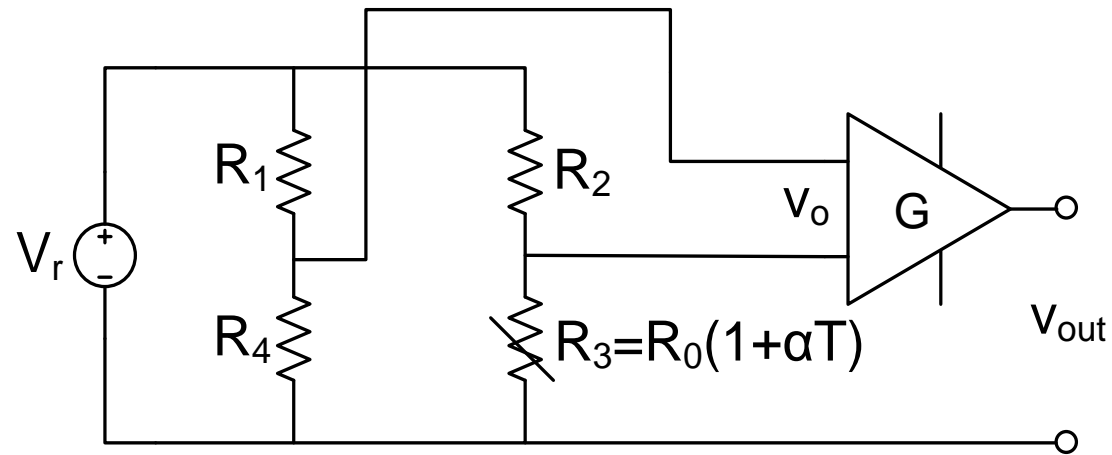- output of voltage divider or bridge may be very small




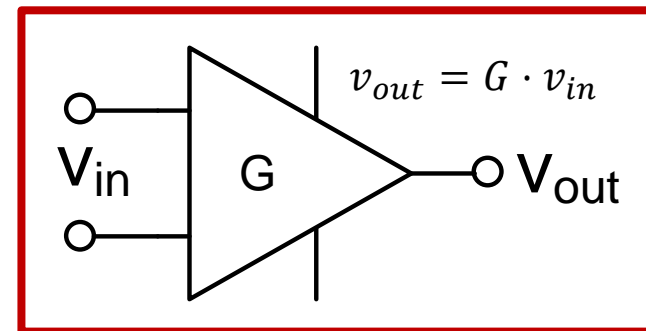- (digital) processing circuits require higher voltage (0-5V)
- two types of amplifiers considered
 - differential amplifiers
 - instrumentation amplifiers




- inverting amplifier
 - amplifier draws no current
 - current through R_1 and R_2 are equal
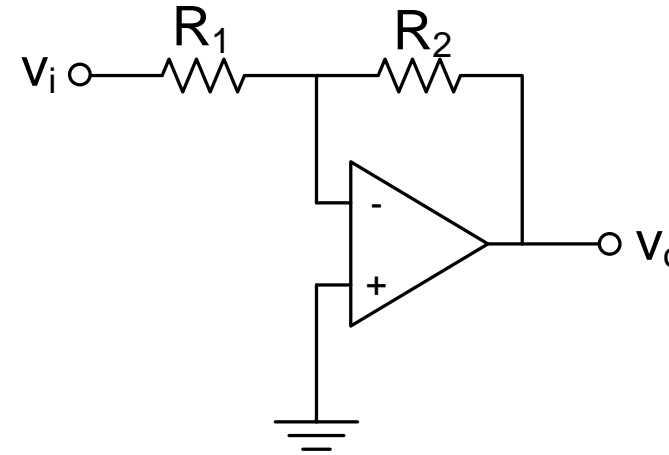
$$\left. \begin{array}{l} \frac{v_i - v_-}{R_1} = \frac{v_- - v_o}{R_2} \\ v_- = v_+ = 0 \end{array} \right\} \Rightarrow v_o = -\frac{R_2}{R_1} v_i$$



- non-inverting amplifier
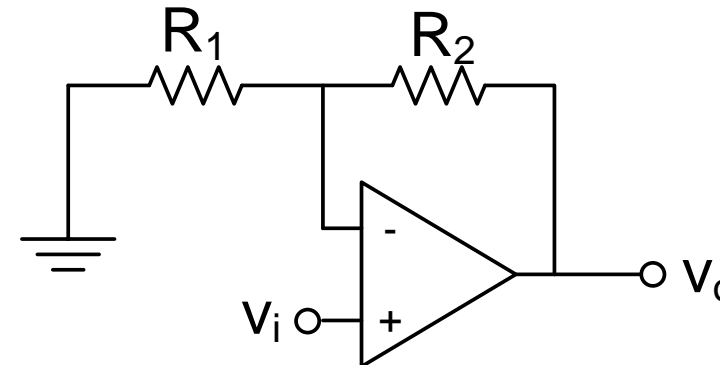
$$\left. \begin{array}{l} \frac{-v_-}{R_1} = \frac{v_- - v_o}{R_2} \\ v_- = v_+ = v_i \end{array} \right\} \Rightarrow v_o = \left(1 + \frac{R_2}{R_1}\right) v_i$$



- these circuits cannot be used in bridge since they have only **one input terminal** and bridge has **two output terminals**

- assumptions about op-amp
 - negligible common mode gain ($A_c=0$)
 - considerable differential gain ($A_d \neq 0$)
- output voltage


$$v_o = \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_2}{R_1} \right) v_2 - \frac{R_2}{R_1} v_1$$

- inputs v_1 and v_2 have **differential** and **common** part

$$v_d = v_2 - v_1, \quad v_c = \frac{v_1 + v_2}{2}$$

- output voltage
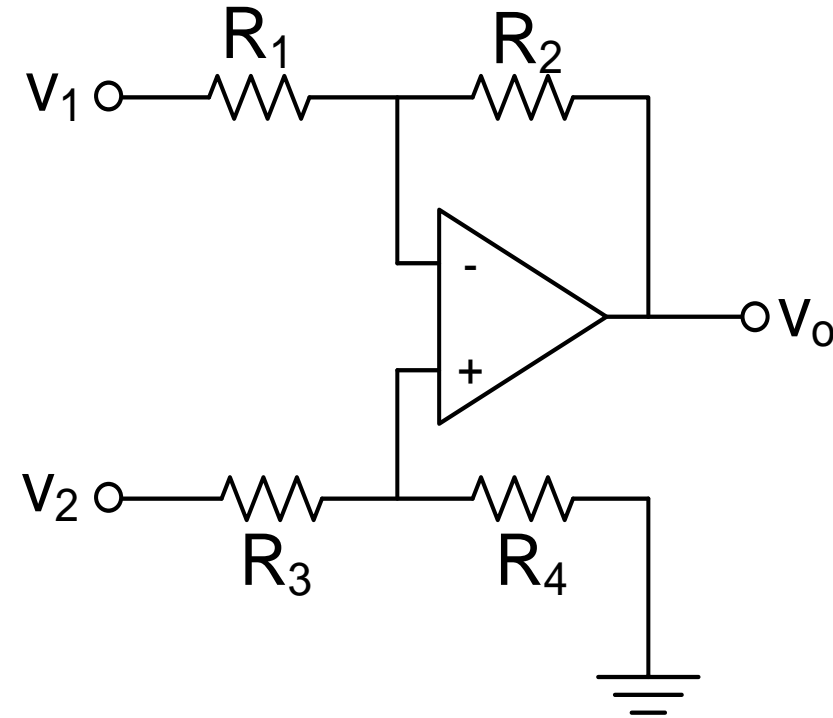
$$v_o = \frac{1}{2} v_d \left[\frac{R_4}{R_3 + R_4} \left(1 + \frac{R_2}{R_1} \right) + \frac{R_2}{R_1} \right] + v_c \left[\frac{R_4 R_1 - R_2 R_3}{R_1 (R_3 + R_4)} \right]$$



- differential mode gain

$$G_d = \left. \frac{v_o}{v_d} \right|_{v_c=0} = \frac{1}{2} \left[\frac{R_4}{R_3 + R_4} \left(1 + \frac{R_2}{R_1} \right) + \frac{R_2}{R_1} \right]$$

- common mode gain

$$G_c = \left. \frac{v_o}{v_c} \right|_{v_d=0} = \frac{R_4 R_1 - R_2 R_3}{R_1 (R_3 + R_4)}$$


- ideal differential amplifier has $G_c=0$

$$\frac{R_4}{R_3} = \frac{R_2}{R_1} = k$$

- differential gain of an ideal differential amplifier

$$G_d = \left. \frac{v_o}{v_d} \right|_{v_c=0} = \frac{1}{2} \left[\frac{k}{1+k} (1+k) + k \right] = \frac{1}{2} \left[\frac{k(1+k) + k(1+k)}{1+k} \right] = \frac{2k(1+k)}{2(1+k)} = k$$

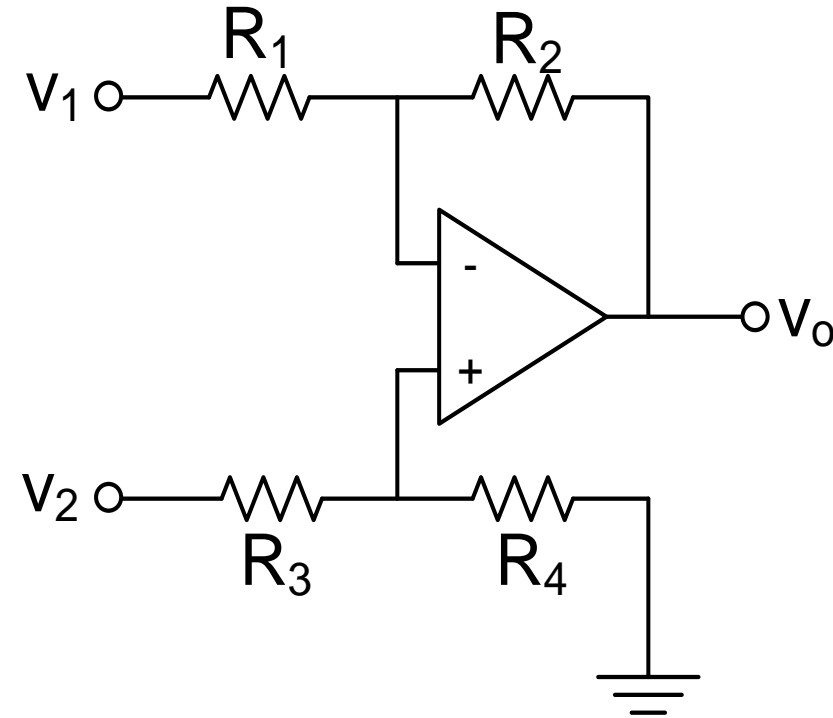- differential gain G_d depends on ratio k of resistors




- matching condition is hard to realize

$$\frac{R_4}{R_3} = \frac{R_2}{R_1} = k$$


- common mode rejection ratio (CMRR)

$$CMRR_R = \frac{G_d}{G_c} = \frac{1}{2} \frac{R_1 R_4 + R_2 R_3 + 2R_2 R_4}{R_1 R_4 - R_2 R_3}$$

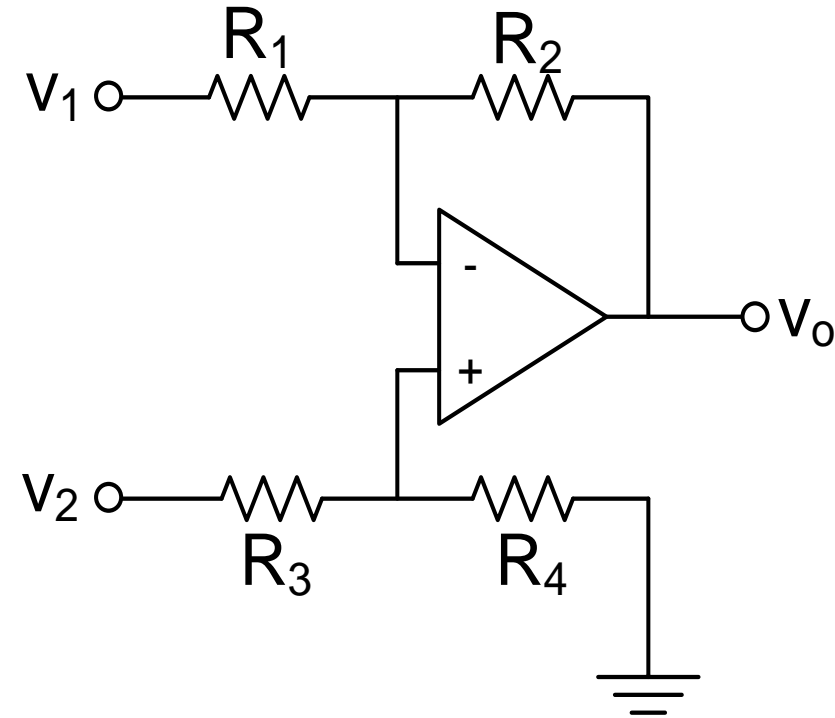
- CMRR_R indicates mismatch only due to resistors
- expressed in decibel (dB), defined as $20 \cdot {}^{10}\log(CMRR_R)$
- amplification of common mode voltage is **error source**
- large CMRR implies small influence of common mode signal on output signal (small error)
- differential and common mode gain are dependent on each other




- sensing circuit with amplifier

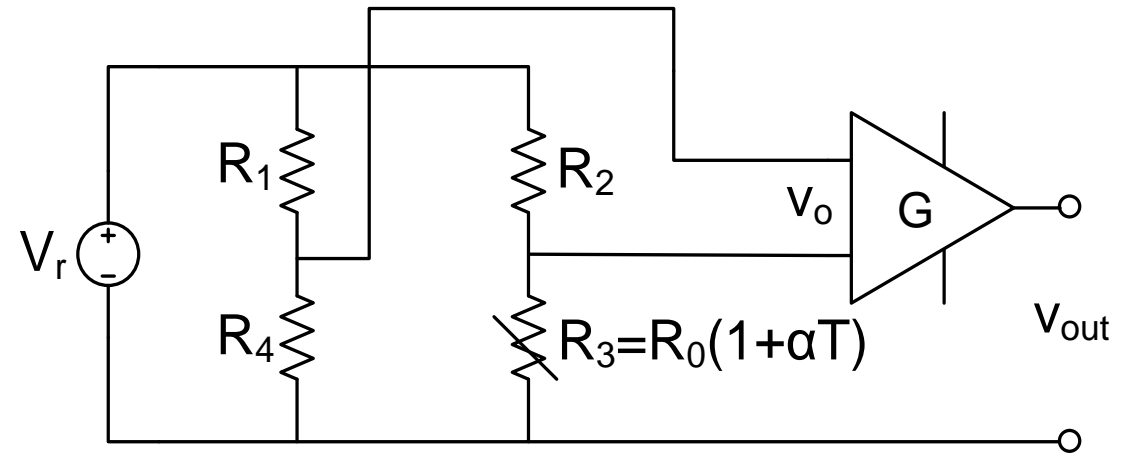




- differential amplifier

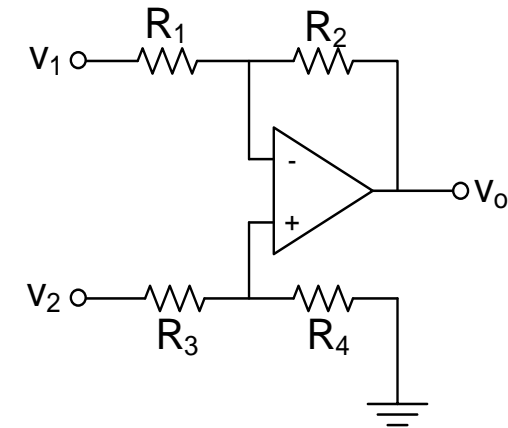

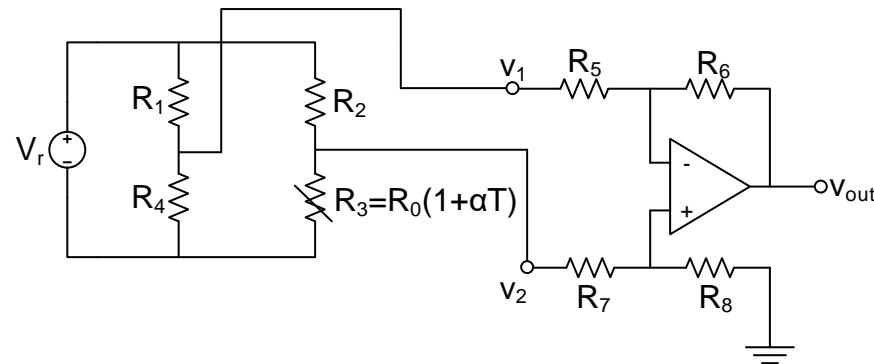- sensing circuit with differential amplifier



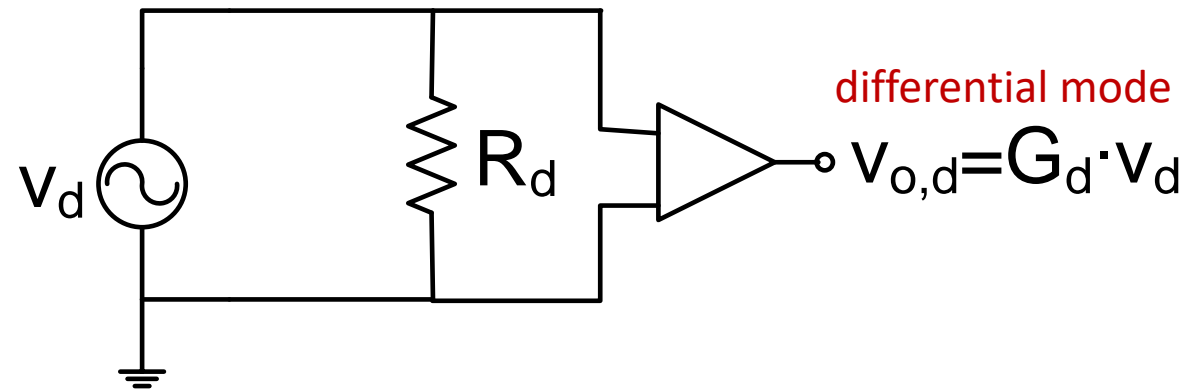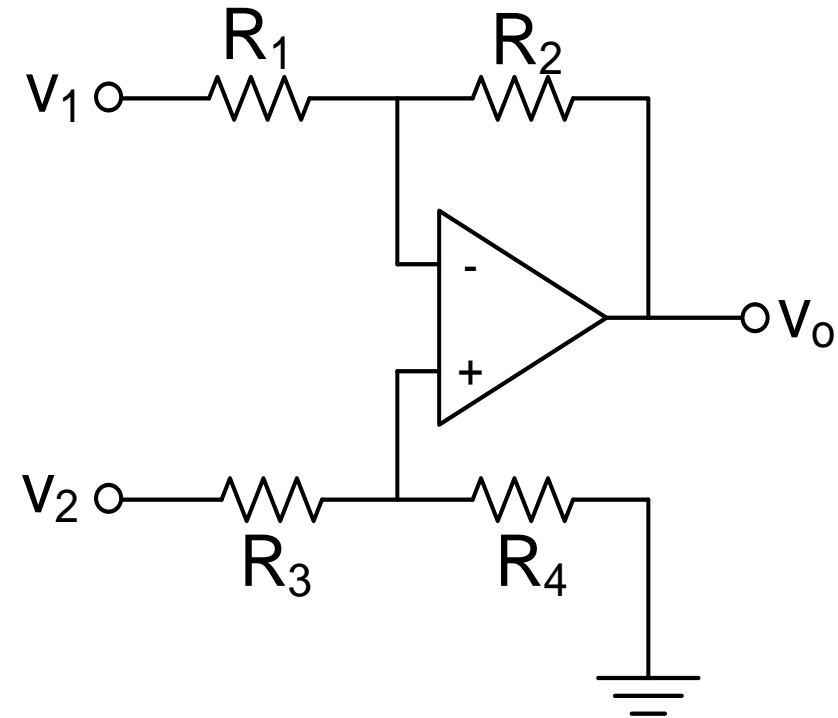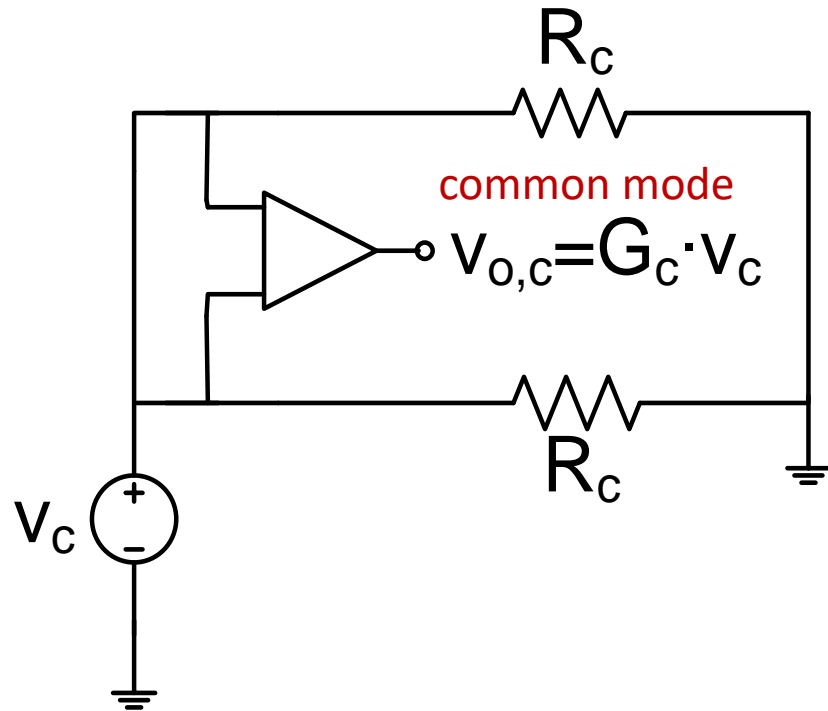
- differential and common mode analysis
- electrically equivalent circuits for both modes




- loading effect is ignored in these electrically equivalent circuits

- loading effect changes common and differential output voltage


common mode

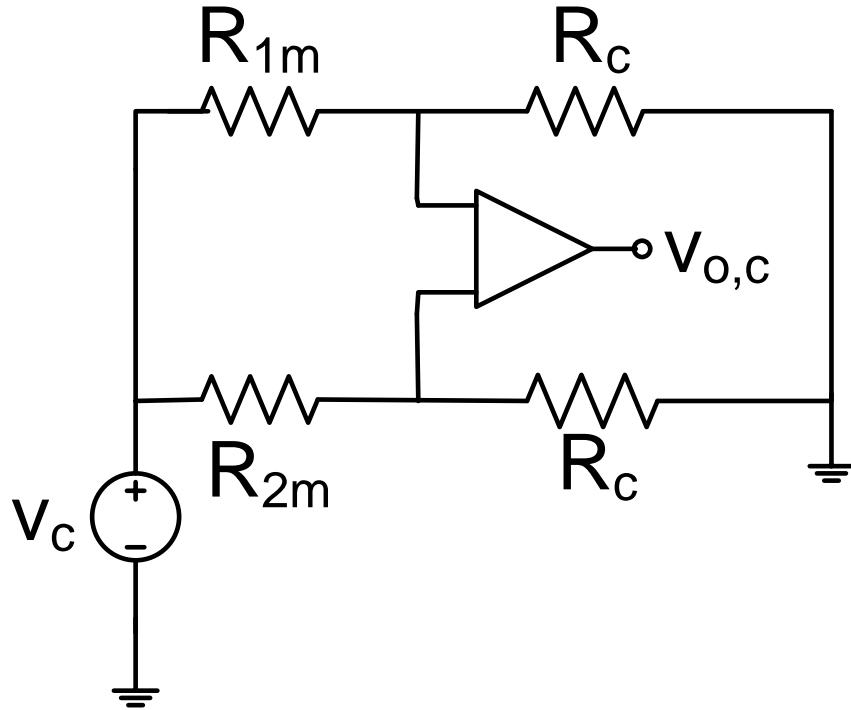


differential mode

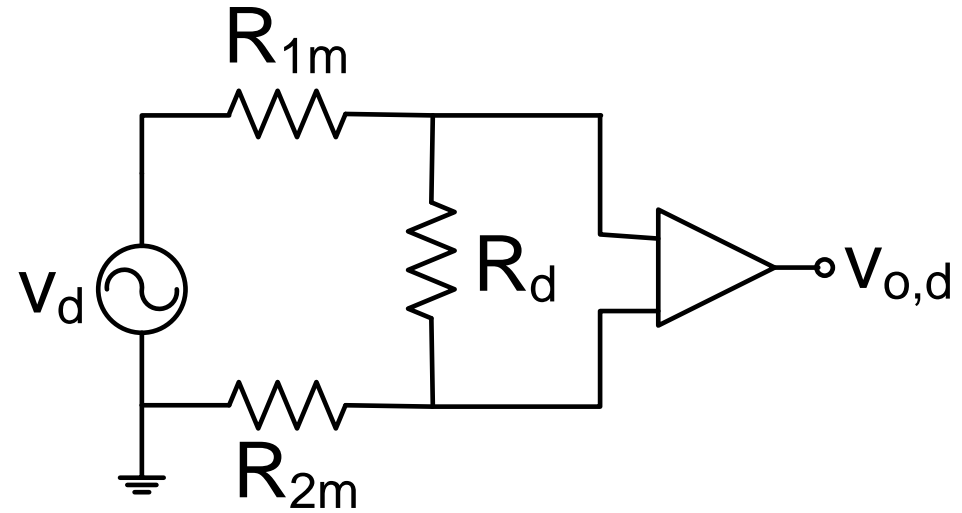

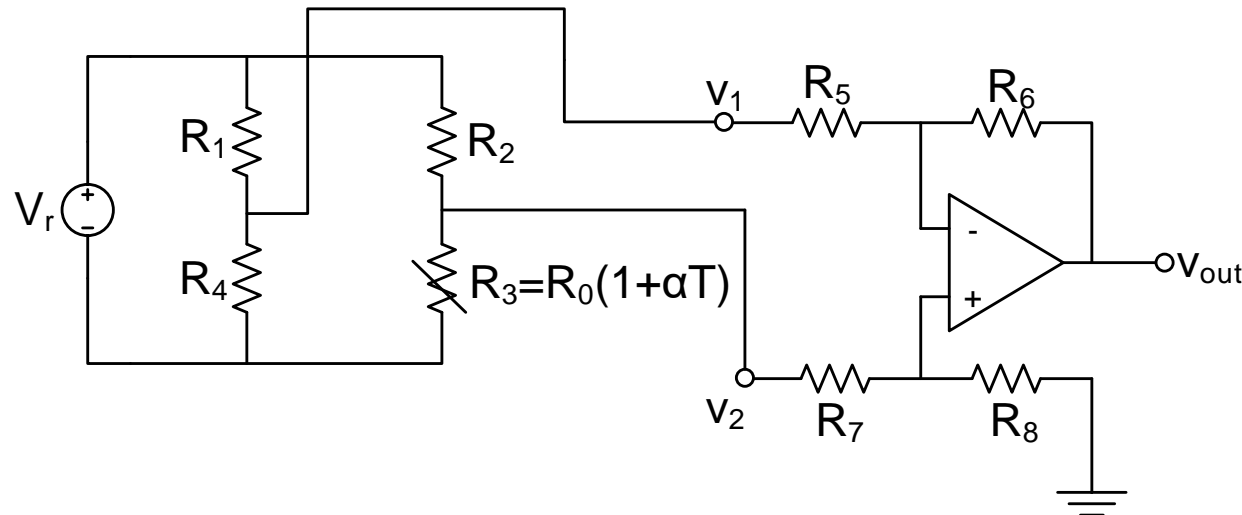
- example – PT100 temperature sensor
- PT100 ($R_0=100\Omega$ and $\alpha=0.004\Omega/\Omega/K$ at 0°C)
- measure temp from -10°C to $+50^\circ\text{C}$ in environment with $\delta=5\text{mW/K}$
- output must range from -1V to $+5\text{V}$ with error $< 0.5\%$ of the reading (due to non-linearity) plus 0.2% FSO (due to self-heating)
- we computed earlier: $R_4=100\Omega$, $R_1=R_2=3900\Omega$, $V_r=8\text{V}$, $G=128.2$
- **what are the minimal input differential and common mode resistances and the CMRR of the differential amplifier to have a negligible error (at most 10% of errors considered so far)?**



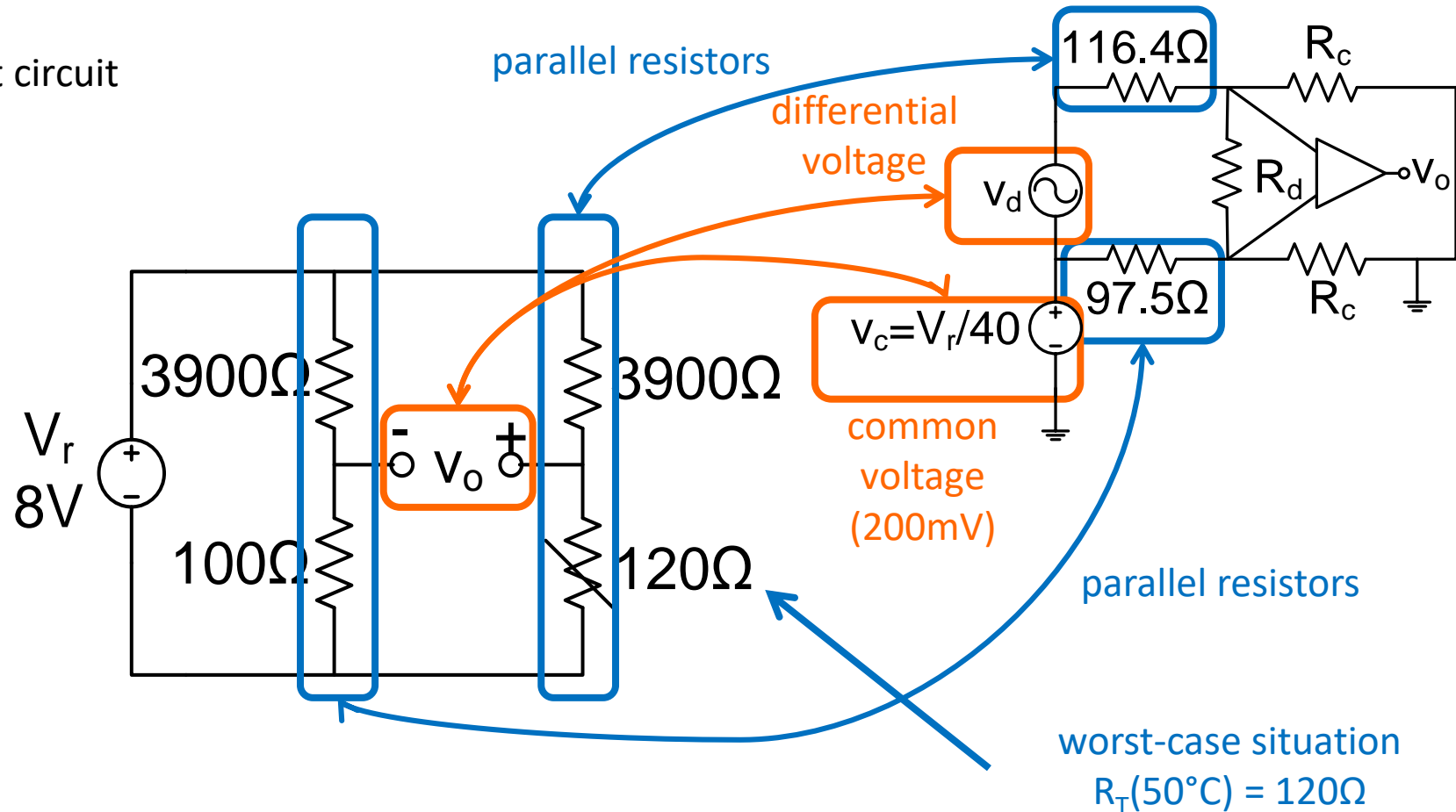- example – PT100 temperature sensor
- what are the minimal input differential and common mode resistances and the CMRR of the differential amplifier to have negligible error?
- equivalent circuit



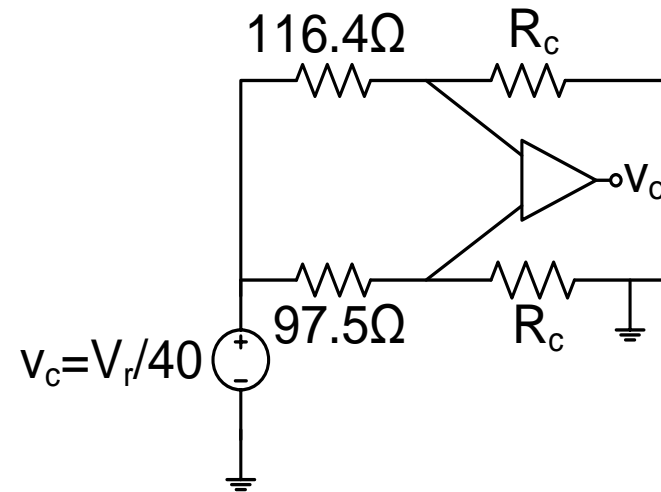- example – PT100 temperature sensor
- **what are the minimal input differential and common mode resistances and the CMRR of the differential amplifier to have negligible error?**
- common mode voltage produces
- differential voltage across bridge
- due to unequal resistors in both arm
- error amplified by differential gain
- choose error to be 10% of constant error



common mode
voltage ($V_r/40$)



bridge
expression



differential
gain



$$(200\text{mV}) \left(\frac{R_c}{R_c + 116.4\Omega} - \frac{R_c}{R_c + 97.5\Omega} \right) \cdot 128.2 < 0.1 \cdot 0.002 \cdot 5\text{V}$$

- this gives $R_c > 484\text{k}\Omega$

- example – PT100 temperature sensor
- **what are the minimal input differential and common mode resistances and the CMRR of the differential amplifier to have negligible error?**
- output voltage v_d sensed by differential
- amplifier (voltage across) R_d lower
- then v_o due to resistors

$$v_o = \frac{R_d}{R_d + 116.4\Omega + 97.5\Omega} v_d = \frac{R_d}{R_d + 213.9\Omega} v_d$$


- leads to relative error

$$\varepsilon = \left| \frac{v_o - v_d}{v_d} \right| = \left| \left(\frac{R_d}{R_d + 213.9\Omega} v_o - v_o \right) / v_o \right| = \frac{213.9\Omega}{R_d + 213.9\Omega}$$

- choose error to be 10x smaller than allowed relative error (0.5%)

$$\frac{213.9\Omega}{R_d + 213.9\Omega} < 0.1 \cdot 0.5\%$$

- this gives $R_d > 428\text{k}\Omega$

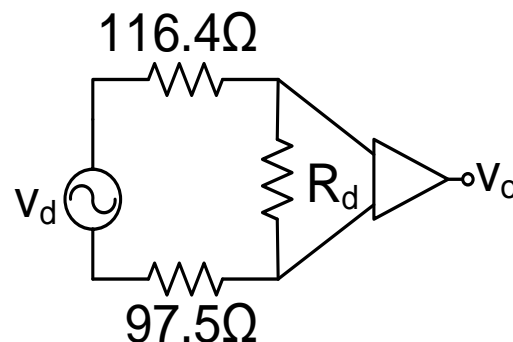


- example – PT100 temperature sensor
- **what are the minimal input differential and common mode resistances and the CMRR of the differential amplifier to have negligible error?**
- choose negligible error to be an error
- which is at most 10% of constant allowed
- error (0.2% of 5V)
- maximal common mode gain

$$G_c = \frac{0.1 \cdot (0.002 \cdot 5V)}{200mV} = 0.005$$

- differential gain is 128.2
- required common mode rejection ratio
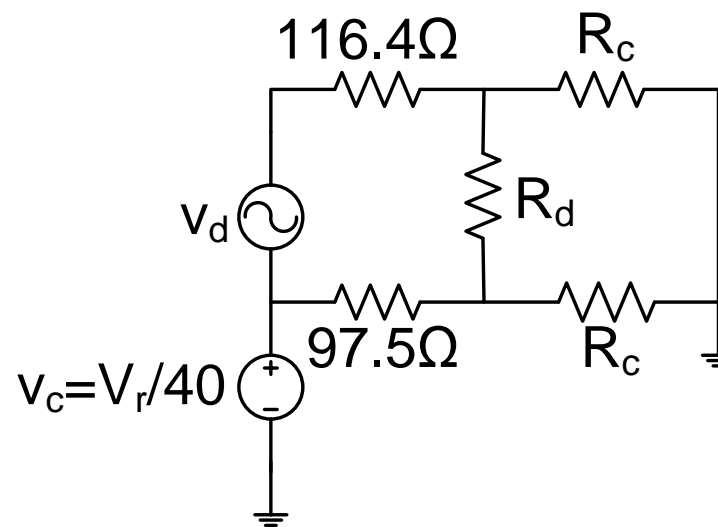
$$CMRR > \frac{128.2}{0.005} = 25640 = 88dB$$



- example – PT100 temperature sensor
- **what are the minimal input differential and common mode resistances and the CMRR of the differential amplifier to have negligible error?**

- summary
 - CMRR = 88dB
 - $R_c > 484\text{k}\Omega$
 - $R_d > 428\text{k}\Omega$


- observations
 - differential impedance high to prevent signal loading
 - common mode impedance high to prevent common mode signal from producing differential voltage
 - result of high impedances is a low CMRR

- **instrumentation amplifier** is a differential amplifier with
 - high input and low output impedance
 - high CMRR
 - high gain (adjustable with resistor R_1)
- output of first stage

$$v_a = \left(1 + \frac{R_2}{R_1}\right)v_1 - \frac{R_2}{R_1}v_2$$

$$v_b = \left(1 + \frac{R_2}{R_1}\right)v_2 - \frac{R_2}{R_1}v_1$$

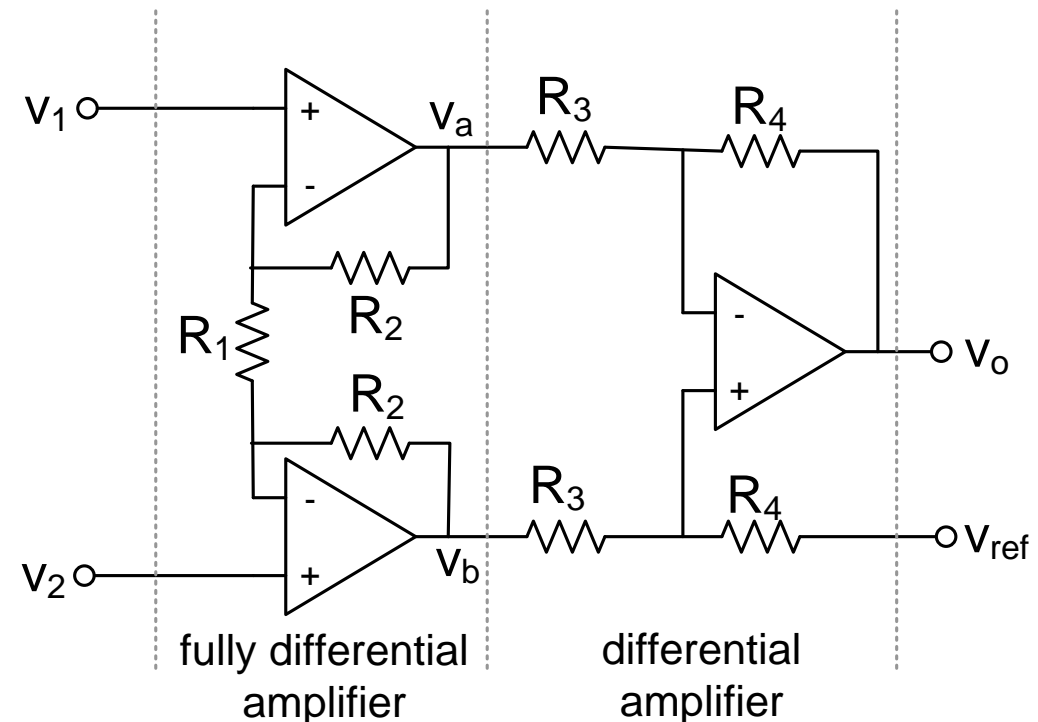- output is combination of
 - non-inverting amplifier
 - inverting amplifier



- **instrumentation amplifier** is a differential amplifier with
 - high input and low output impedance
 - high CMRR
 - high gain (adjustable with resistor R_1)
- output of second stage


$$v_a = \left(1 + \frac{R_2}{R_1}\right)v_1 - \frac{R_2}{R_1}v_2$$

$$v_b = \left(1 + \frac{R_2}{R_1}\right)v_2 - \frac{R_2}{R_1}v_1$$

$$v_o - v_{ref} = (v_b - v_a) \frac{R_4}{R_3}$$

$$= \left(1 + \frac{2R_2}{R_1}\right) \frac{R_4}{R_3} (v_2 - v_1)$$
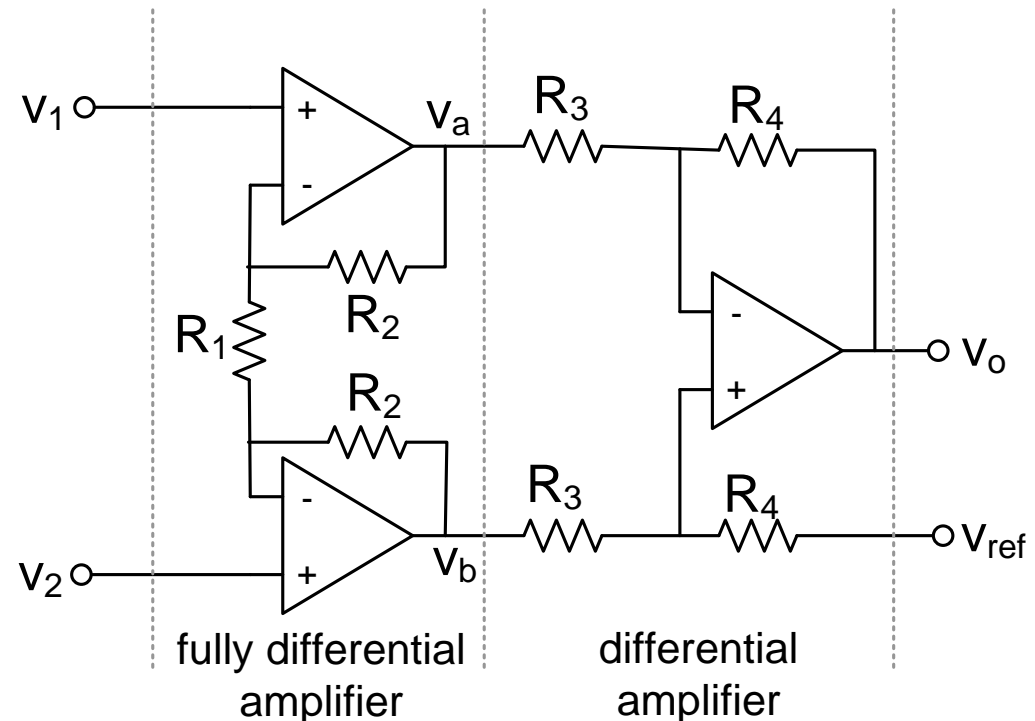
$$= (1 + G)k(v_2 - v_1) \quad \text{with } G = \frac{2R_2}{R_1}$$



- **instrumentation amplifier** is a differential amplifier with
 - high input and low output impedance
 - high CMRR
 - high gain (adjustable with single resistor)


- output of second stage

$$v_o - v_{ref} = (1 + G)k(v_2 - v_1)$$



$$G = \frac{2R_2}{R_1} \quad k = \frac{R_4}{R_3}$$

- R_1 plays no role in matching of differential amplifier
- differential mode gain independent of CMRR

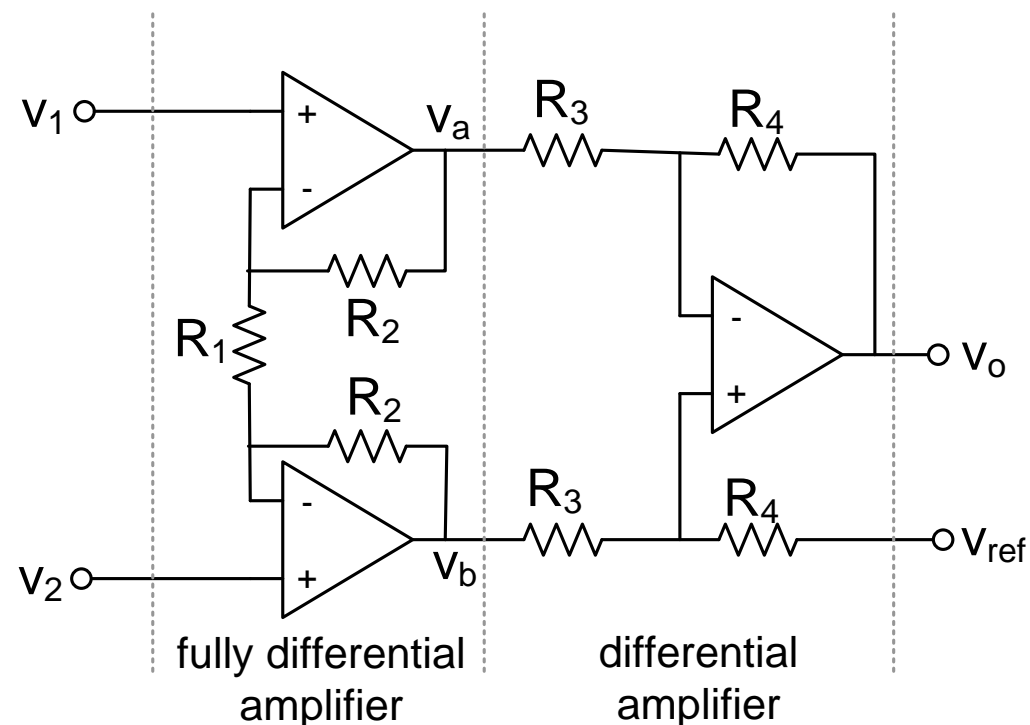
$$CMRR_{IA} \approx (1 + G) \cdot CMRR_{DA}$$



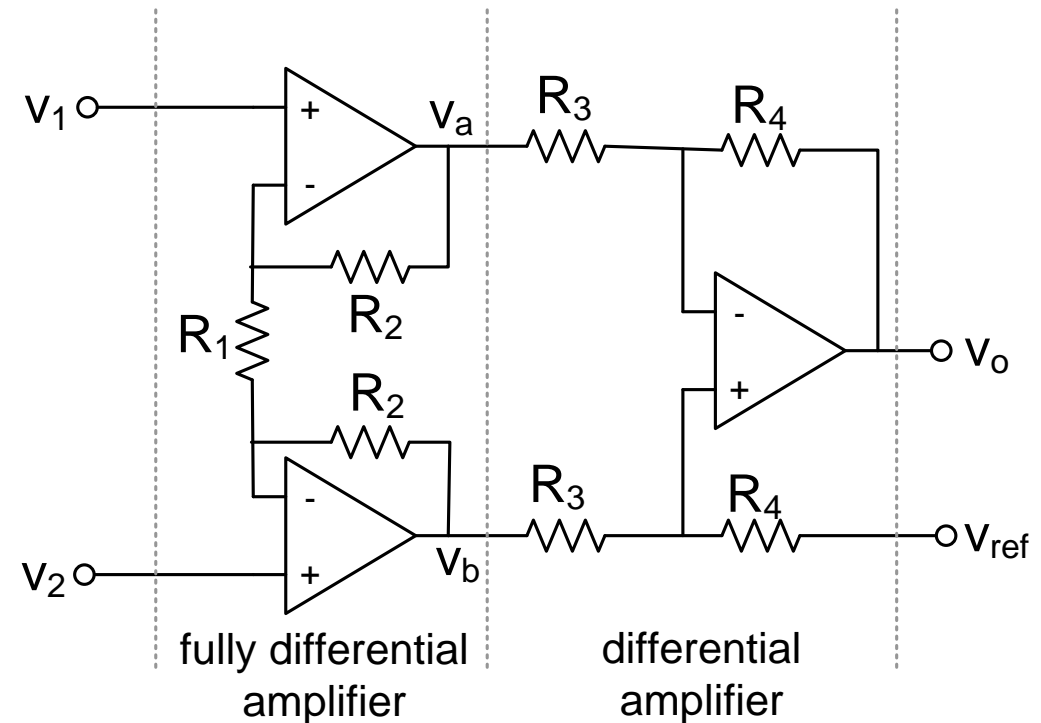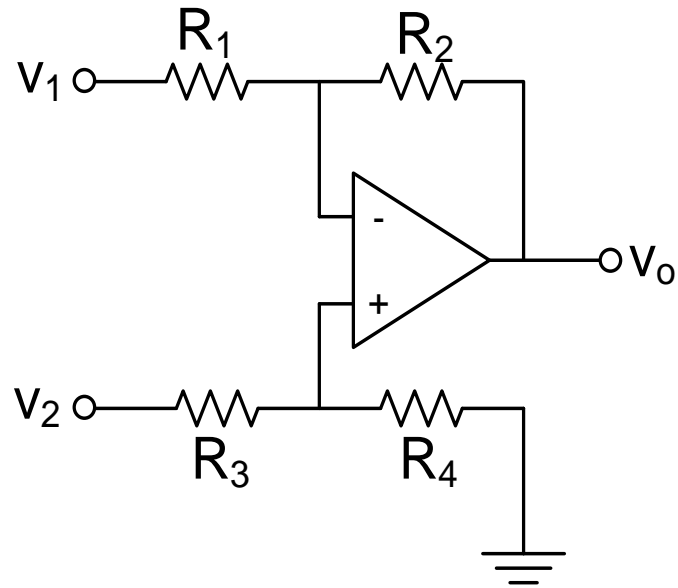- operational amplifiers can increase output signal
- errors are increased with same magnitude
- two types of amplifiers studied
 - differential amplifiers
 - instrumentation amplifiers



Example – pressure sensor

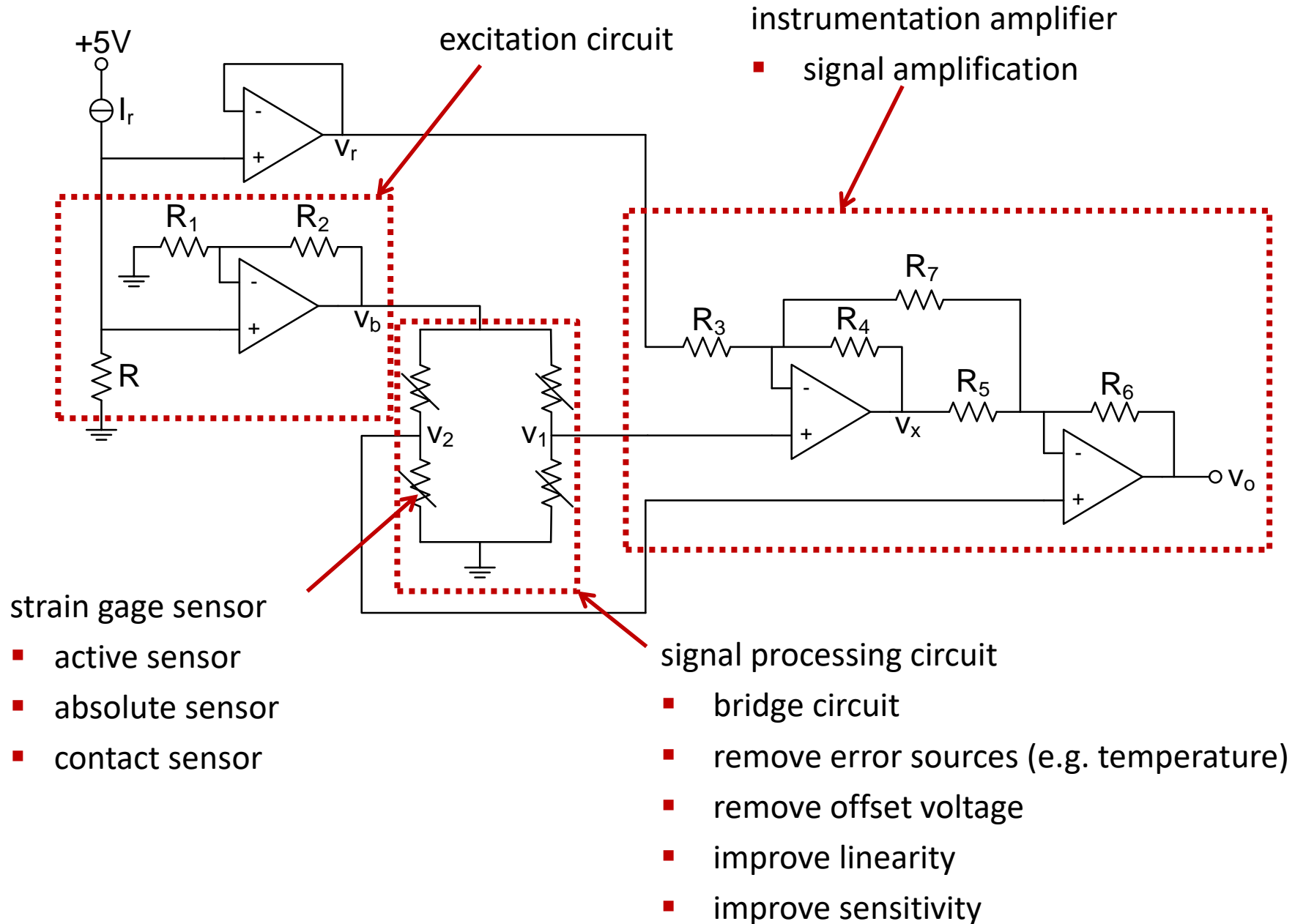

- **increase sensitivity** by adding sensor on other side of opposing arm
- bridge output voltage

$$v_o = \left(\frac{R_3}{R_3 + R_4} - \frac{R_1}{R_1 + R_2} \right) V_r$$


$$R_2 = R_3 = R_0(1+x), \quad k = \frac{R_0}{R_4} = \frac{R_1}{R_0}$$

$$\left. \begin{array}{l} \Rightarrow v_o = \frac{x}{1+x+k} V_r \\ R_1 = R_4 \Rightarrow k = 1 \end{array} \right\} \Rightarrow v_o = \frac{x}{2+x} V_r$$




- **relative non-linearity** error due to bridge circuit
 - ideal output voltage $v_i = \frac{x}{2} V_r$

$$\varepsilon = \frac{|v_o - v_i|}{v_i} = \frac{\left| \frac{x}{2+x} V_r - \frac{x}{2} V_r \right|}{\frac{x}{2} V_r} = \left| \frac{2}{x} \frac{x}{2+x} - 1 \right|$$

$$\Leftrightarrow \varepsilon = \left| \frac{2}{2+x} - 1 \right| = \left| \frac{-x}{2+x} \right| = \left| \frac{x}{2+x} \right|$$

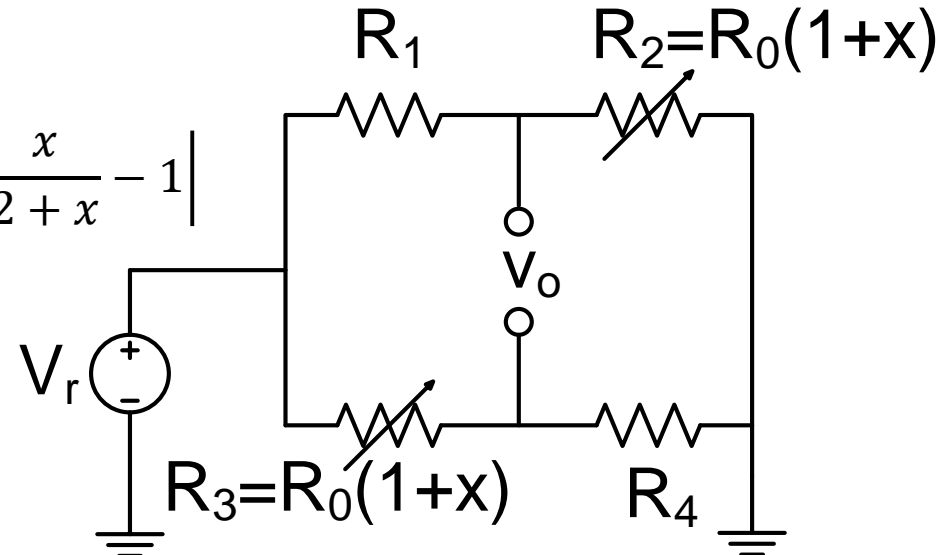

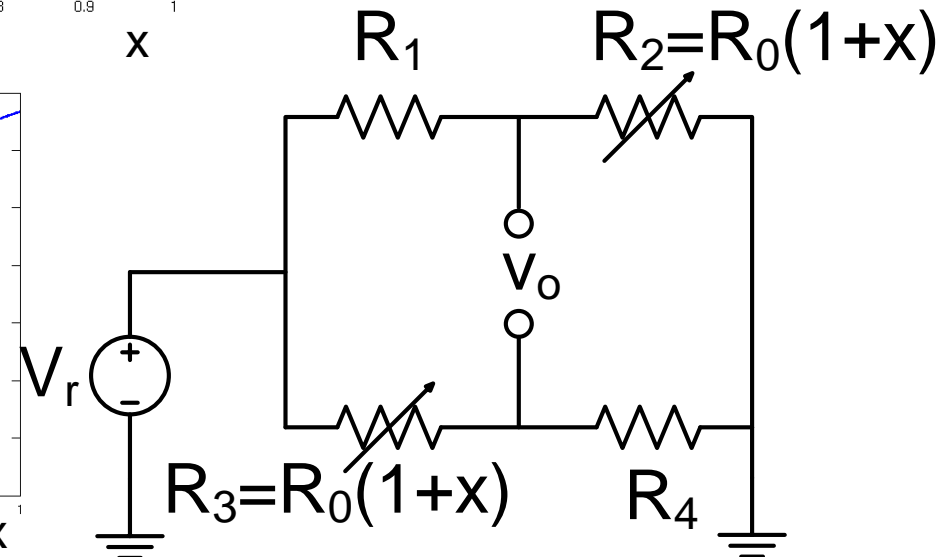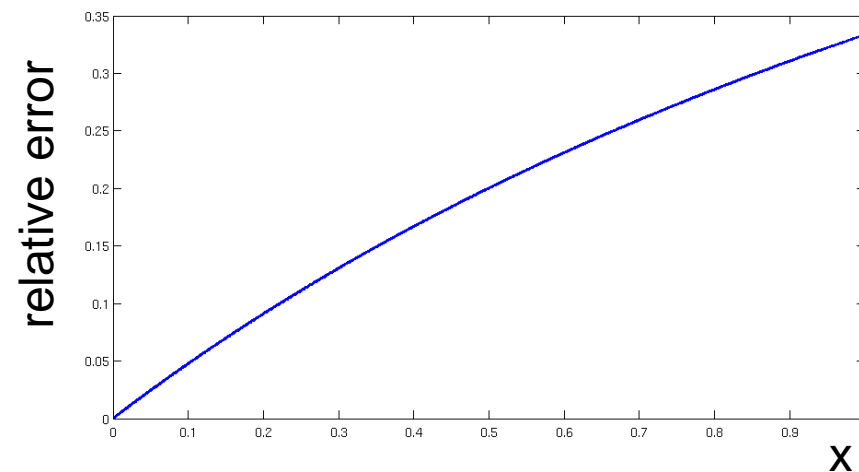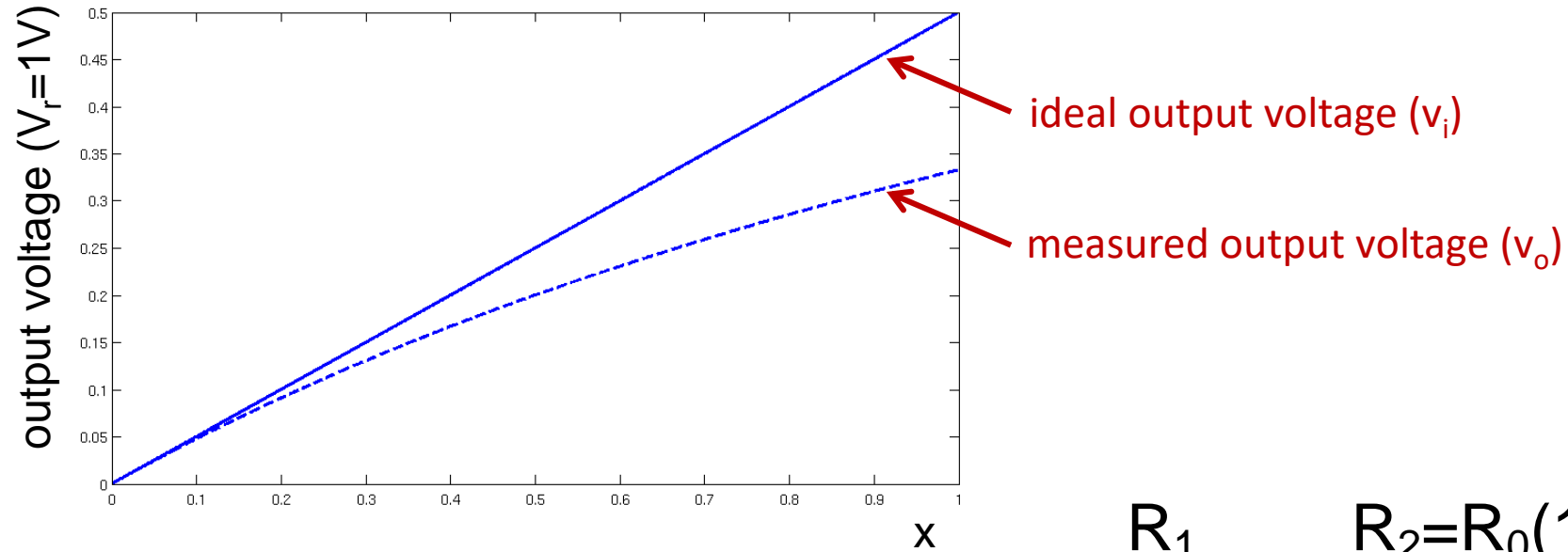- **increase sensitivity** by adding sensor on other side of opposing arm



example – pseudo-bridge with two resistive sensors

- two equal linear resistance sensors: $R_3=R_2=R_0(1+x)$
- two equal fixed resistors: $R_1=R_4$

what value should R_1 and R_4 have to get an output voltage (V_o) which is directly proportional to the measured quantity x ?


$$\frac{V_r - v_p}{R_3} = \frac{v_p}{R_4} \Leftrightarrow v_p = \frac{R_4}{R_3 + R_4} V_r \quad (= \text{voltage divider})$$

$$\frac{V_r - v_n}{R_1} = \frac{v_n - v_o}{R_2} \Leftrightarrow \frac{R_2}{R_1} V_r - \frac{R_2}{R_1} v_n - v_n = -v_o$$

$$\Leftrightarrow v_o = -\frac{R_2}{R_1} V_r + \left(\frac{R_2}{R_1} + 1 \right) v_n$$

using $v_p=v_n$ we find
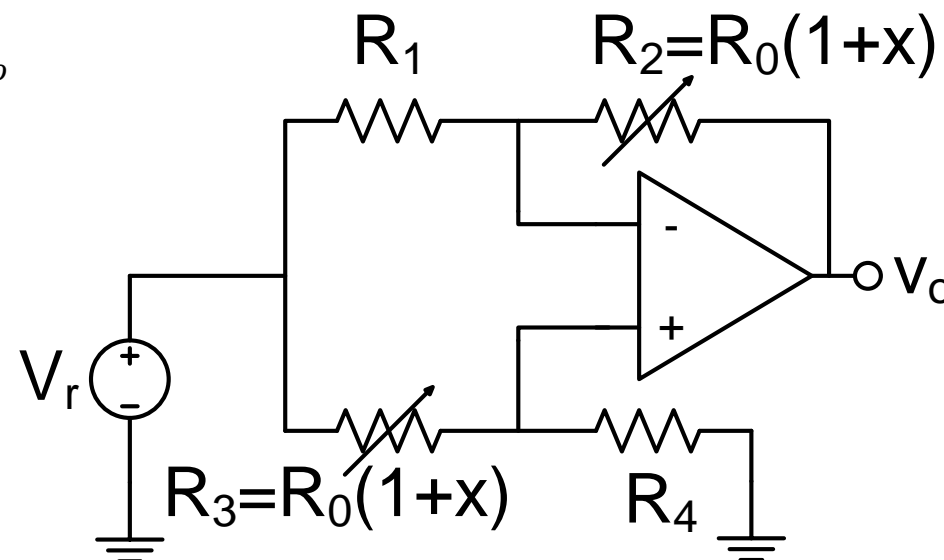
$$v_o = -\frac{R_2}{R_1} V_r + \left(\frac{R_2 + R_1}{R_1} \right) \left(\frac{R_4}{R_3 + R_4} \right) V_r$$



example – pseudo-bridge with two resistive sensors

- two equal linear resistance sensors: $R_3=R_2=R_0(1+x)$
- two equal fixed resistors: $R_1=R_4$

what value should R_1 and R_4 have to get an output voltage (V_o) which is directly proportional to the measured quantity x ?


$$v_o = -\frac{R_2}{R_1}V_r + \left(\frac{R_2 + R_1}{R_1}\right)\left(\frac{R_4}{R_3 + R_4}\right)V_r$$

using $R_1=R_4$ and $R_2=R_3$ we find

$$v_o = -\frac{R_2}{R_1}V_r + \left(\frac{R_2 + R_1}{R_2 + R_1}\right)V_r$$

using $R_2=R_0(1+x)$ we find
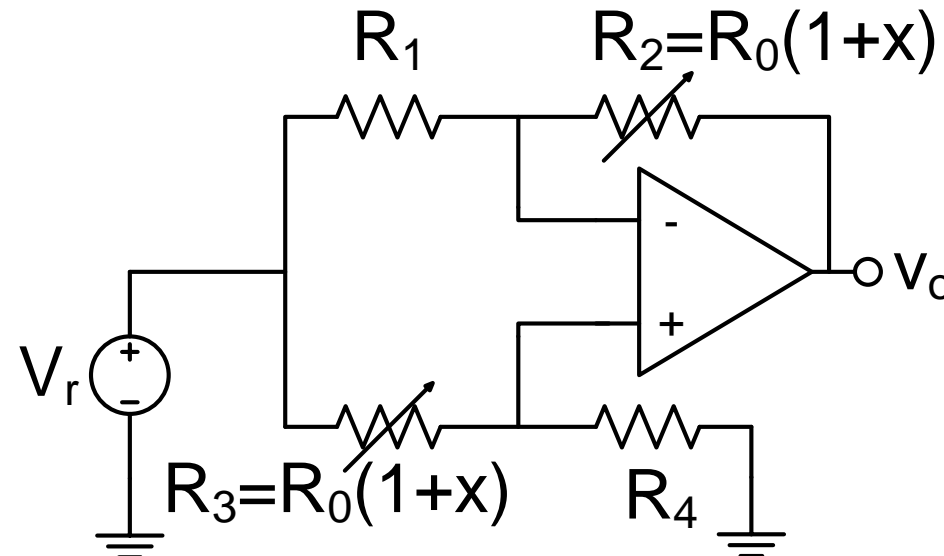
$$v_o = -\frac{R_0(1+x)}{R_1}V_r + V_r = \left[1 - \frac{R_0}{R_1} - \frac{R_0}{R_1}x\right]V_r$$



example – pseudo-bridge with two resistive sensors

- two equal linear resistance sensors: $R_3=R_2=R_0(1+x)$
- two equal fixed resistors: $R_1=R_4$

what value should R_1 and R_4 have to get an output voltage (V_o) which is directly proportional to the measured quantity x ?

$$v_o = -\frac{R_0(1+x)}{R_1}V_r + V_r = \left[1 - \frac{R_0}{R_1} - \frac{R_0}{R_1}x\right]V_r$$

v_o directly proportional to x when

$$1 - \frac{R_0}{R_1} = 0 \Rightarrow R_0 = R_1$$

output voltage then equal to

$$v_o = -xV_r$$

non-linearity is removed by circuit

