


## Sensing, Computing, Actuating


Sander Stuijk ([s.stuijk@tue.nl](mailto:s.stuijk@tue.nl))

# **ANALOG-DIGITAL CONVERSION**



(Chapter 2.7)

# Example – pressure sensor

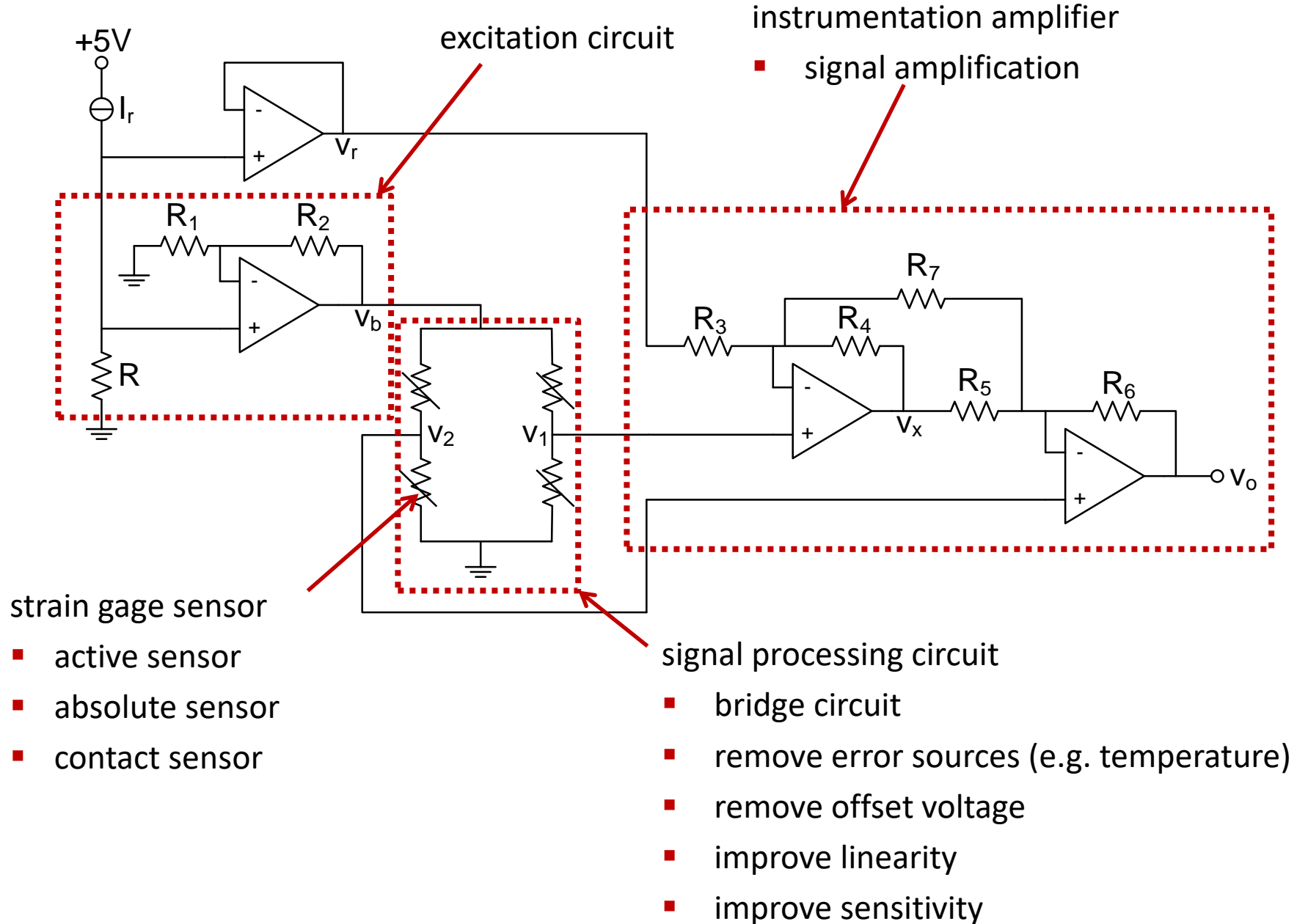


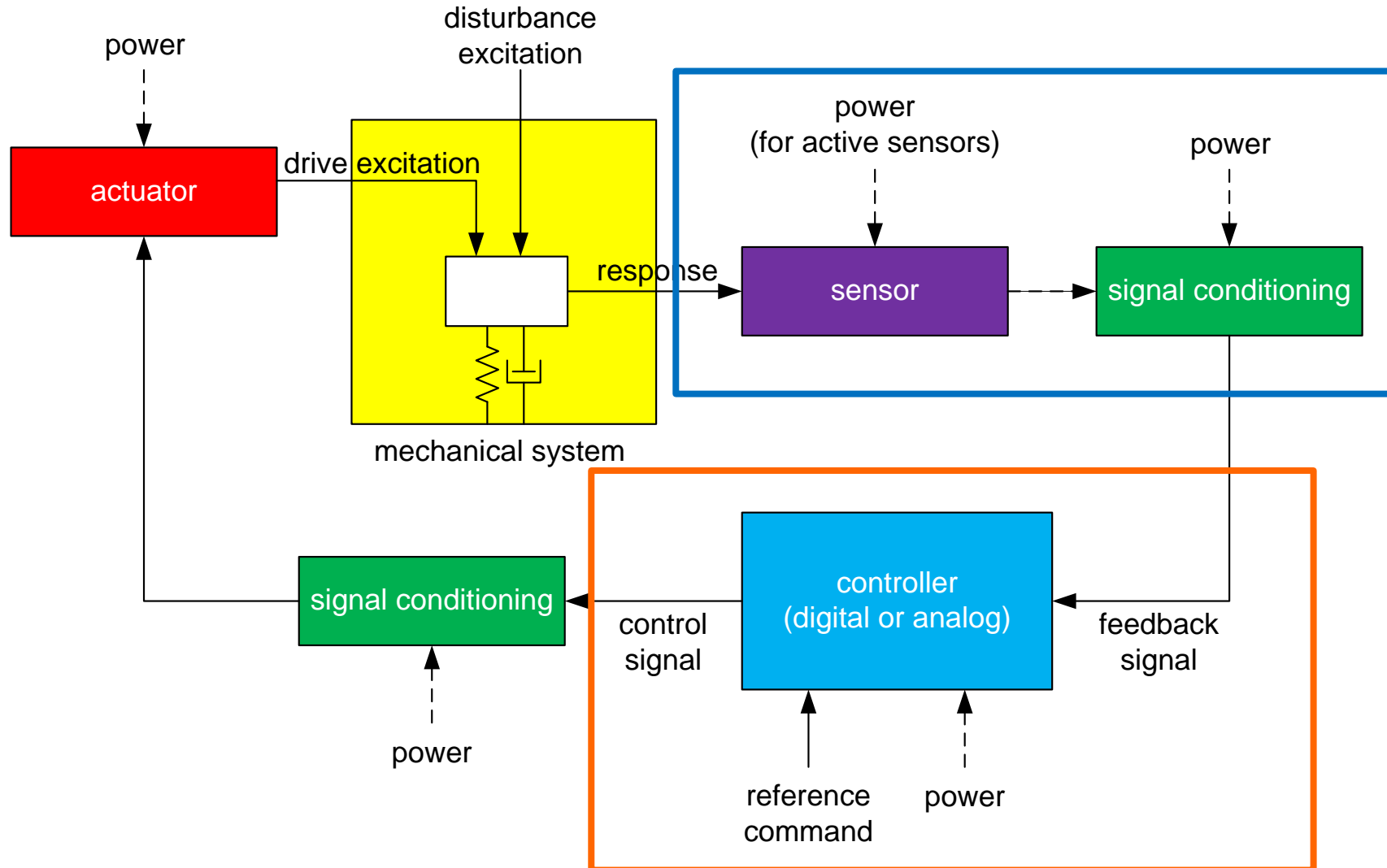

  
- most **physical signals** are **continuous**
  - speech and music signals, biomedical signals
  - most communication signals that are broadcast through the air
- **analog signal**
  - continuous in time
  - continuous in value (amplitude)
- **analog system**
  - works directly on analog signals
  - circuits: resistors, capacitors, transistors, op-amps, ...




 
- **digital systems**
  - computers, microprocessors, embedded processors, micro controllers, ...
- **digital signal**
  - discrete in time
  - discrete in value
- advantages of digital systems compared to analog systems
  - it is easier to **process** signals
  - it is easier to **store** signals
  - it is easier to **transmit** signals



 - **limitations** of digital systems
  - cannot deal with **continuous-time** signals
    - solution: sample signal at regular time interval







  - **limitations** of digital systems
  - cannot deal with **continuous-time** signals
    - solution: sample signal at regular time interval
  - cannot store values with a **continuous range**
    - solution: approximate continuous value with digital value





    - analog signal digitized using **ADC**
- ADC determines resolution of sensor system
- **resolution** is smallest change in input which can be sensed
- 2-bit A/D converter (assume max input voltage = 4V)
  - $2^2 = 4$  levels
  - resolution: 1V/bit
- 3-bit A/D converter
  - $2^3 = 8$  levels
  - resolution: 0.5V/bit



- analog signal digitized using **ADC**
- ADC determines resolution of sensor system
- **resolution** is smallest change in input which can be sensed
- **how many bits should an A/D converter have to achieve a resolution of 3.5mV/bit if its maximal input voltage is 4V?**
- in general it holds that

$$n = \left\lceil \frac{\log\left(\frac{V_{\max}}{\text{resolution } V/\text{bit}}\right)}{\log(2)} \right\rceil$$


- substituting values gives

$$n = \left\lceil \frac{\log\left(\frac{4V}{3.5 \cdot 10^{-3}V/\text{bit}}\right)}{\log(2)} \right\rceil = 11\text{bit}$$

- digital system works on digitized samples of the signal



 - connecting the analog and digital world



- S/H – sample and hold circuit
- ADC – analog to digital conversion
- DAC – digital to analog conversion

- what is the output voltage  $V_o$  of the weighted-resistor DAC in terms of the input bits (digital data –  $b_i$ )?

- Kirchhoff current law at node A
  - use  $V_A = 0$  V

$$\frac{v_{n-1}}{R} + \frac{v_{n-2}}{2R} + \dots + \frac{v_0}{2^{n-1}R} + \frac{v_o}{R/2} = 0$$


- relation voltage  $v_i$  and bit  $b_i$

$$v_i = -b_i \cdot v_{ref}$$

- output voltage

$$v_o = \left( b_{n-1} + \frac{b_{n-2}}{2} + \dots + \frac{b_0}{2^{n-1}} \right) \frac{v_{ref}}{2}$$

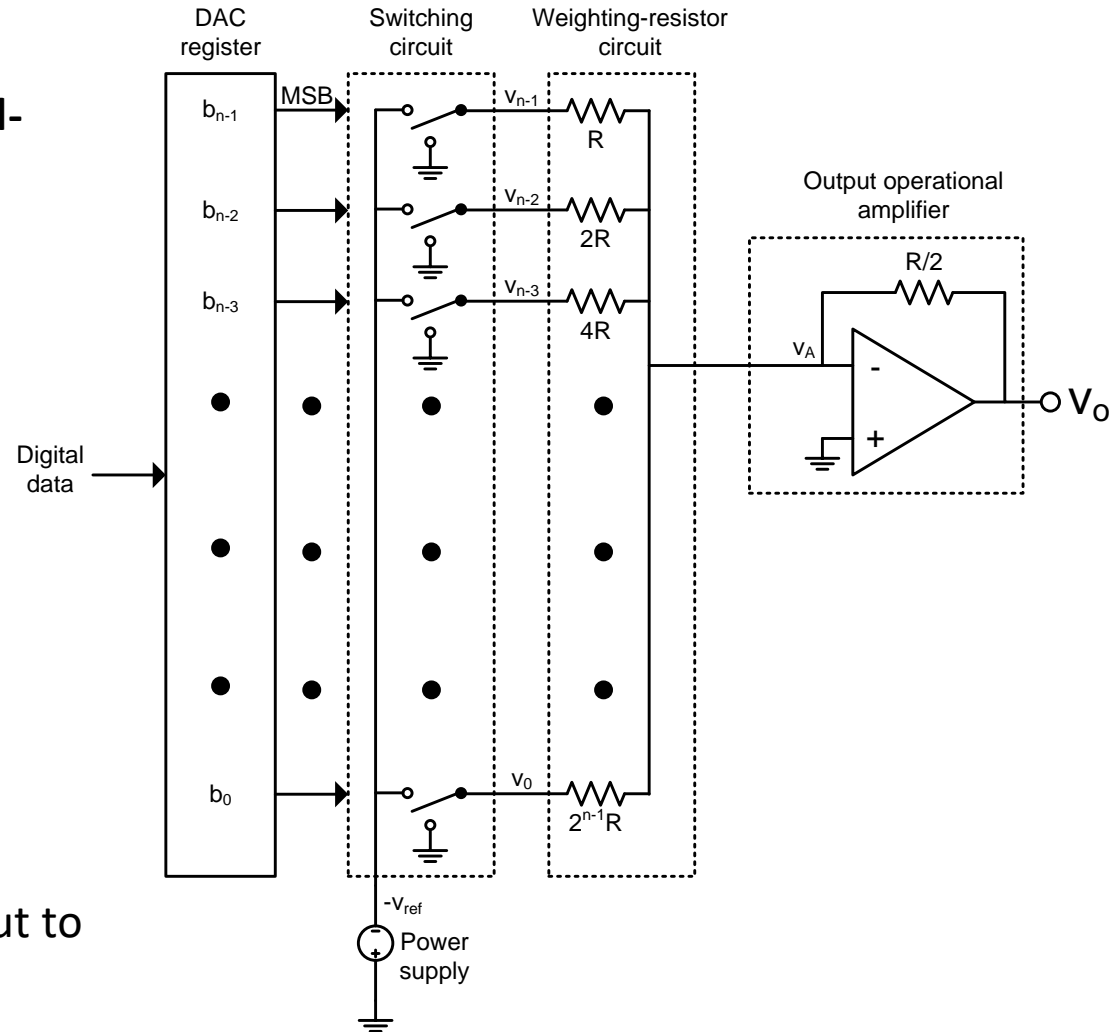- output voltage proportional to digital data input to DAC



- what is the output voltage  $V_o$  of the weighted-resistor DAC when all bits are equal to 1?

- output voltage

$$v_o = \left( b_{n-1} + \frac{b_{n-2}}{2} + \dots + \frac{b_0}{2^{n-1}} \right) \frac{v_{ref}}{2}$$

- full-scale voltage (all  $b_i = 1$ )


$$FSV = \left( 1 + \frac{1}{2} + \dots + \frac{1}{2^{n-1}} \right) \frac{v_{ref}}{2}$$

- use geometric series

$$1 + r + r^2 + \dots + r^{n-1} = \frac{1 - r^n}{1 - r}$$

- gives

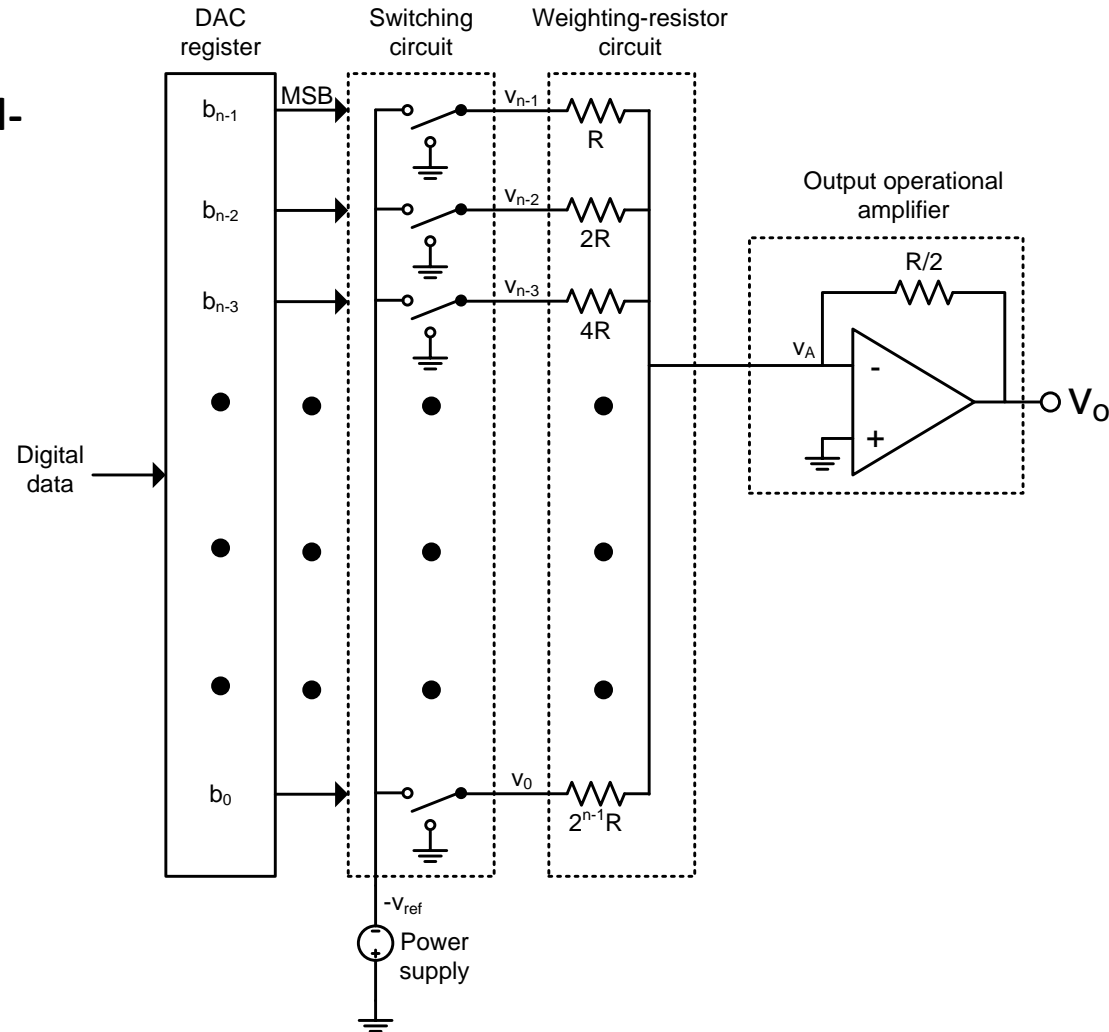
$$FSV = \left( 1 - \frac{1}{2^n} \right) v_{ref}$$




- what is the output voltage  $V_o$  of the weighted-resistor DAC when all bits are equal to 1?

$$FSV = \left(1 - \frac{1}{2^n}\right) v_{ref}$$

 - full scale output voltage is smaller than  $v_{ref}$
- error is negligible if  $n$  is large enough



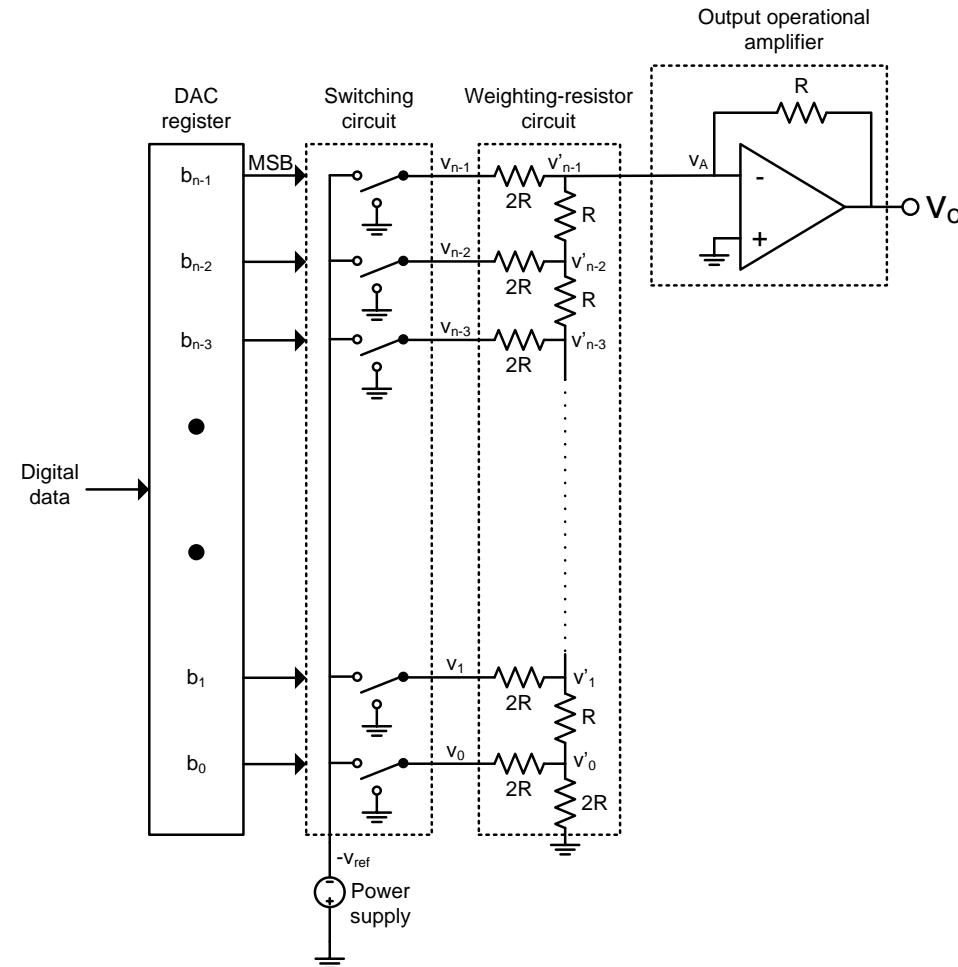- different resistor values in weighted-resistor DAC hard to produce
- ladder DAC provides alternative with only two resistor values
- what is the output voltage  $V_o$  of the ladder DAC in terms of the input bits (digital data –  $b_i$ )?**



- what is the output voltage  $V_o$  of the ladder DAC in terms of the input bits (digital data –  $b_i$ )?
- apply KCL at node  $i$

$$\frac{v_i - v'_i}{2R} + \frac{v'_{i+1} - v'_i}{R} + \frac{v_{i-1} - v'_i}{R} = 0$$


- for all nodes except nodes 0 and  $n-1$  this can be written as

$$\frac{1}{2}v_i = \frac{5}{2}v'_i - v'_{i-1} - v'_{i+1}$$

- for node 0 holds

$$\frac{v_0 - v'_0}{2R} + \frac{v'_1 - v'_0}{R} + \frac{0 - v'_0}{2R} = 0$$
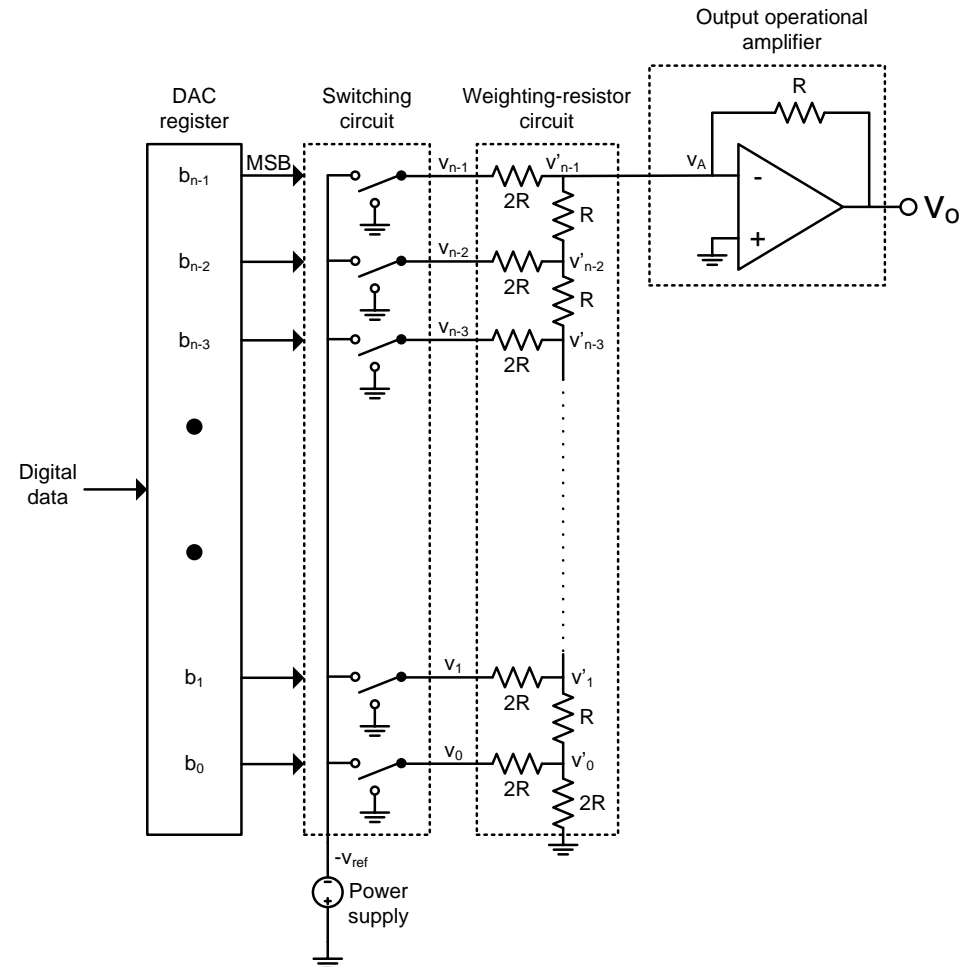
$$\Rightarrow \frac{1}{2}v_0 = 2v'_0 - v'_1$$





- what is the output voltage  $V_o$  of the ladder DAC in terms of the input bits (digital data –  $b_i$ )?
- for node  $n-1$  holds

$$\frac{v_{n-1} - v'_{n-1}}{2R} + \frac{v'_{out} - v'_{n-1}}{R} + \frac{v'_{n-2} - v'_{n-1}}{R} = 0$$


- it holds that

$$v'_{n-1} = 0$$

- hence

$$\frac{v_{n-1}}{2R} + \frac{v_{out}}{R} + \frac{v'_{n-2}}{R} = 0$$
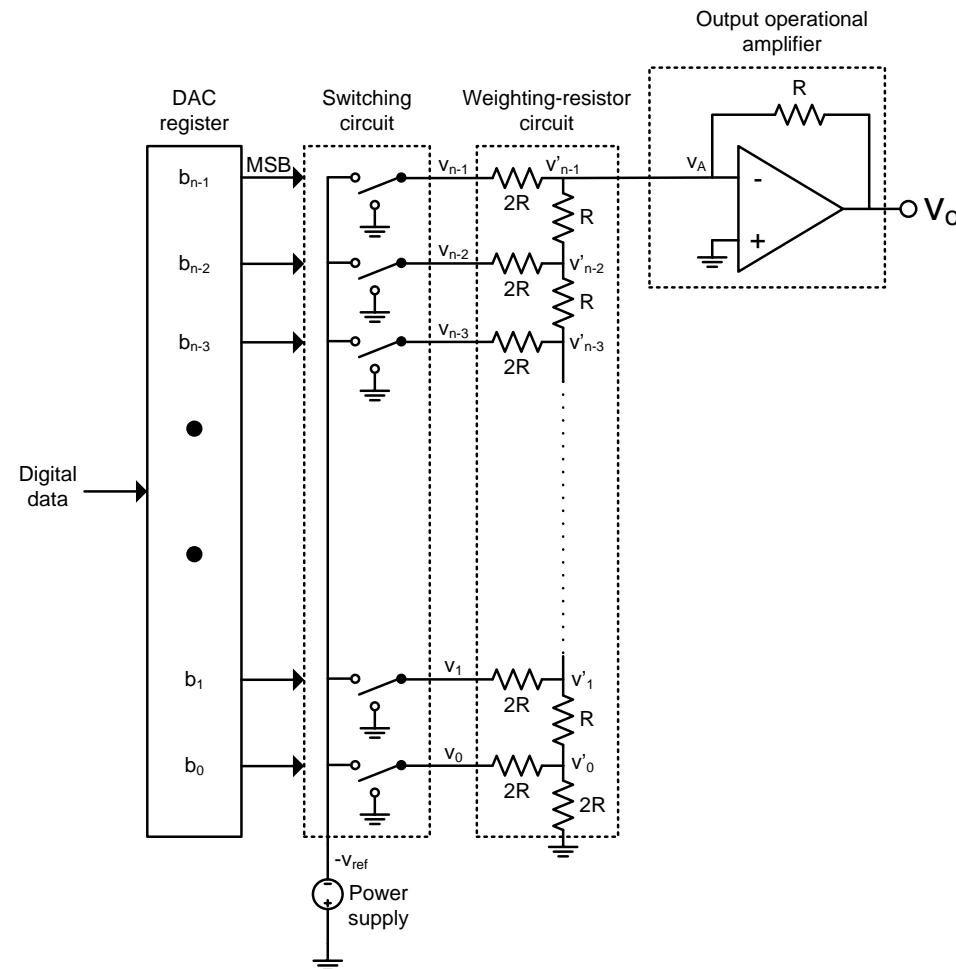
$$\Rightarrow \frac{1}{2}v_{n-1} = -v_{out} - v'_{n-2}$$



- what is the output voltage  $V_o$  of the ladder DAC in terms of the input bits (digital data –  $b_i$ )?

- summary

- for node  $i$  (except 0 and  $n-1$ ) holds

$$\frac{1}{2}v_i = \frac{5}{2}v'_i - v'_{i-1} - v'_{i+1}$$

- for node 0 holds

$$\frac{1}{2}v_0 = 2v'_0 - v'_1$$

- for node  $n-1$  holds

$$\frac{1}{2}v_{n-1} = -v_{out} - v'_{n-2}$$

- combine these equations while using  $v'_{n-1}=0$

- what is the output voltage  $V_o$  of the ladder DAC in terms of the input bits (digital data –  $b_i$ )?
- combine these equations while using  $v'_{n-1}=0$

$$\frac{1}{2}v_{n-1} = -v_{out} - v'_{n-2}$$

$$\frac{1}{2^2}v_{n-2} = \frac{1}{2} \frac{5}{2} v'_{n-2} - \frac{1}{2} v'_{n-3}$$

$$\frac{1}{2^3}v_i = \frac{1}{2} \frac{5}{2} v'_{n-3} - \frac{1}{2^2} v'_{n-4} - \frac{1}{2^2} v'_{n-2}$$

$$\frac{1}{2^{n-1}}v_0 = \frac{1}{2} \frac{5}{2} v'_0 - \frac{1}{2^{n-2}} v'_0 - \frac{1}{2^{n-2}} v'_2$$

$$\frac{1}{2^2} \frac{1}{2} v_0 = \frac{1}{2^{n-1}} 2v'_0 - \frac{1}{2^{n-1}} v'_1$$

- sum these n equations

$$\frac{1}{2}v_{n-1} + \frac{1}{2^2}v_{n-2} + \frac{1}{2^3}v_{n-3} + \dots + \frac{1}{2^n}v_0 = -v_{out}$$

- what is the output voltage  $V_o$  of the ladder DAC in terms of the input bits (digital data –  $b_i$ )?
- sum these  $n$  equations


$$\frac{1}{2}v_{n-1} + \frac{1}{2^2}v_{n-2} + \frac{1}{2^3}v_{n-3} + \dots + \frac{1}{2^n}v_0 = -v_{out}$$

- use  $v_i = -b_i v_{ref}$


$$v_{out} = \left( \frac{1}{2}b_{n-1} + \frac{1}{2^2}b_{n-2} + \frac{1}{2^3}b_{n-3} + \dots + \frac{1}{2^n}b_0 \right) v_{ref}$$

- output voltage is identical to result for the weighted-resistor DAC
- result realized with fewer resistor values (easier to manufacture)

 - digital system works on digitized samples of the signal



 
- connecting the analog and digital world





- S/H – sample and hold circuit
- ADC – analog to digital conversion
- DAC – digital to analog conversion

- several different ADC implementations are used in practical system
- most important characteristics
  - time needed for conversion
  - amount of hardware needed
- three commonly used types and their differences (speed, area)
  - flash ADC (fastest, large)
  - dual-slope ADC (slow, small)
  - successive approximation ADC (fast, medium)

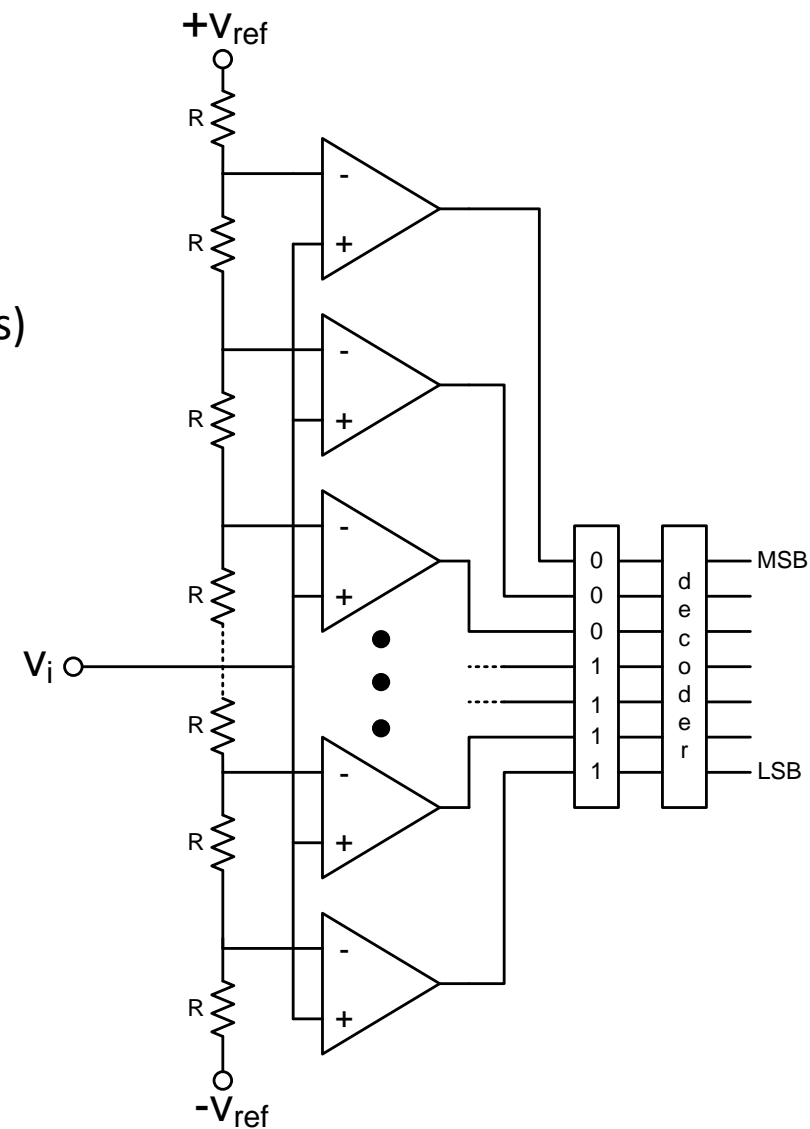- resistive divider with  $2^N$  resistors
- divider provides reference voltages
- comparators output 1 when  $v_i$  above reference voltage or 0 otherwise
- code at output of comparators known as digital thermometer code
- decoder translates code to digital value (using inverters and NAND gates)
  
- pro's and con's
  - fast
  - many comparators required



  - dual-slope ADC based operation of RC integrating circuit





- **what is the output voltage  $v_o(t)$  of the integrating circuit?**

- it holds that voltage  $V_A = 0$
- input voltage  $v_i$  is constant over time
- using KCL



$$\frac{v_i}{R} + C \frac{dv_o}{dt} = 0 \Rightarrow v_o(t) = v_o(0) - \frac{v_i \cdot t}{RC}$$

 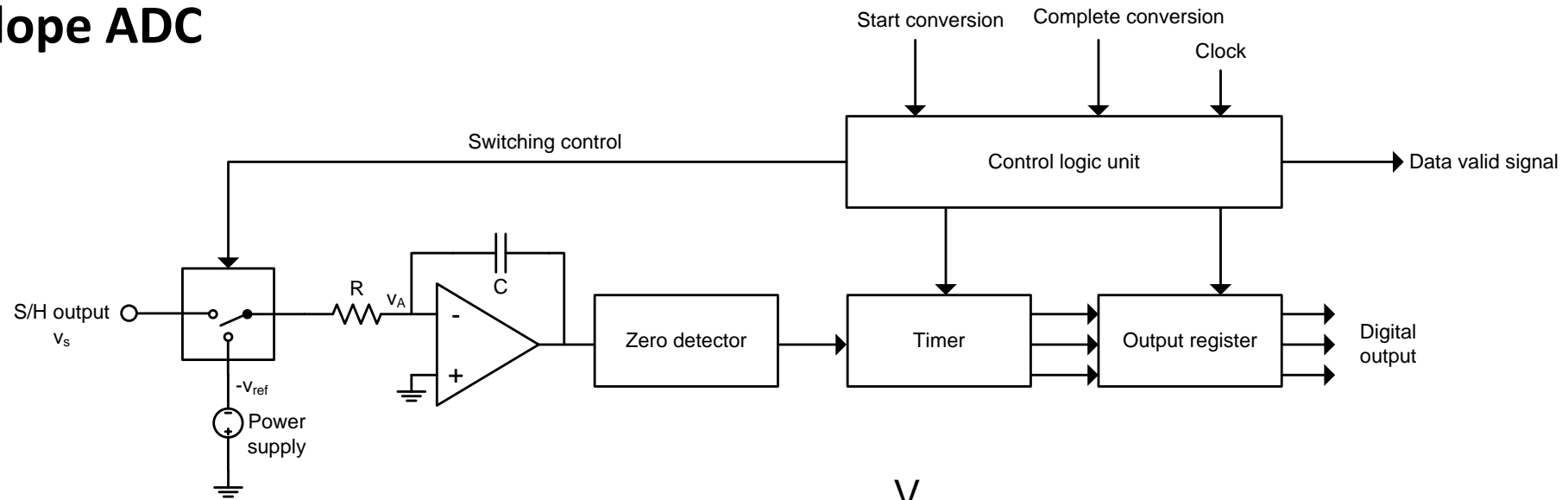- slope of curve proportional to input voltage  $v_i$






 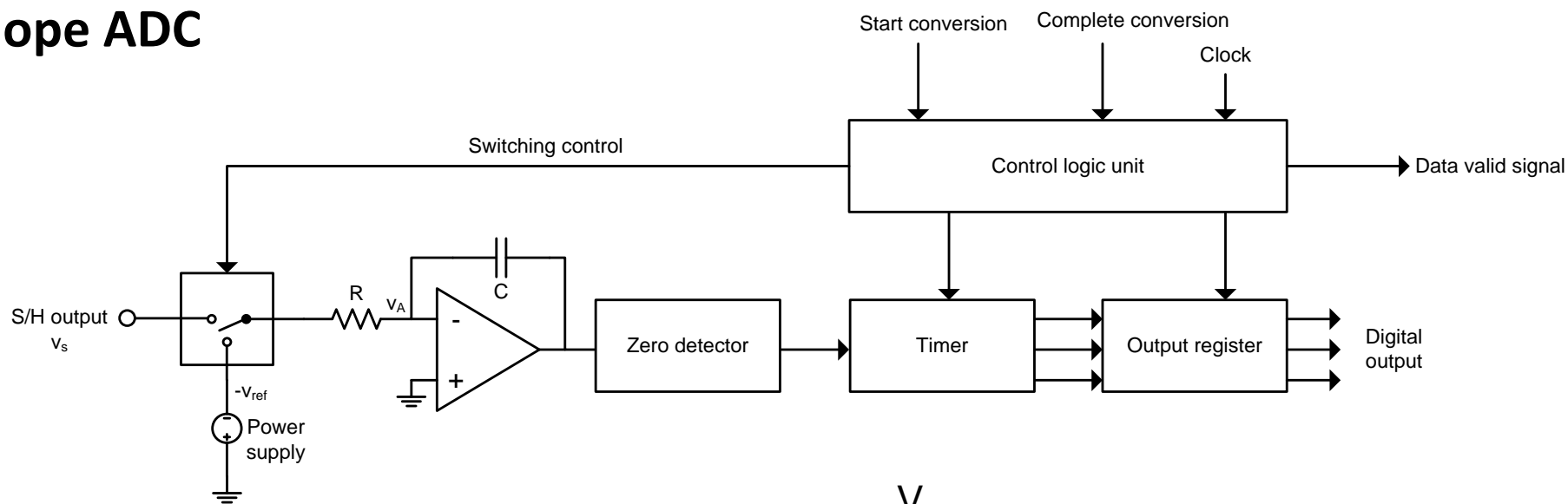- operation
- initially capacitor C is discharged (zero voltage)
- voltage  $v_s$  applied to input of switch
- start conversion signal applied
  - timer reset to zero
  - output register reset to zero
  - voltage  $v_s$  applied to integrating circuit



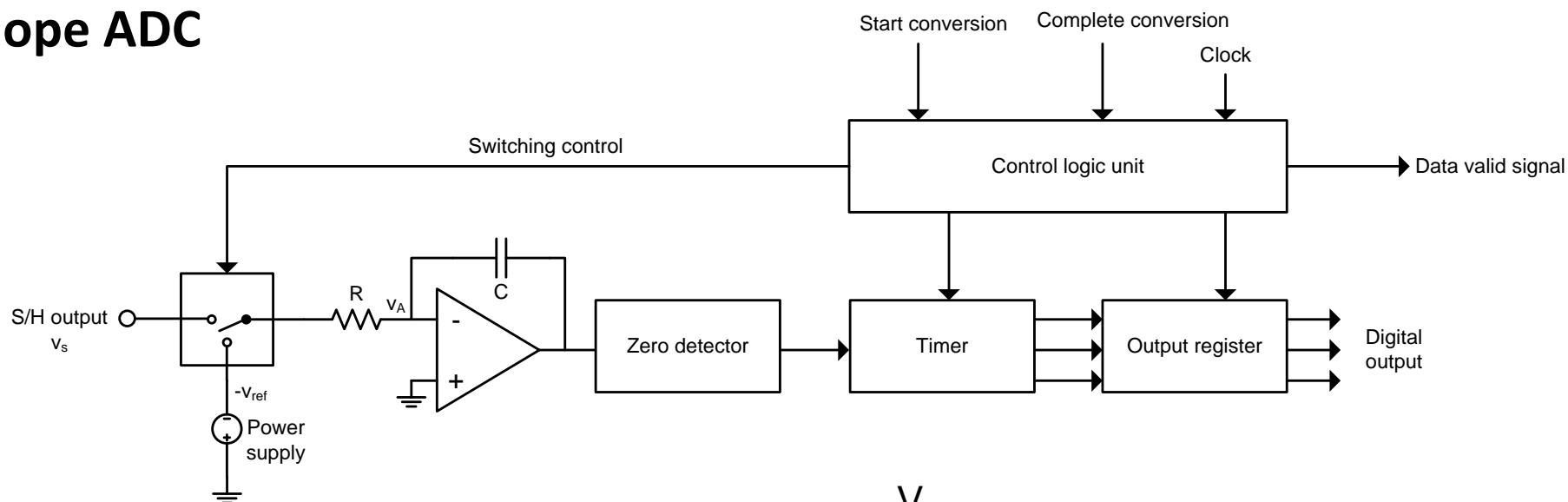- operation
- after time  $t_1$  ( $n_1$  clock cycles)
  - switch input integrating circuit to  $-v_{\text{ref}}$
  - clear timer and start timing (counting) again
- capacitor is discharging
- zero detector (comparator) detects zero crossing and stops timer at time  $t_2$  ( $n_2$  clock cycles)



- $v_o$  of integrating circuit


$$v_o(t) = v_o(0) - \frac{v_i \cdot t}{RC}$$



- at  $t_1$  it holds  $-v_c = 0 - \frac{v_s \cdot t_1}{RC} \Leftrightarrow v_c = \frac{v_s \cdot t_1}{RC}$

- at  $t_2$  it holds  $0 = -v_c + \frac{v_{ref} \cdot t_2}{RC} \Leftrightarrow v_c = \frac{v_{ref} \cdot t_2}{RC}$

$$\left. \begin{array}{l} \text{at } t_1 \\ \text{at } t_2 \end{array} \right\} \Rightarrow v_s \cdot t_1 = v_{ref} \cdot t_2 \Leftrightarrow v_s = v_{ref} \frac{t_2}{t_1} = v_{ref} \frac{n_2}{n_1} = \frac{v_{ref}}{n_1} n_2$$

 - $v_{ref}$  and  $n_1$  are fixed;  $v_s$  proportional to  $n_2$




 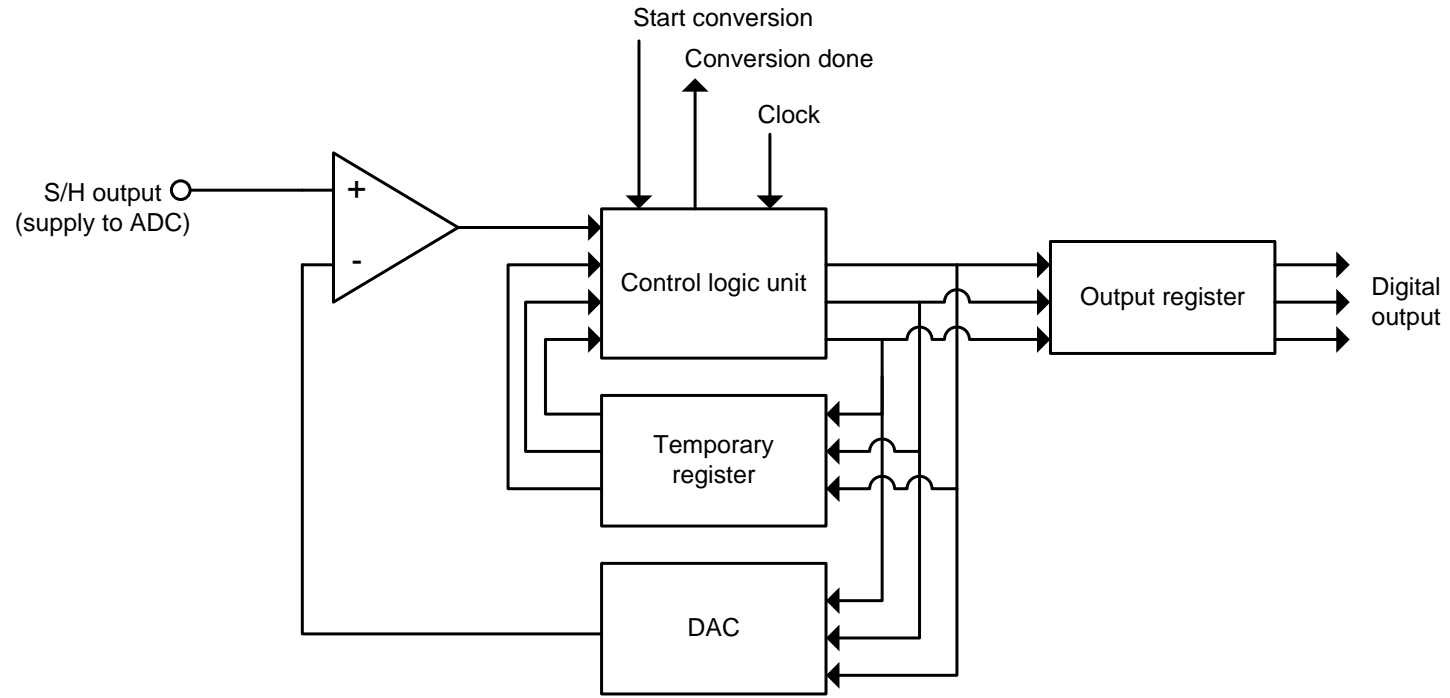

- digital system works on digitized samples of the signal




 - connecting the analog and digital world




- S/H – sample and hold circuit
- ADC – analog to digital conversion
- DAC – digital to analog conversion

 
- analog to digital conversion takes time
- continuous signal may change value during conversion process



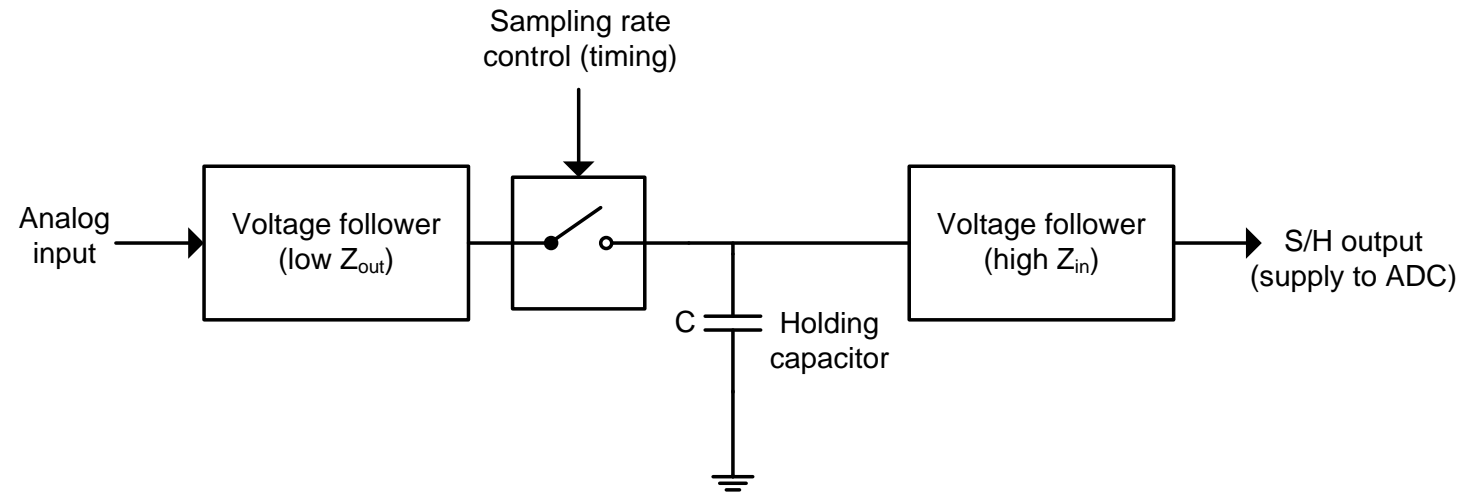
- stable (constant) value must be provided to ADC
- solution: use sample and hold circuit



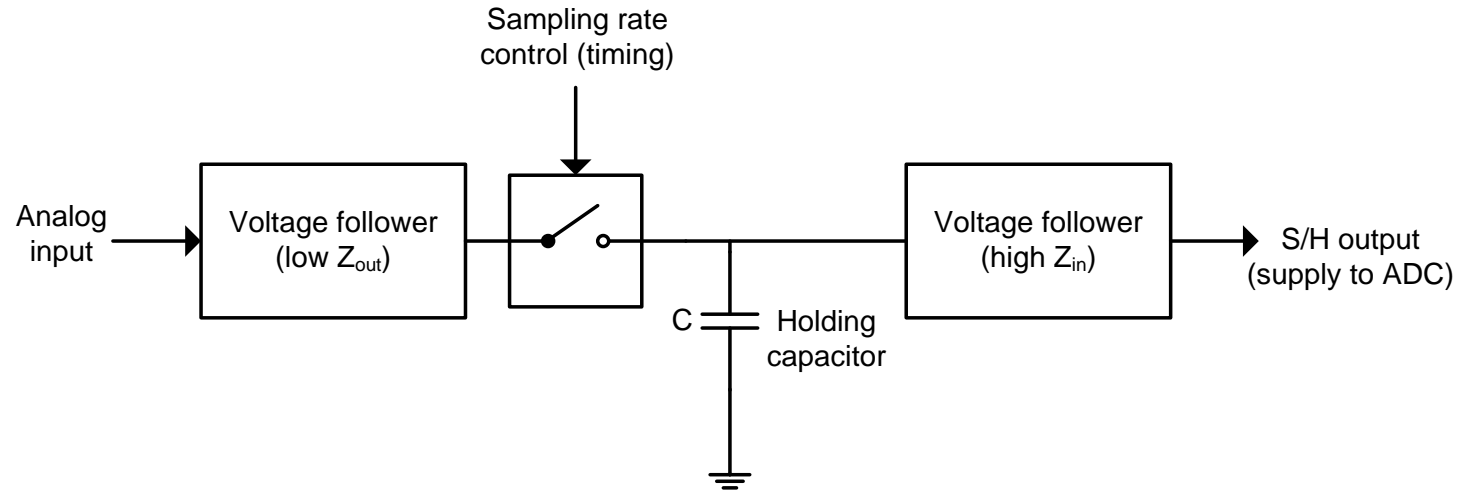
- concept
  - charge holding capacitor to voltage of analog signal
- requirements
  - charging needs to be done quickly
  - charge needs to stay on capacitor during ADC



 
- requirement: charging needs to be done quickly
  - charging time constant  $\tau_s = R_s C$ 
    - capacitance C fixed because of holding requirement (typically  $\sim 100$  pF)
  - to get a small  $\tau_s$ , the source resistance  $R_s$  must be small
  - use voltage follower with low output impedance
    - output voltage  $v_o = v_i$
    - op-amp has low output impedance











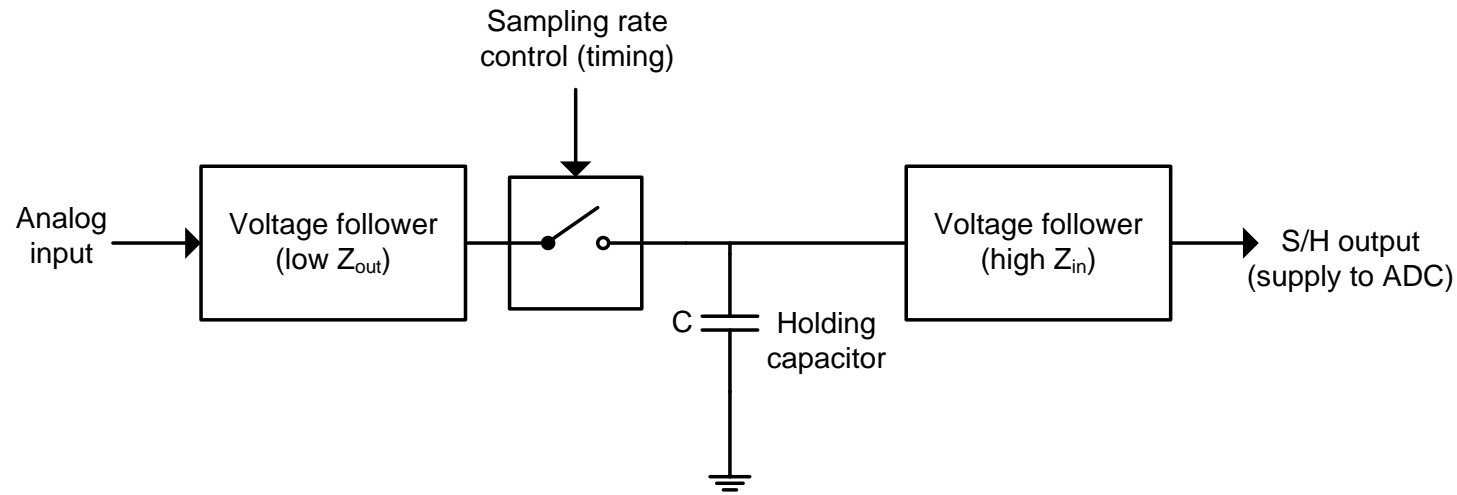

 - requirement: charge needs to stay on capacitor during ADC
  - circuit connected to holding capacitor must have high input impedance
  - use voltage follower which has high input impedance



      

- S/H – sample and hold circuit
- ADC – analog to digital conversion
- DAC – digital to analog conversion