


Sensing, Computing, Actuating

Sander Stuijk (s.stuijk@tue.nl)


INDUCTIVE SENSORS / DEMODULATION

(Chapter 2.5, 2.6, 2.10, 5.4)



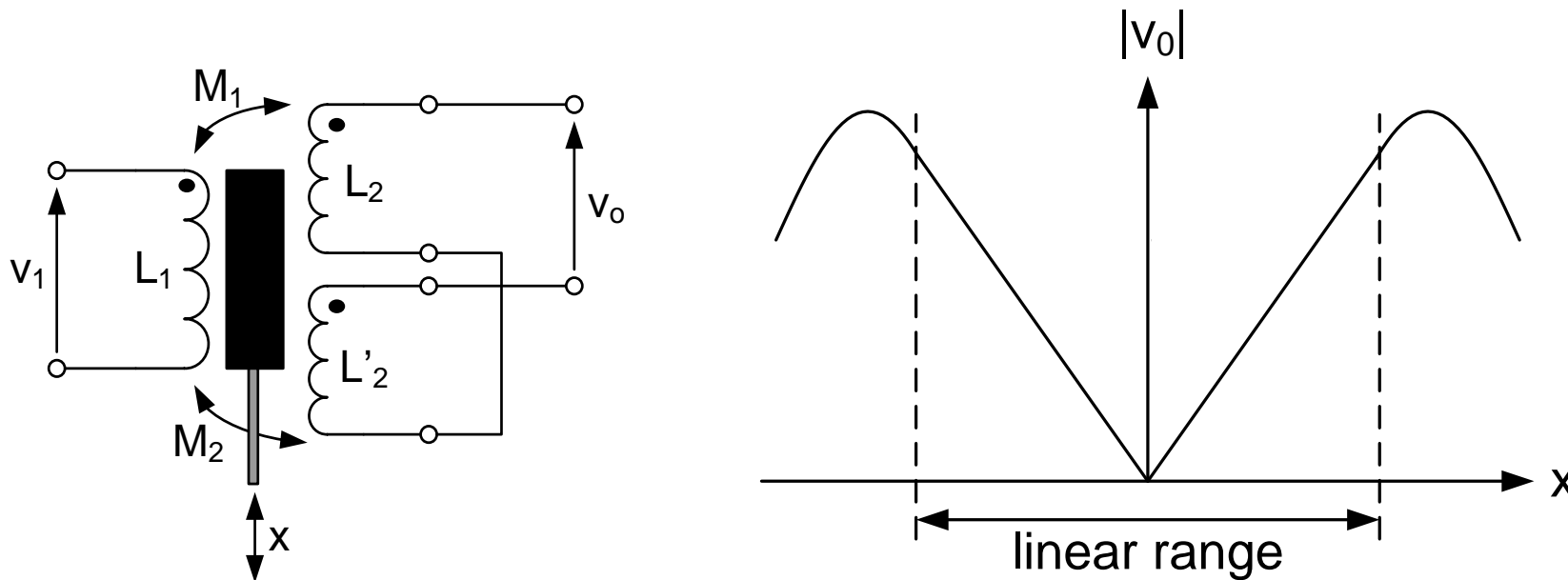
- Linear Variable Differential Transformer (LVDT)
 - two secondary coils in series-opposition
 - linear relation between output voltage and core displacement
 - operation based on mutual inductance







- assume sinusoidal excitation of primary circuit
 - $v_1(t) = V_1 \sin(\omega t)$
- output voltage of secondary circuit
 - $v_o(t) = S_\omega \cdot x \cdot V_1 \sin(\omega t + \phi)$
 - S_ω – sensitivity at frequency ω
 - x – displacement of the core from center
 - ϕ – phase shift (in voltage) from primary to secondary circuit
- S_ω and ϕ depend on
 - load R_L of measurement circuit
 - excitation frequency ω
- phase shift can be compensated

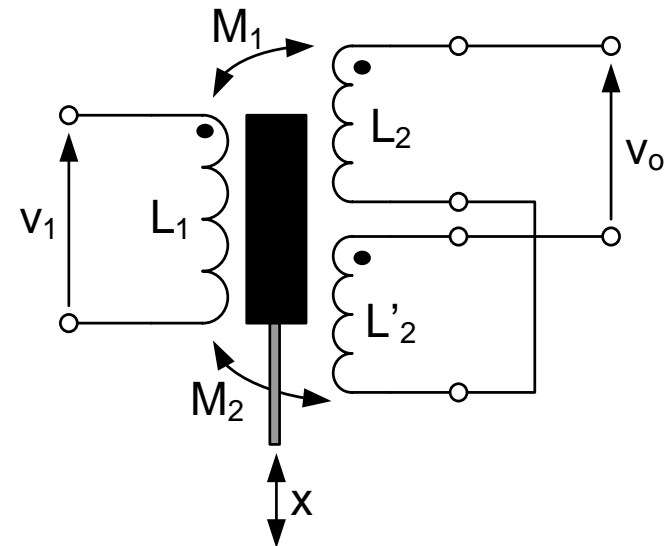

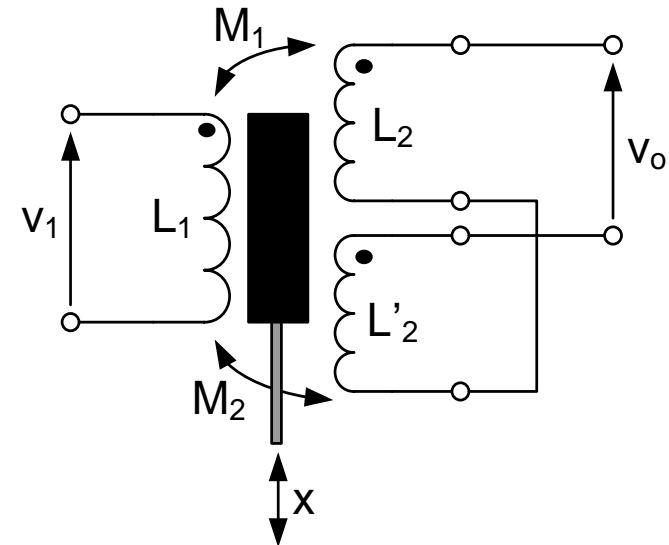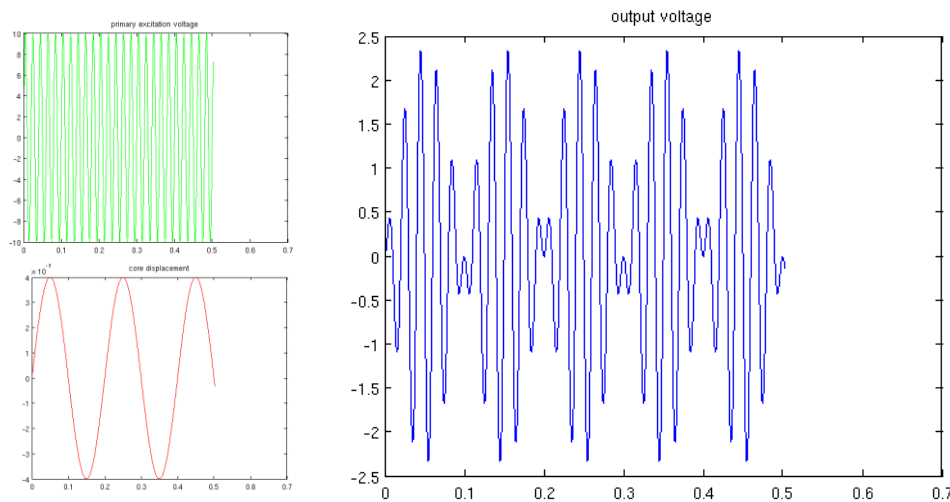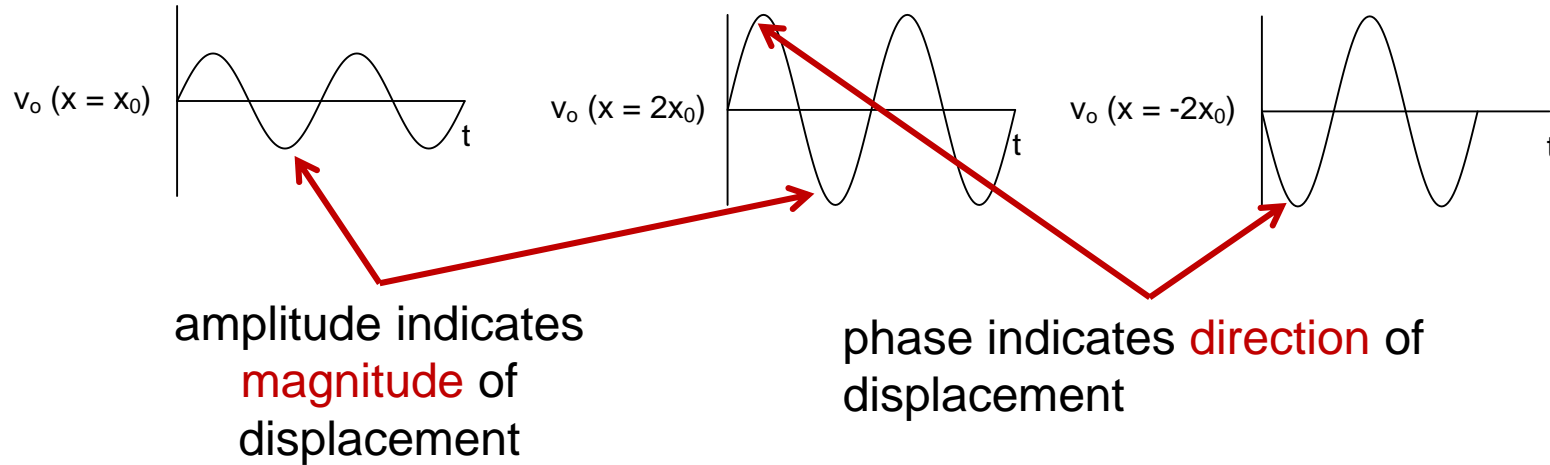- output signal of LVDT is amplitude modulated ac signal








Bridge rectifier with low-pass filtering

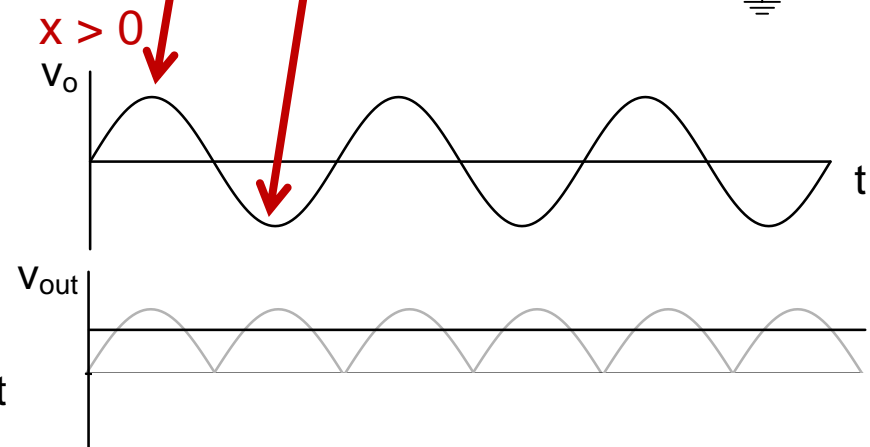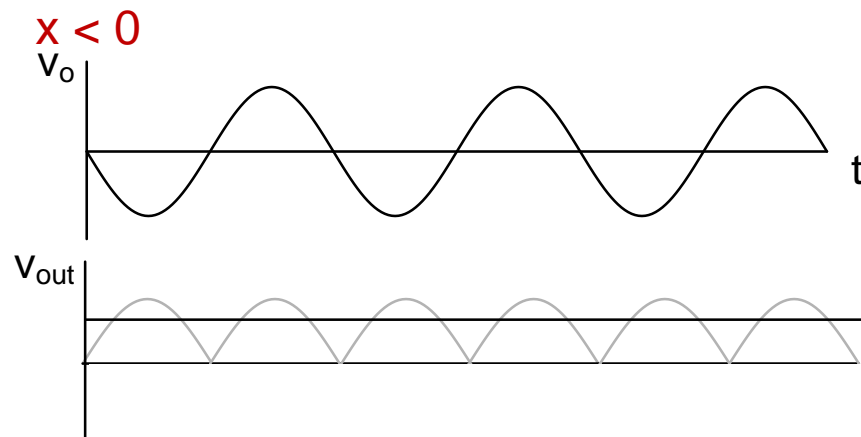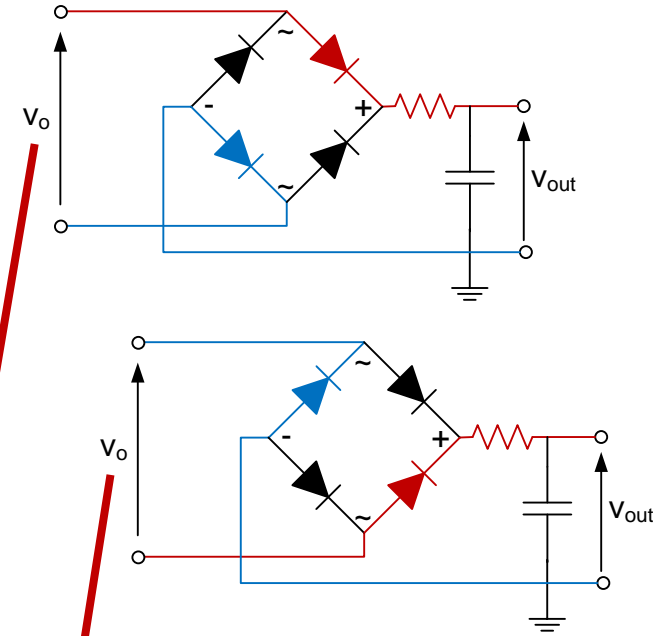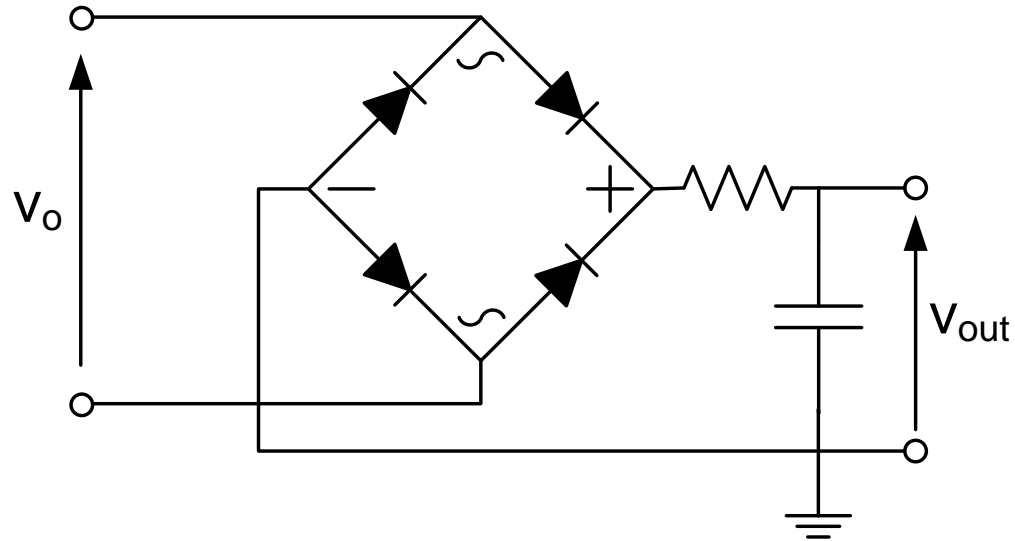

- amplitude of x recovered
- sign of x not recovered

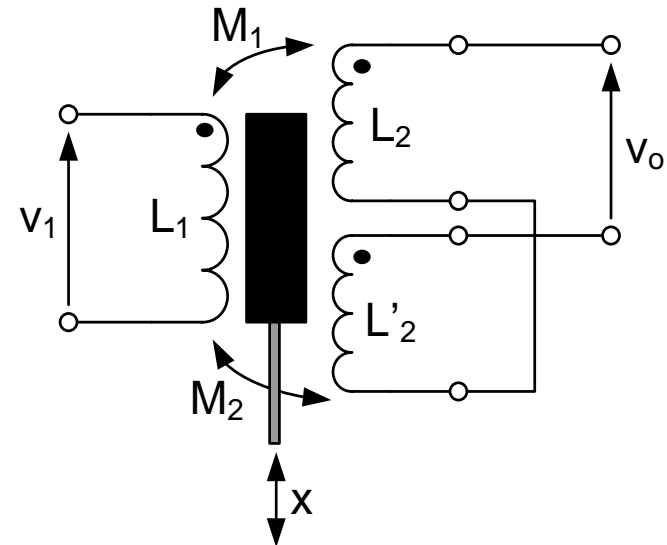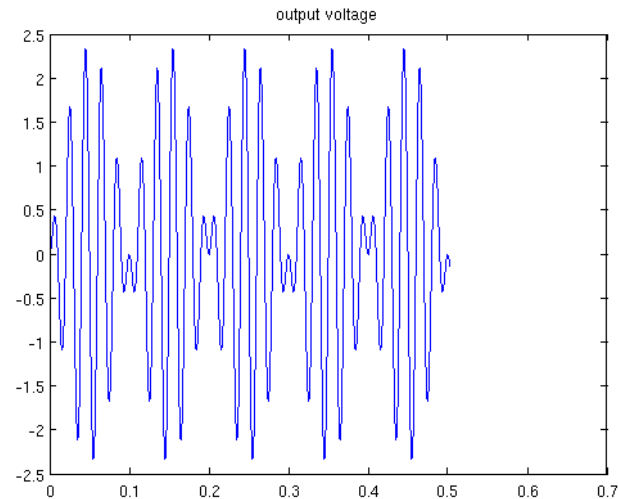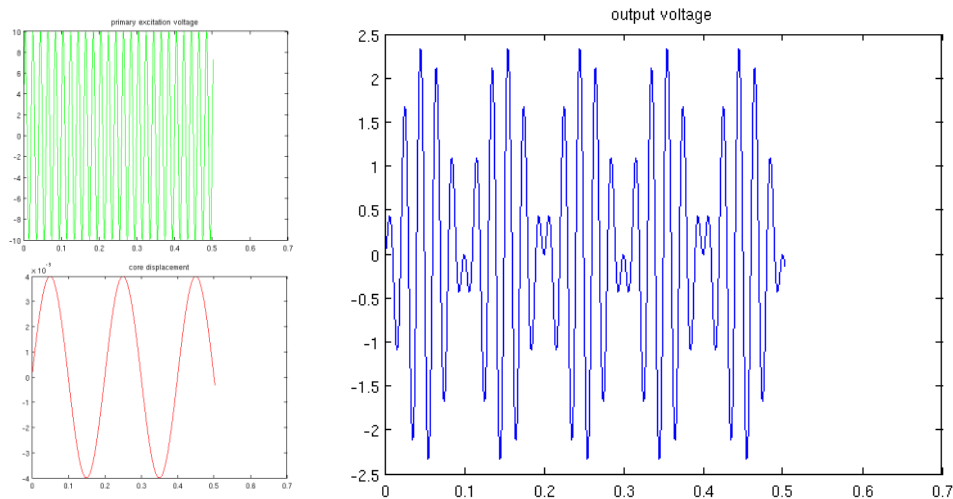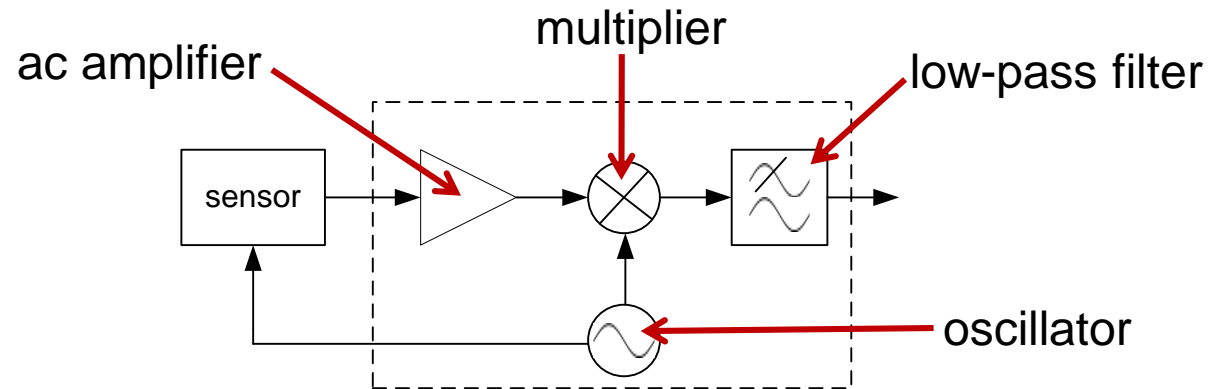- output signal of LVDT is amplitude modulated ac signal
- carrier amplifier and coherent detector



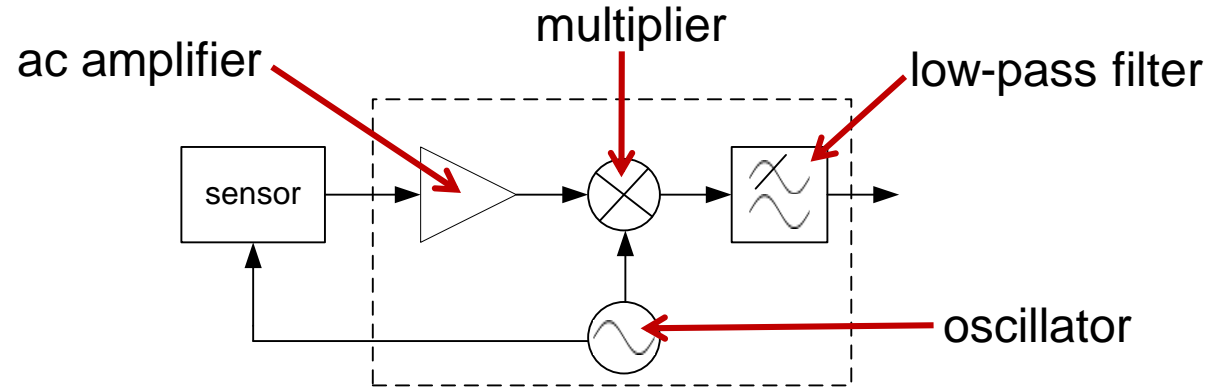

- excitation voltage of the sensor

$$v_e(t) = V_e \cos(2\pi \cdot f_e \cdot t)$$

- output of the sensor (assume no phase shift input/output voltage)

$$v_o(t) = S_\omega \cdot x(t) \cdot v_e(t)$$

- assume measured object is moving


$$x(t) = X \cos(2\pi \cdot f_x \cdot t + \phi_x)$$

- output voltage then equal to

$$v_o(t) = S_\omega X V_e \cos(2\pi \cdot f_x \cdot t + \phi_x) \cos(2\pi \cdot f_e \cdot t)$$

$$= \frac{S_\omega V_e X}{2} (\cos(2\pi(f_e - f_x)t - \phi_x) + \cos(2\pi(f_e + f_x)t + \phi_x))$$

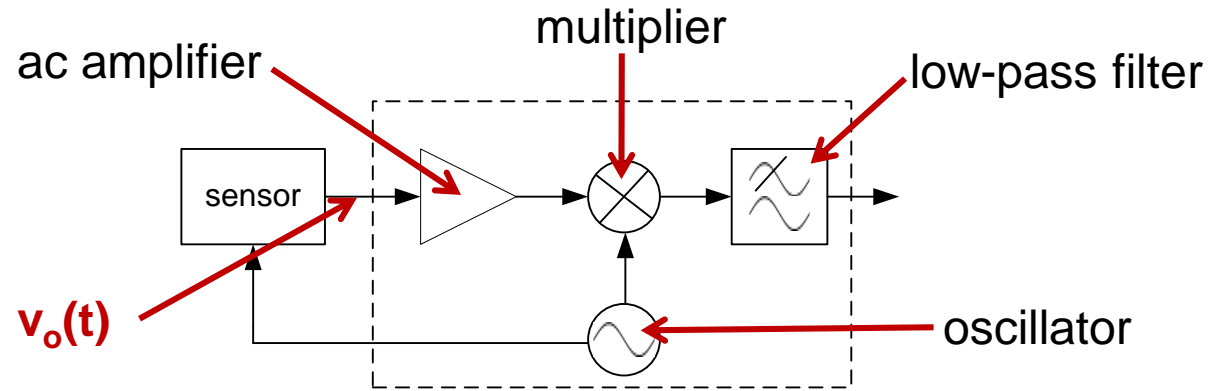
$$\cos(A) \cos(B) = \frac{1}{2} (\cos(A + B) + \cos(A - B))$$



- output of the sensor (=input to detector)

$$v_o(t) = \frac{S_\omega V_e X}{2} (\cos(2\pi(f_e - f_x)t - \phi_x) + \cos(2\pi(f_e + f_x)t + \phi_x))$$

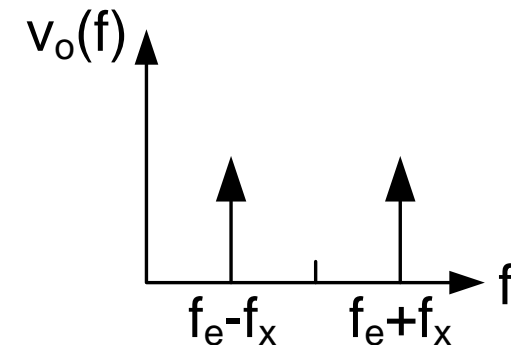- frequency spectrum (double-sideband signal)
- detector must recover $x(t) = X \cos(2\pi \cdot f_x \cdot t + \phi_x)$
 - maximal displacement of object (X)
 - frequency with which object changes direction (f_x)
 - phase shift of moving object (ϕ_x)



- multiplier inputs

$$v_r(t) = V_r \cos(\omega_r t + \phi_r)$$

$$v_o(t) = S_\omega \cdot x(t) \cdot v_e(t) = S_\omega x(t) \cdot V_e \cos(\omega_e t + \phi_e)$$

- signals have same phase ($\phi_r = \phi_e$)
- output of the multiplier

$$v_p(t) = v_r(t) \cdot v_o(t) = \frac{V_r V_e}{2} S_\omega x(t) [\cos((\omega_e - \omega_r) \cdot t) + \cos((\omega_e + \omega_r) \cdot t)]$$


- frequency of the signals are equal ($\omega_r = \omega_e$)

$$v_p(t) = \frac{V_r V_e}{2} S_\omega x(t) [1 + \cos(2\omega_e t)]$$

- output of low-pass filter

$$v_d(t) = LPF\{v_p(t)\} = \frac{V_r V_e}{2} S_\omega x(t)$$


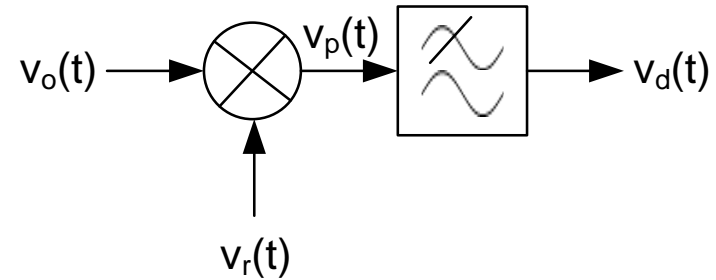
- output of demodulator equal to $x(t)$ (except for scaling factor)



- coherent detector output

$$v_d(t) = \frac{V_r V_e}{2} S_\omega x(t)$$

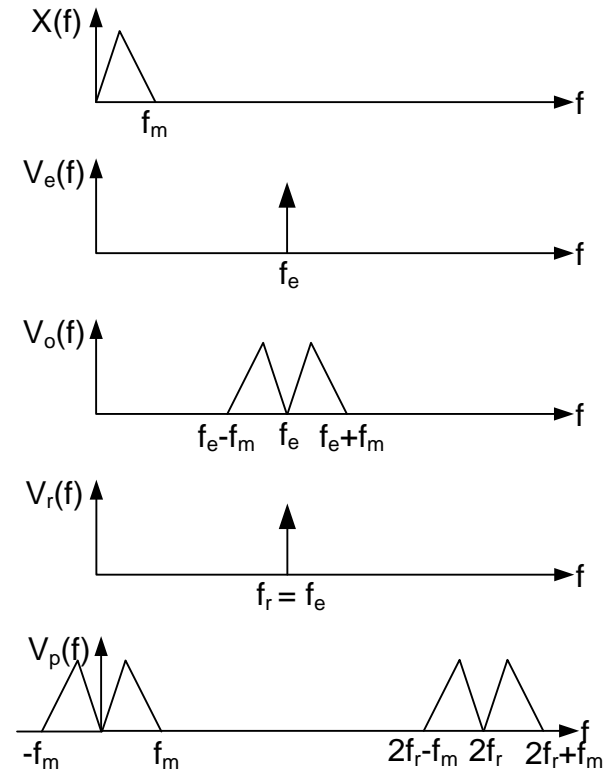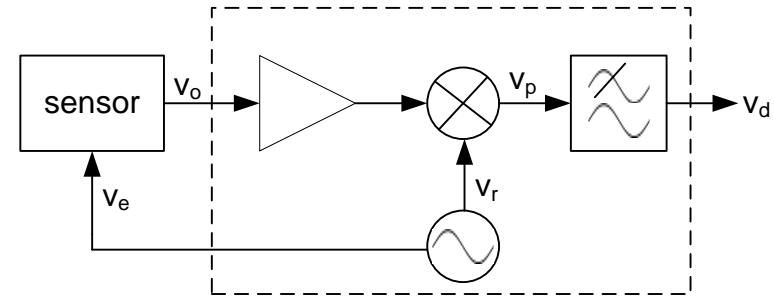- signal $x(t)$ does not have to be a sinusoid
 - band-limited input signal
 - sensor excitation signal
 - sensor output signal
 - reference signal
 - multiplier output signal



- coherent detector output

$$v_d(t) = \frac{V_r V_e}{2} S_\omega x(t)$$



- signal $x(t)$ does not have to be a sinusoid

- band-limited input signal



- multiplier output signal

- LPF frequency response

- detector output

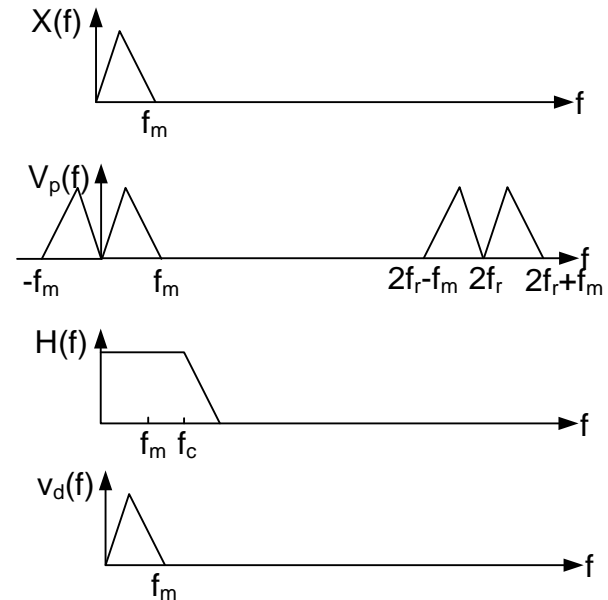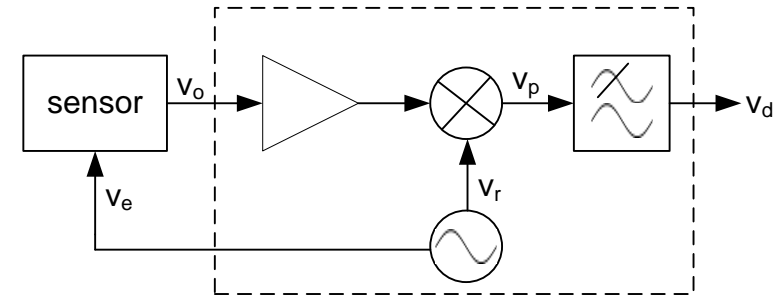

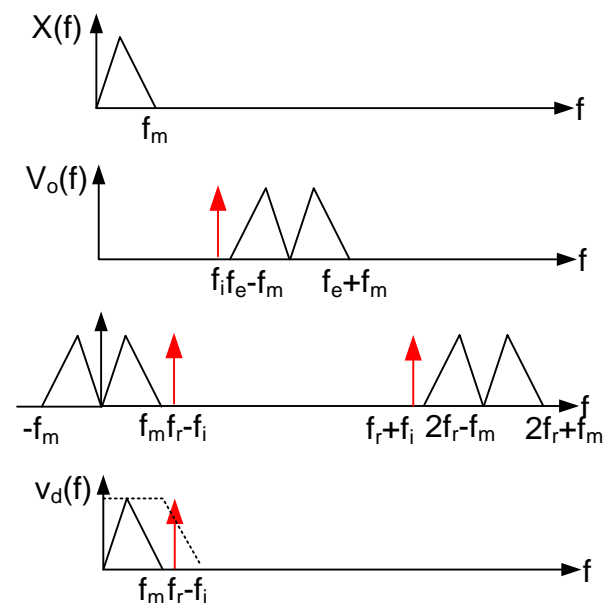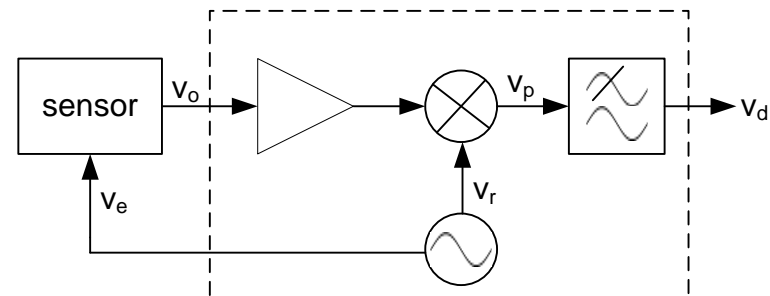- output of sensor may contain interference (e.g. from power line)
- signal $x(t)$ and interference signal
 - band-limited input signal
 - sensor output signal
 - multiplier output signal
 - detector output
- interference may be part of output signal
- attenuation of interference may be limited by LPF response



- amplitude response LPF

$$\left| \frac{V_d}{V_p} \right| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_c} \right)^2}}$$


- ω_c – corner frequency
- output voltage due to interference

$$|v_d|_i = \frac{V_r V_i}{2 \sqrt{1 + \left(\frac{\omega_e - \omega_i}{\omega_c} \right)^2}}$$


- normal mode rejection ratio (NMRR)

$$NMRR = 20 \log \left| \frac{v_d(\omega_e)}{v_d(\omega_i)} \right| = 10 \log \left[1 + \left(\frac{\omega_e - \omega_i}{\omega_c} \right)^2 \right] \approx 20 \log \left[\frac{|\omega_e - \omega_i|}{\omega_c} \right]$$

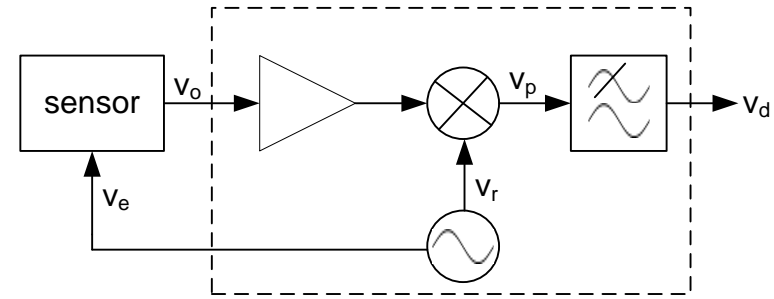- reflects capability of filter to reject interference
- approximation valid when $\omega_i \ll \omega_e$



$$v_i(t) = V_i \cos(\omega_i t)$$

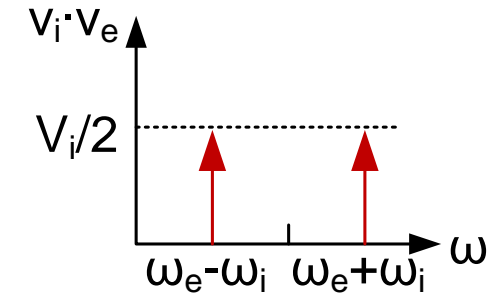

- **example – select frequencies for coherent detector**
- measure 5 Hz signal with amplitude error < 1 LSB for 8 bit ADC
- 40dB attenuation for 50 Hz interference at input of demodulator
- **which excitation and corner frequencies should be used?**
- amplitude error should be less than $1/2^8$

- corner frequency should be



$$\frac{1}{\sqrt{1 + \left(\frac{2\pi \cdot 5\text{Hz}}{2\pi \cdot f_c}\right)^2}} > 1 - \frac{1}{2^8} \Rightarrow f_c > \frac{5\text{Hz}}{\sqrt{\left(\frac{2^8}{2^8 - 1}\right)^2 - 1}} = 56.4\text{Hz}$$

- NMMR(50Hz) = 40dB, hence



$$40\text{dB} = 20 \cdot \log \left[\frac{f_e - 50\text{Hz}}{56.4\text{Hz}} \right] \Rightarrow f_e = 5.69\text{kHz}$$

- excitation frequency may be too high for practical circuit
 - use bandwidth filter in front of coherent detector
 - use high-order LPF filter

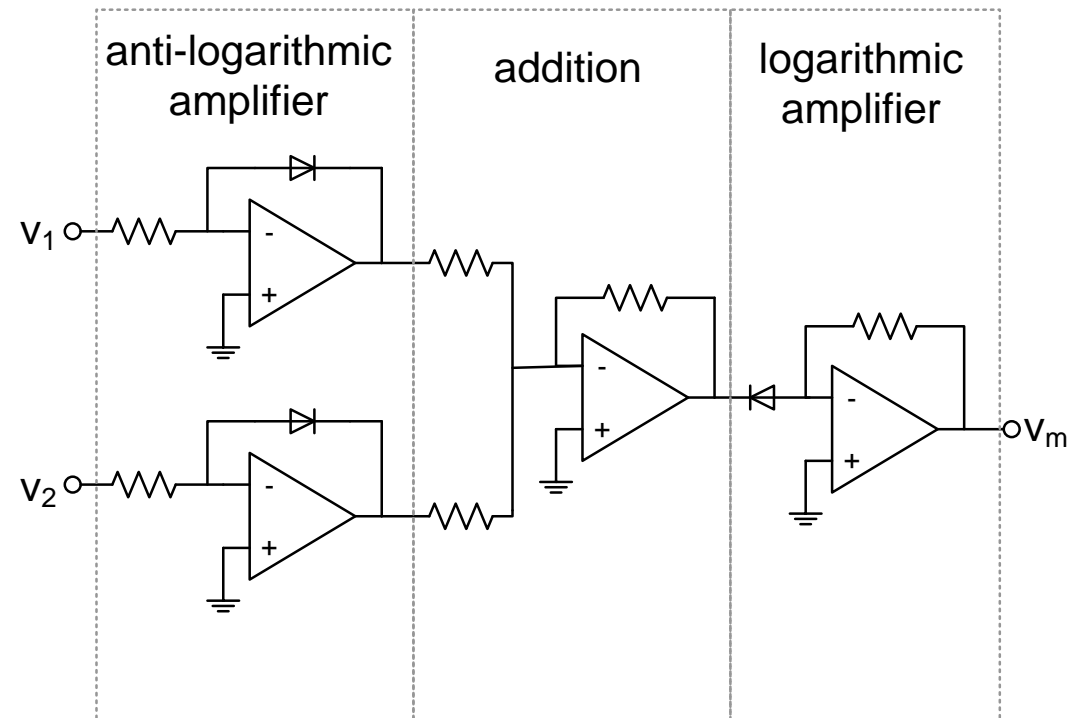
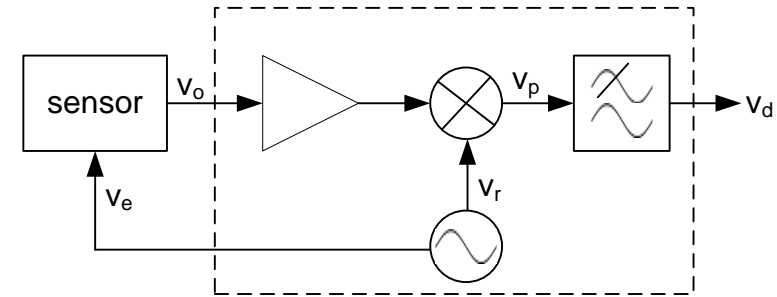
- multiplier at the center of the PSD
- analog multipliers are expensive
- two solutions for multiplier
 - use (anti-)logarithmic amplifiers
 - use symmetrical square wave as reference



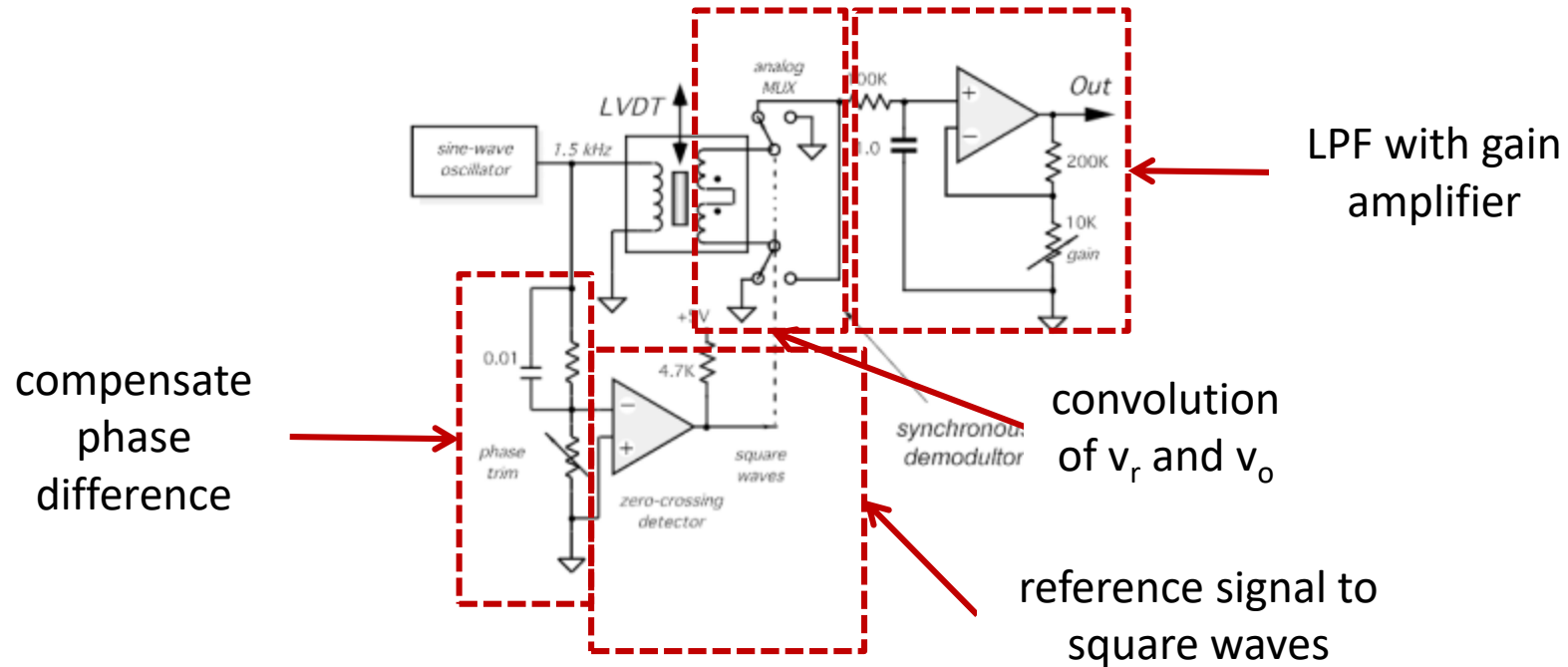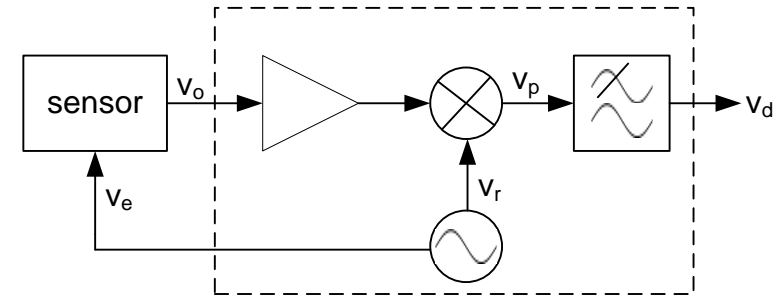- multiplier at the center of the PSD
- analog multipliers are expensive
- two solutions for multiplier
 - use (anti-)logarithmic amplifiers
 - use symmetrical square wave as reference



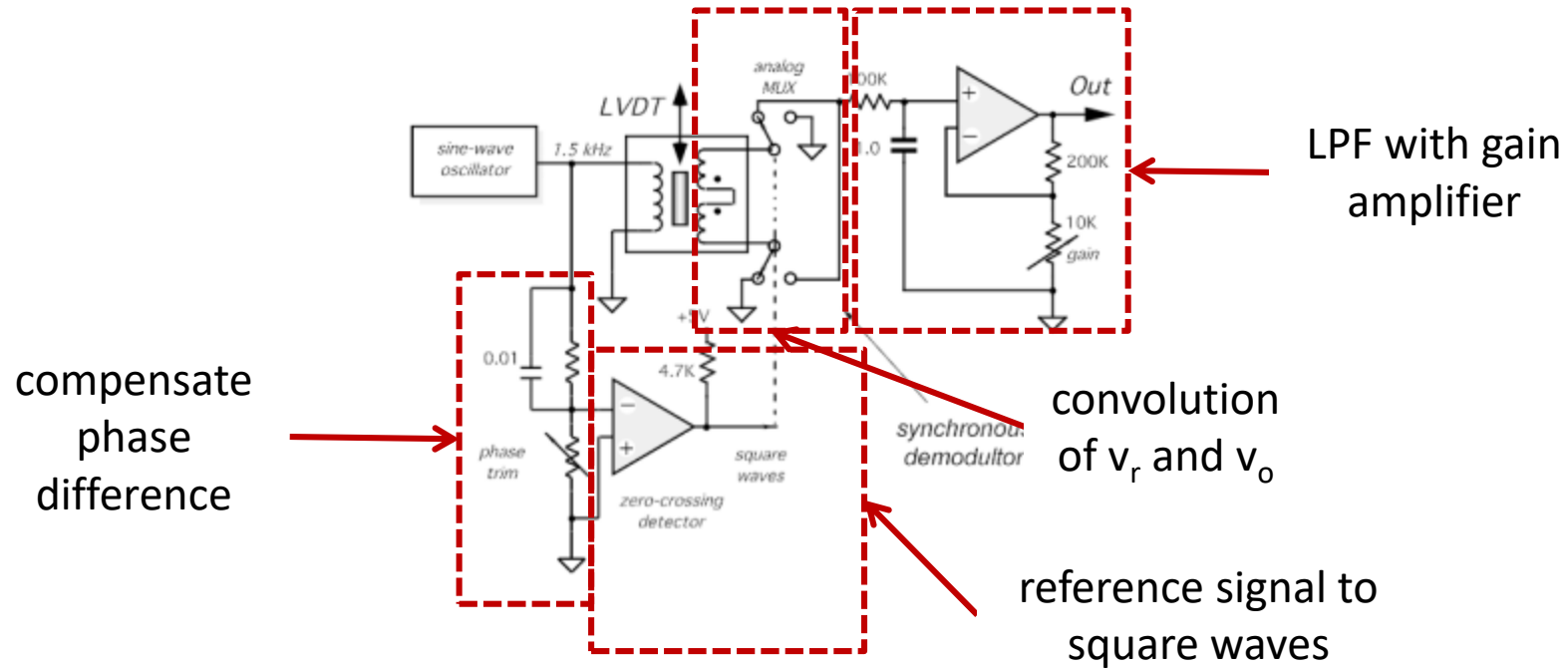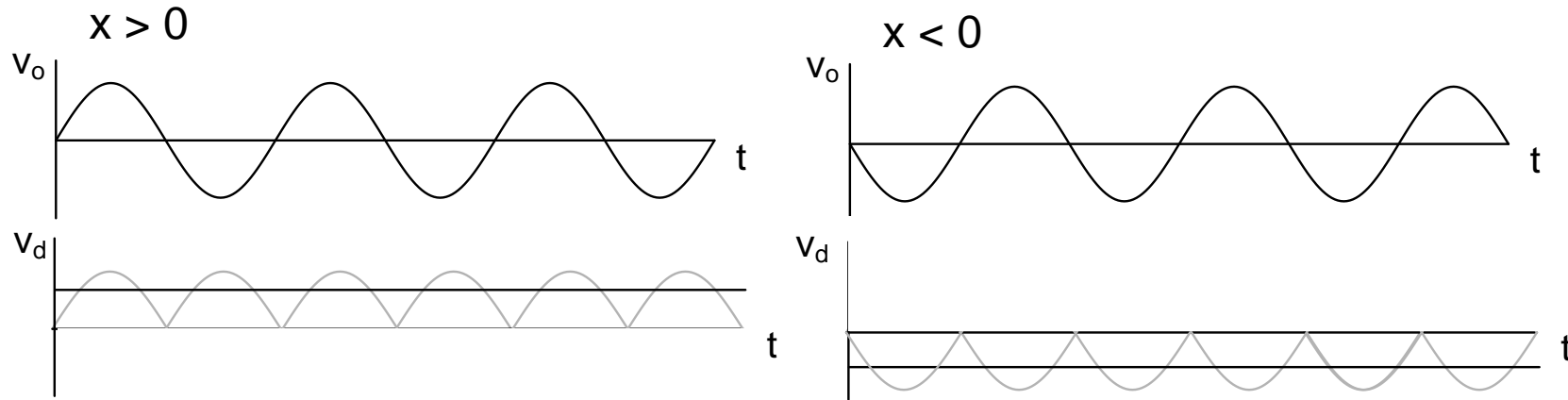Phase-sensitive (synchronous) demodulation



pro's and con's of LVDTs

(+) non-contact sensor (no friction)

(+) infinitesimal resolution

(+) solid and robust construction


(+) no hysteresis (mechanical and magnetic)

(+) output impedance is very low

(-) sensitive to stray magnetic fields (interference)

(-) complex signal processing required

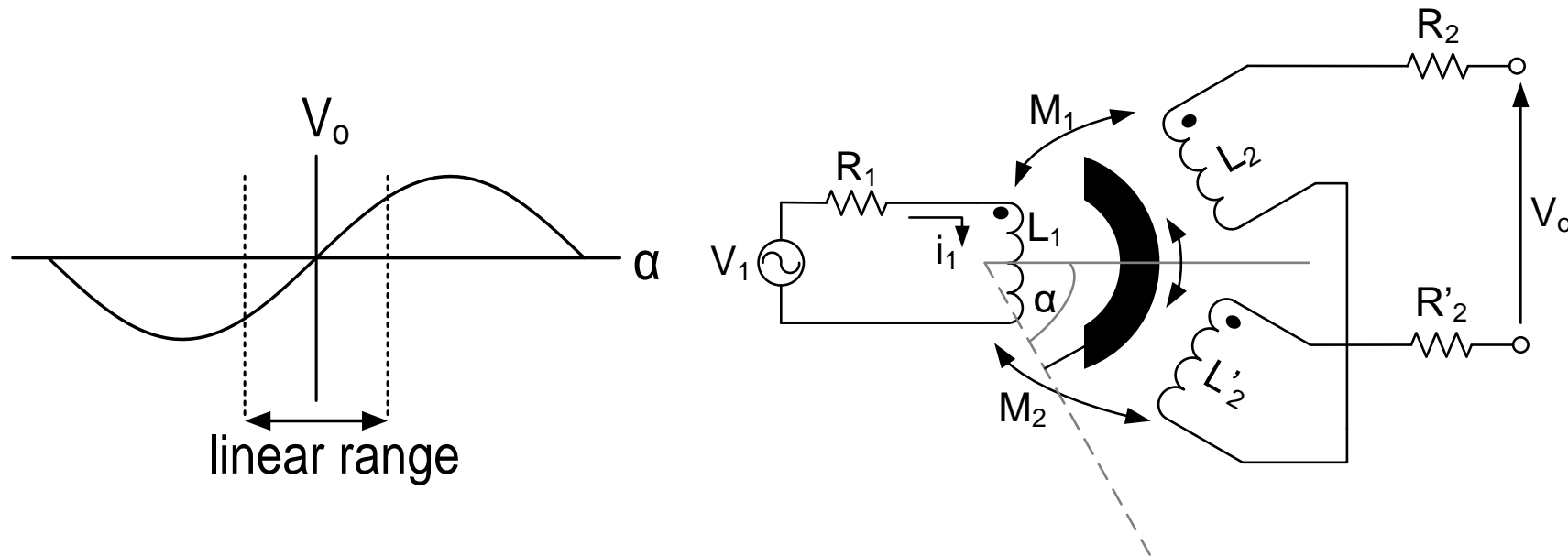- similar construction and operation as LVDT



- output of (unloaded) RVDT

$$V_o = S_\omega \alpha V_1$$

- linear relation between core rotation and output voltage
- linear measurement range limited to $\pm 20^\circ$
- measuring full rotation is not possible

- mutual inductance

$$M_{12} = N_2 \frac{\Phi_2}{i_1}$$

- flux linked by secondary winding


$$\Phi_2 = \mathbf{B} \cdot \mathbf{S} = BS \cos \alpha = \mu HS \cos \alpha = \mu \frac{N_1 i_1}{l} S \cos \alpha$$

- B – magnetic flux density
- S – secondary cross section
- H – magnetic field strength
- μ – magnetic permeability of the core
- l – length of primary winding

- mutual inductance is equal to

$$M_{12} = N_2 N_1 \frac{\mu}{l} S \cos \alpha = M \cos \alpha$$

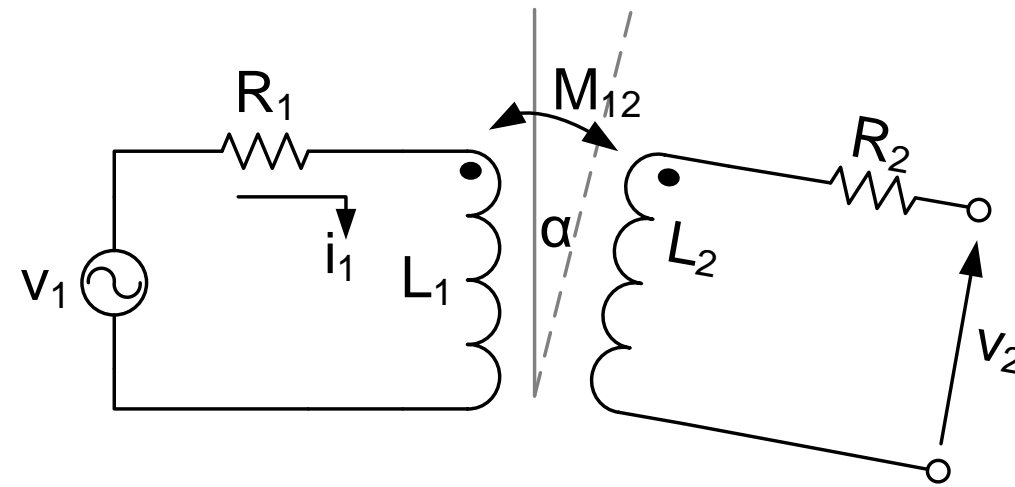- mutual inductance has relation with angle



- mutual inductance

$$M_{12} = N_2 N_1 \frac{\mu}{l} S \cos \alpha = M \cos \alpha$$

- what is the voltage on the secondary winding?

- consider open-circuit situation

- voltage on primary winding

$$v_1 = V_p \sin(\omega t)$$

- current through primary winding


$$i_1 = I_p \cos(\omega t)$$

- voltage on secondary winding

$$v_2 = M_{12} \frac{di_1}{dt}$$

$$\Rightarrow V_2 = s I_1 M_{12} = s I_p M \cos(\alpha) \cos(\omega t) = k \cos(\alpha) \cos(\omega t)$$

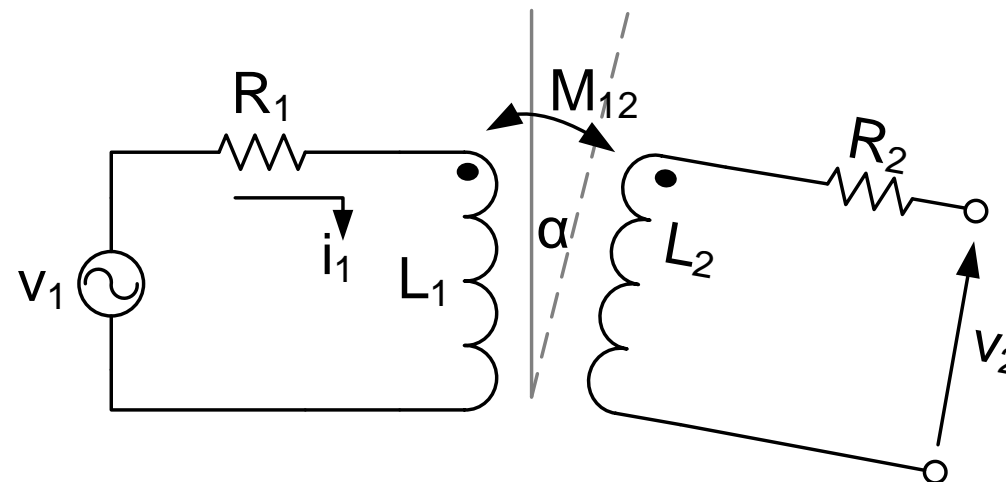- amplitude of output voltage depends on angle between windings



- rotor winding acts as primary winding
- two stator windings at 90° act as secondary windings

- voltage on primary winding

$$v_i = V_p \sin(\omega t) \Rightarrow i_i = I_p \cos(\omega t)$$

- induced voltages on secondary windings


$$v_{o1} = K \cos(\omega t) \cos(\alpha)$$


$$v_{o2} = K \cos(\omega t) \sin(\alpha)$$



- output voltage is product of

- measured object (α)
- excitation voltage (v_i)

- outputs differ by 90° phase difference

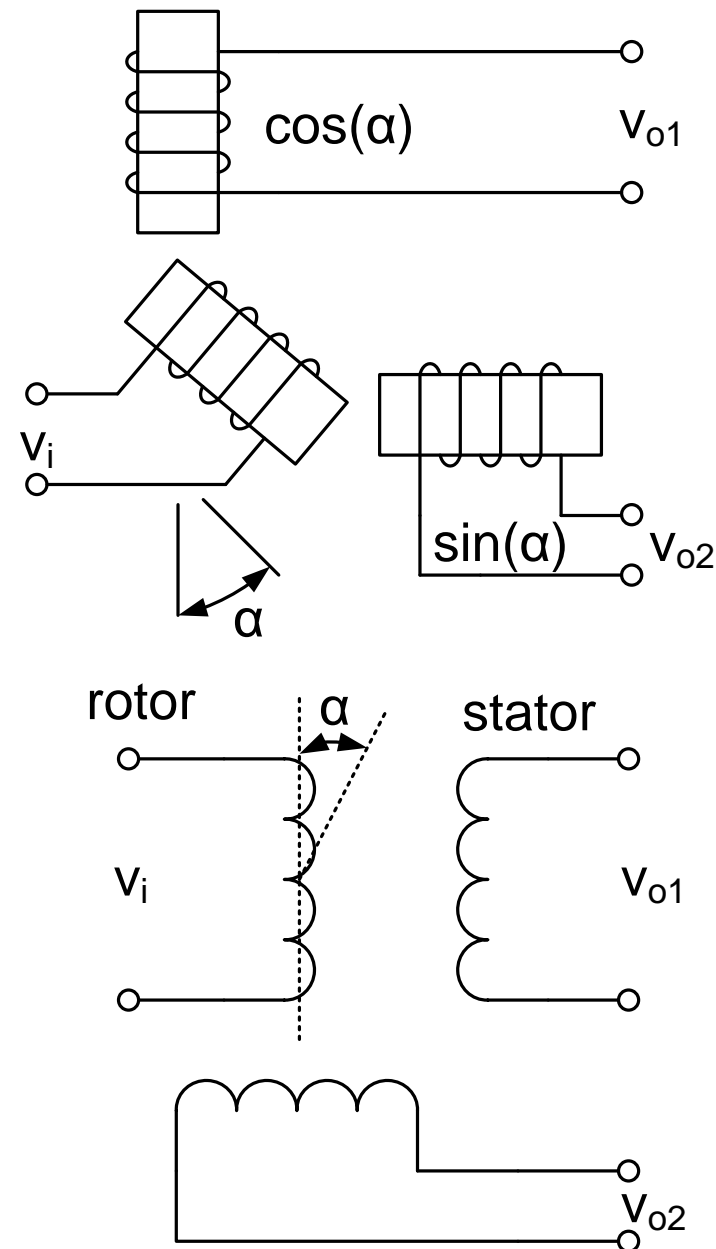



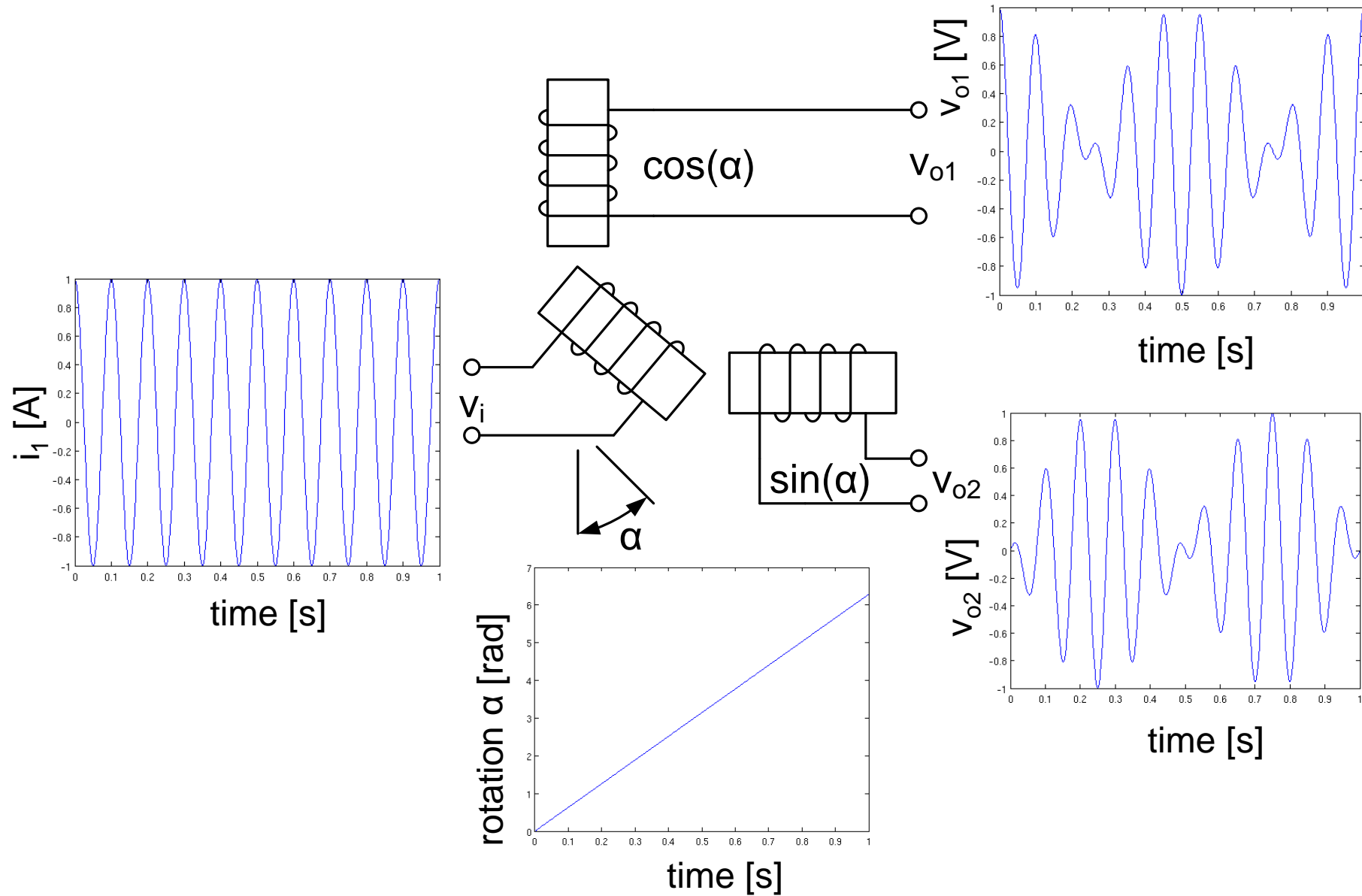


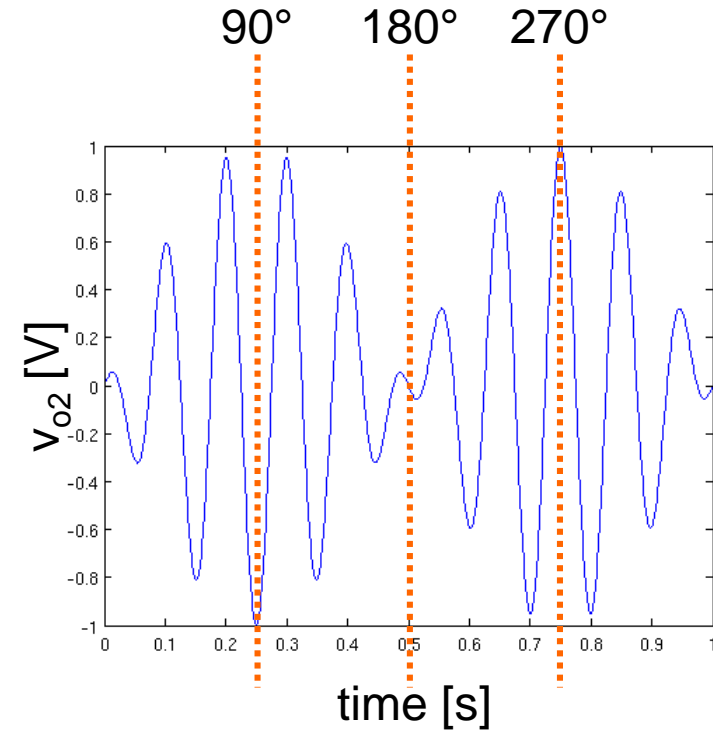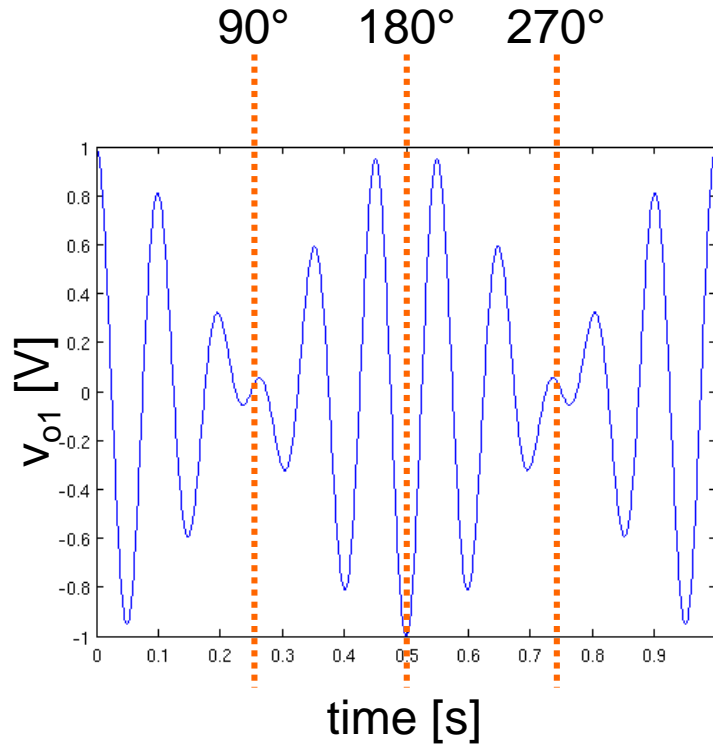

	0°	90°	180°	270°
v_{o1} [V]	1	0	-1	0
v_{o2} [V]	0	-1	0	1

- bridge rectifier can be used to recover angle between $0^\circ \leq \alpha \leq 90^\circ$
- phase sensitive detector needed to recover angle in all quadrants

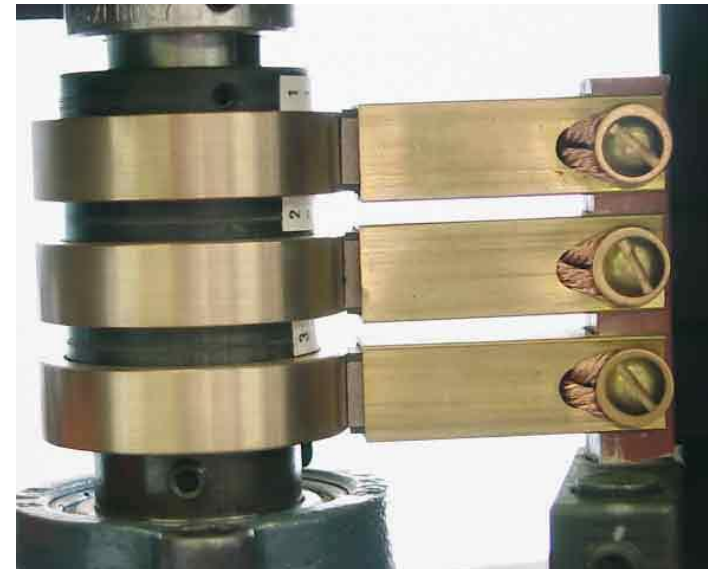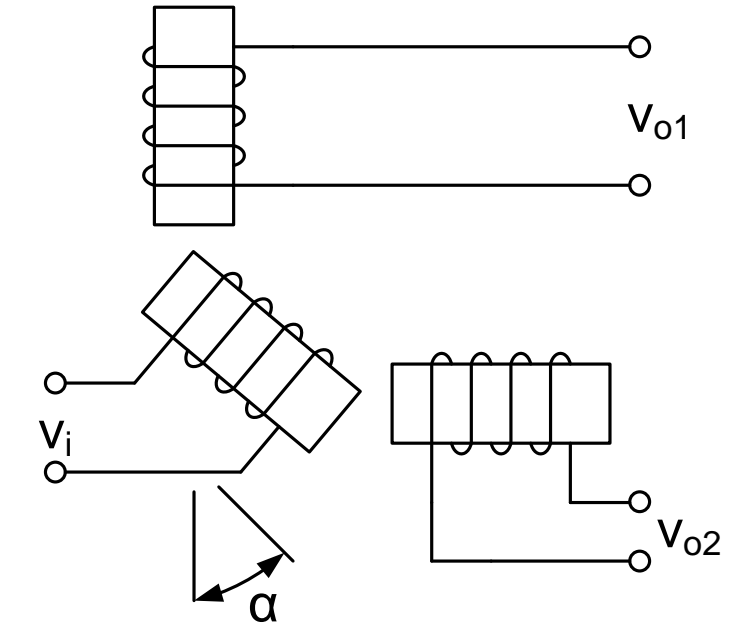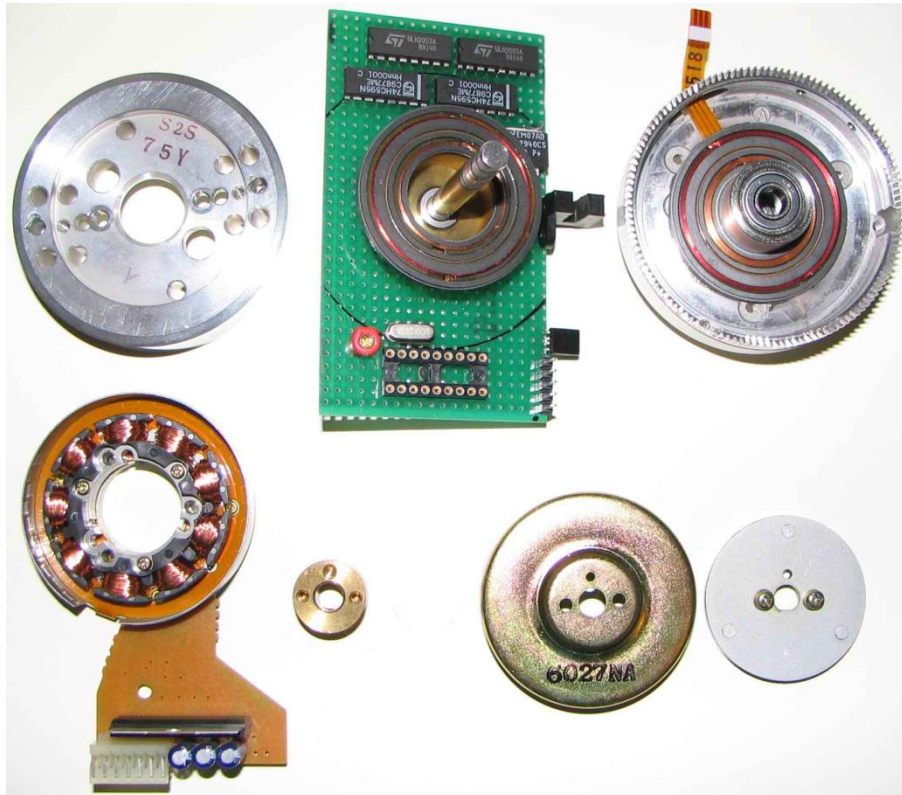- how to supply v_i to the rotor?
 - use brushes or slips (friction, wear)
 - brushless transformer (preferred)



- how to supply v_i to the rotor?
 - use brushes or slips (friction, wear)
 - brushless transformer (preferred)

