

Sensing, Computing, Actuating

Lecture 6 - Amplifiers

Exercise 1: Tire-pressure monitoring system

A tire-pressure monitoring system (TPMS) is an electronic system to measure the air pressure inside the tires of a vehicle. A TPMS sensor delivers real-time information on the tire pressure to the driver of the vehicle by displaying the pressure inside the tires or through a simple light that turns on when the pressure becomes too low. There exist two different types of TPMS sensors. The indirect type derives the tire pressure through external factors such as the rotation speed of the wheels. The direct type measures the pressure by placing a sensor inside the tire. This sensor measures the air pressure inside the tire and send the result through a wireless connection to the ECU who further processes the signal and controls the actuators (see Figure 1). The wireless sensor placed inside the tire (see Figure 2) measures the air pressure using a number of strain gauges. The voltage across these sensors is too low to immediately be transmitted wireless. For this purpose, the signal should first be amplified¹. An instrumentation amplifier can be used for this purpose.

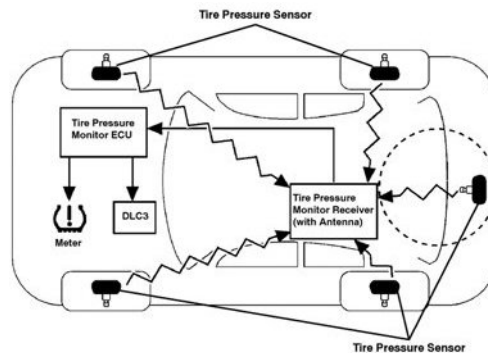


Figure 1: Tire-pressure monitoring system.

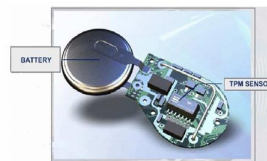


Figure 2: Tire-pressure sensor.

An instrumentation amplifier is a differential amplifier who at the same time has a high input-impedance, a low output-impedance and a high common-mode rejection-ratio (CMRR). The gain of an instrumentation amplifier can typically be changed with a single resistor. Figure 3 shows an instrumentation amplifier that consists of two operational amplifiers. (You may assume that these op-amps have an ideal behavior.)

¹Additional signal processing is often applied in practice such that it becomes for example possible to detect errors in the wireless transmission.

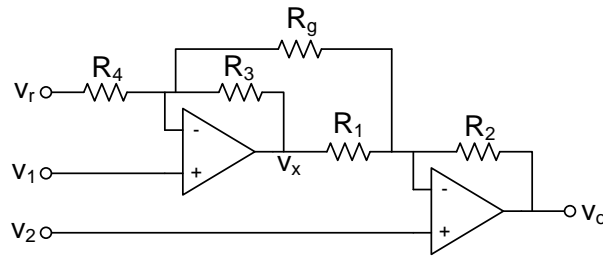


Figure 3: Instrumentation amplifier with two op-amps.

- (a) Show that the output voltage v_o of the instrumentation amplifier shown in Figure 3 is equal to:

$$v_o = \left(1 + k + \frac{R_2 + R_4}{R_g} \right) v_d + v_r$$

with $v_d = v_2 - v_1$. Assume that $R_4/R_3 = R_2/R_1 = k$ (i.e., the CMRR is infinite).

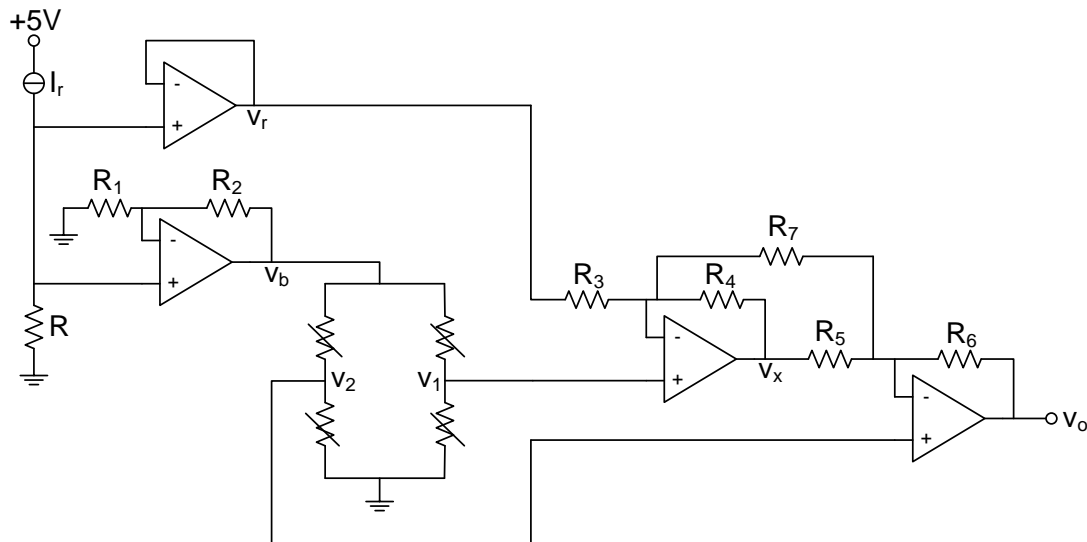


Figure 4: Signal processing circuit for a resistive pressure sensor.

The instrumentation amplifier from Figure 3 is used to amplify the output signal of a bridge circuit with four strain gauges (see Figure 4). The strain gauges each have a resistance R_0 of 4000Ω and a sensitivity of 1 mV/psi when a supply voltage of 12 V is placed across the strain gauges. The current source delivers a stable current $I_r = 100 \mu\text{A}$.

- (b) Show that the output voltage v_o of this circuit is equal to:

$$v_o = (v_2 - v_1) \left(1 + \frac{R_6}{R_5} + \frac{R_3 + R_6}{R_7} \right) + V_r = (v_2 - v_1) G + v_r$$

assume that $R_3/R_4 = R_6/R_5 = k$. (Hint: use the result from the question 1(a).)

- (c) The circuit should have an output voltage v_o of 0.5 V at a pressure of 0 psi . What value should R have to satisfy this constraint?
- (d) The bridge circuit is supplied with a voltage v_b . What ratio should R_2/R_1 have such that the supply voltage of the bridge is equal to 3.5 V ?
- (e) At a pressure of 100 psi , the circuit must have an output voltage v_o of 4 V . What gain G should the instrumentation amplifier have to satisfy this constraint?
- (f) Assume that $R_3 = R_4 = R_5 = R_6 = 100 \text{ k}\Omega$. What value should R_7 have to realize the gain that you computed in the previous question?