

Sensing, Computing, Actuating

Lecture 14 - Thermocouple

Exercise 1: Gasoline exhaust gas temperature measurement

To maximize the fuel efficiency of a gasoline engine and to minimize the toxic gases exhausted by the engine, the engine control unit will regulate the fuel/air mixture to keep the temperature of the exhaust gas within certain limits. Exhaust gases in a gasoline engine are lower than in a diesel engine, but they may still reach temperatures between 700°C and 1200°C . A K-type thermocouple can be used to measure the temperature of this gas. Figure 1 shows a circuit to measure a temperature T by means of such a K-type thermocouple. The ambient temperature T_a at the reference junction is compensated using a NTC thermistor. The thermocouple has a sensitivity $k = 41 \mu\text{V}/\text{K}$. The NTC thermistor has $B = 3546 \text{ K}$ and resistance $R_0 = 10 \text{ k}\Omega$ at 25°C . The voltage source $V_R = 1.35\text{V}$ and $R_2 = 100 \Omega$. The output voltage of the circuit $v_o = k \cdot T$ (with T in $^{\circ}\text{C}$).


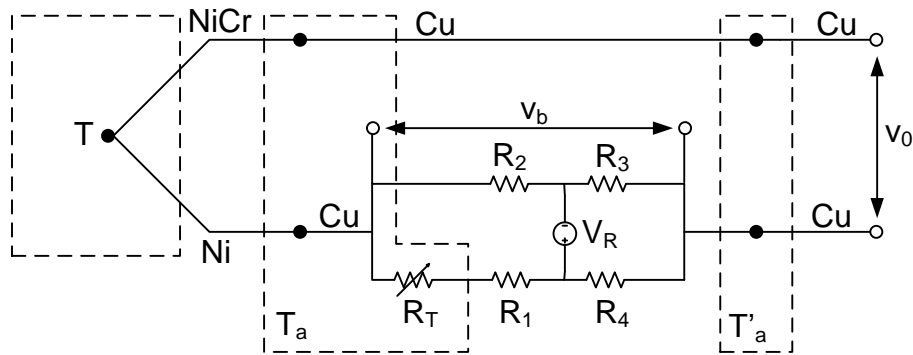


Figure 1: Circuit for cold junction compensation.

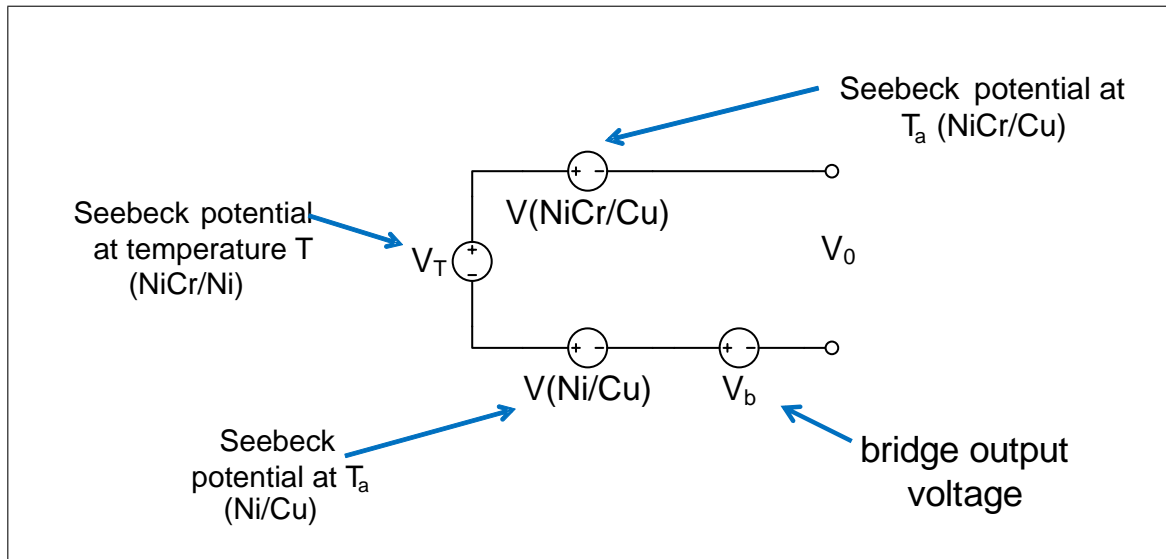- (a) Draw an equivalent circuit that represents the three thermocouple junctions and the bridge as voltage sources. (Note your circuit should contain in total four voltage sources, i.e., V_T , $V(\text{NiCr}/\text{Cu})$, $V(\text{Ni}/\text{Cu})$, and V_b .)

Answer: Assumption: volt meter has high impedance. As a result, the current in thermocouple wires is low.



- (b) Show that the bridge output voltage V_b should be equal to $k \cdot T_a$ to compensate for the ambient temperature T_a . (Hint: use law of intermediate metals.)

Answer: It follows from the circuit that

$$V_o = V_T - V(NiCr/Cu) |_{T_a} + V(Ni/Cu) |_{T_a} + V_b$$

The ambient temperature should not affect measurement. It must therefore hold that

$$V_o = V_T$$

Applying law of intermediate metals gives

$$-V(NiCr/Cu) |_{T_a} + V(Ni/Cu) |_{T_a} = -V(NiCr/Ni) |_{T_a} \approx -kT_a$$

We need $V_b = kT_a$ to compensate for the ambient temperature at the reference junction.

- (c) Show that the bridge sensitivity at the reference junction is equal to:

$$\frac{dV_b}{dT} = \left(\frac{\frac{BR_2}{T^2} R_0 e^{B(1/T-1/T_0)}}{(R_1 + R_0 e^{B(1/T-1/T_0)} + R_2)^2} \right) V_R$$

Answer: The bridge circuit is shown (rearranged) below. The + and - sign on V_b follow from the choice made in assignment (a). Note that the top of V_r is negative. This follows from Figure 1.

The bridge output is equal to:

$$V_b = -V_R \cdot \left(\frac{R'_1}{R'_1 + R_2} - \frac{R_4}{R_3 + R_4} \right) = V_R \cdot \left(\frac{R_4}{R_3 + R_4} - \frac{R'_1}{R'_1 + R_2} \right)$$

with $R'_1 = R_1 + R_T = R_1 + R_0 e^{B(1/T-1/T_0)}$.

Note that you can also compute the bridge output voltage as:

$$V_b = V_R \cdot \left(\frac{R_2}{R_1 + R_2} - \frac{R_3}{R_3 + R_4} \right)$$

The sign on V_r changes in this case. The output voltage V_b will not change. Hence you will find the same sensitivity as when you continue with the earlier expression.

Use quotient rule to compute derivative:

$$\frac{d}{dx} \frac{g(x)}{h(x)} = \frac{g'(x)h(x) - g(x)h'(x)}{(h(x))^2}$$

The derivative of R_T is given by:

$$\frac{dR_T}{dT} = \frac{d}{dT} R_0 e^{B(1/T - 1/T_0)} = -\frac{B}{T^2} R_T$$

Hence, the derivative of the bridge voltage (sensitivity) is equal to:

$$\begin{aligned} \frac{dV_b}{dT} &= \left(\frac{-\frac{B}{T^2} R_T (R_1 + R_T + R_2) + (R_1 + R_T) \frac{B}{T^2} R_T}{(R_1 + R_T + R_2)^2} \right) V_r \\ &= \left(\frac{\frac{B}{T^2} R_2 R_T}{(R_1 + R_T + R_2)^2} \right) V_r \\ &= \left(\frac{\frac{B R_2}{T^2} R_0 e^{B(1/T - 1/T_0)}}{(R_1 + R_0 e^{B(1/T - 1/T_0)} + R_2)^2} \right) V_R \end{aligned}$$

- (d) In question 1(b), you showed that the output voltage V_b should be equal to $k \cdot T_a$ to compensate for the ambient temperature T_a . Hence, the bridge should have a sensitivity k . What value for R_1 should be used to ensure that the bridge sensitivity is equal to k ?

Answer: We derived earlier that it must hold that $V_b = kT_a$. It follows from this requirement that the bridge sensitivity should be equal to k . In the previous part we computed the sensitivity of the bridge. This bridge sensitivity is not constant (k) as required. Instead, the bridge sensitivity depends on the temperature. As a result, the bridge output is non-linear. We can however choose a linearization criterion by choosing the desired slope k at 25 °C.

It must hold:

$$\frac{dV_b}{dT} = \left(\frac{\frac{B R_2}{T^2} R_0 e^{B(1/T - 1/T_0)}}{(R_1 + R_0 e^{B(1/T - 1/T_0)} + R_2)^2} \right) V_R = k$$

It is given that: $R_2 = 100 \Omega$, $R_0 = 10 \text{ k}\Omega$, $B = 3546 \text{ K}$, $T_0 = 25^\circ\text{C}$, $T = 25^\circ\text{C}$, $V_r = 1.35 \text{ V}$, $k = 41 \mu\text{V/K}$.

Solving this equation yields $R_1 = 26160 \Omega$.

- (e) What ratio should R_3/R_4 have to ensure that the circuit shown in Figure 1 compensates the ambient temperature at the reference junction?

Answer: We computed before that it must hold that $V_b = kT_a$ to compensate for the ambient temperature at the reference junction. We can choose **any** value for T_a , but the easiest is to use $T_a = 25^\circ\text{C}$. (Note that any other value for T_a will yield the same ratio R_3/R_4 .)

It must thus hold that

$$V_b(25^\circ C) = 41\mu V \cdot 25^\circ C = 1.0mV$$

The bridge output is equal to

$$V_b = \left(\frac{R_4}{R_3 + R_4} - \frac{R'_1}{R'_1 + R_2} \right) V_R$$

Using $R_2 = 100 \Omega$, $R_1 = 22097 \Omega$, $T = 25^\circ C$, and $V_R = 1.35 \text{ V}$, we find $R_3/R_4 = 2.0 \cdot 10^{-3}$.